


Electrical Circuit and Electronics

Semiconductor Diodes

sharafat.ali@ieee.org



Reference Books Recommended

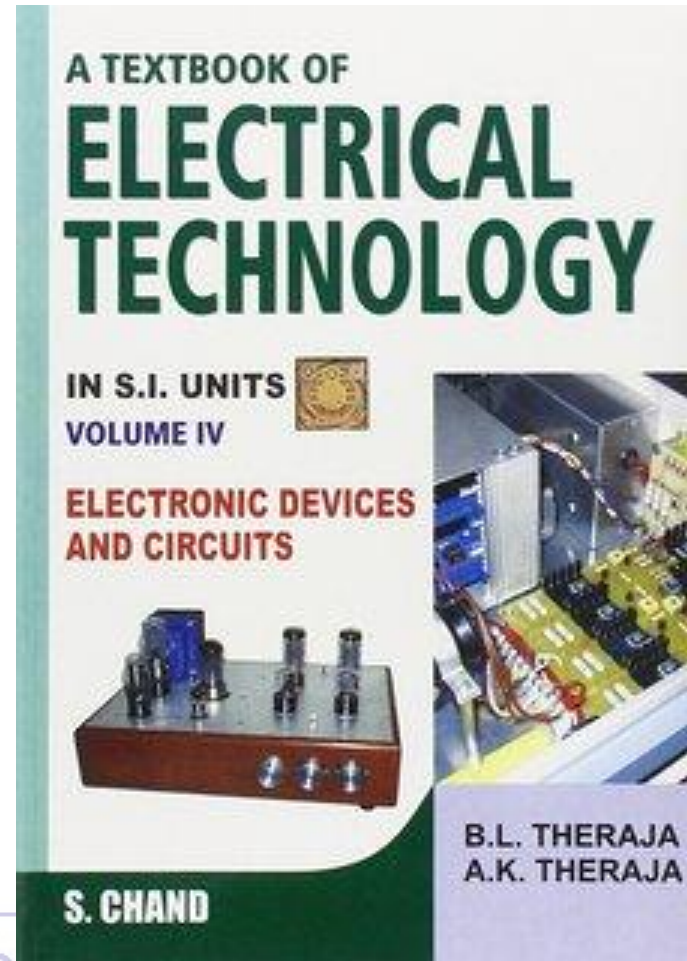- **A Textbook of
Electrical Technology**
VOLUME: IV
(Electronic Devices and Circuits)
- *B. L. Theraja*



sharafat.ali@ieee.org

Modern Electronics

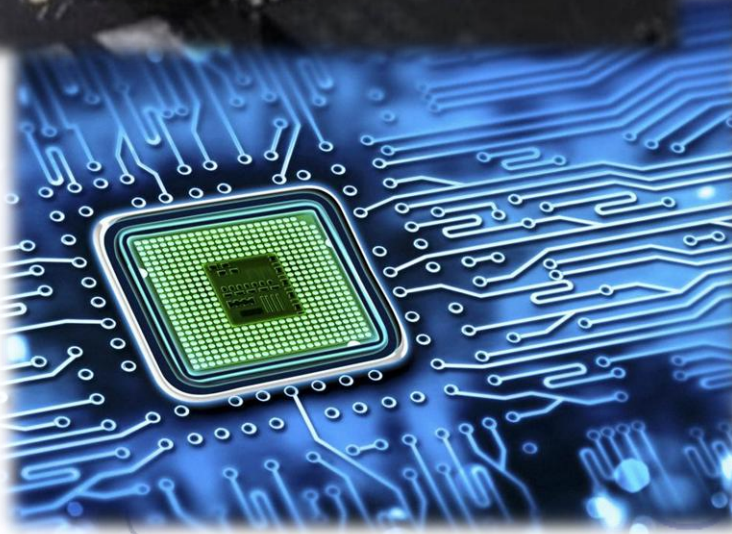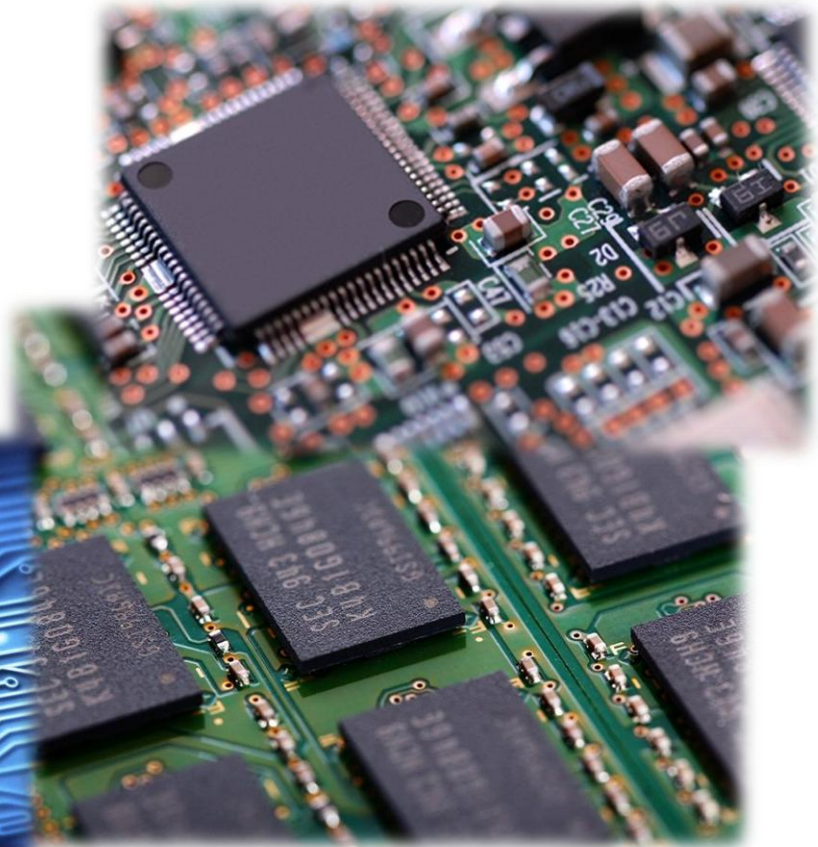


ieee.org

It is a solid substance that has a conductivity between that of an insulator and that of most metals. Such as: Silicon (Si)

sharafat.ali@ieee.org

Semiconductors

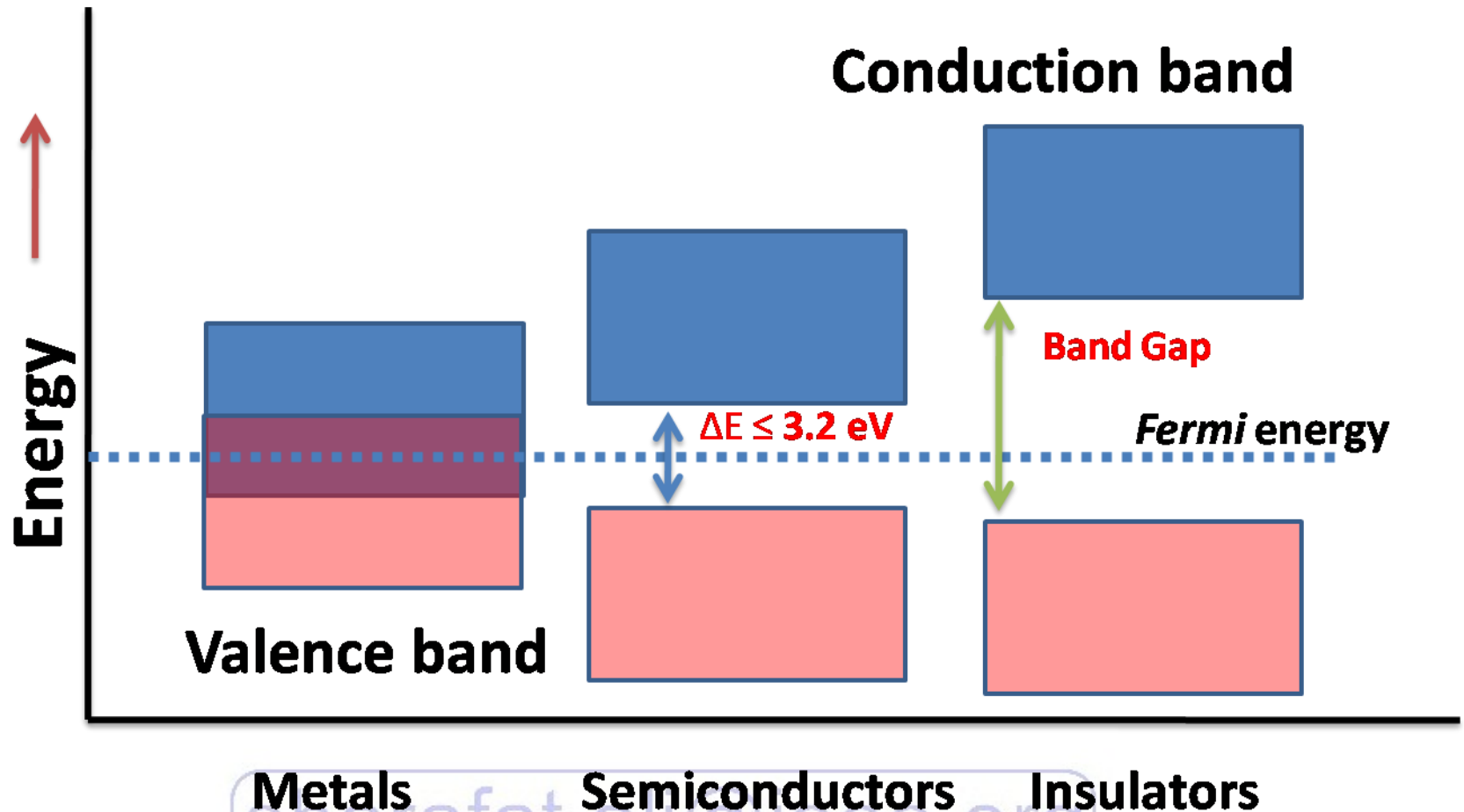

Metals

Semiconductors

Insulators

sharafat.ali@ieee.org


Semiconductors

Intrinsic Semiconductors	Extrinsic Semiconductors
Pure materials	Have impurities
Low conductivity	High Conductivity
Number of electrons = Number of holes	Number of electrons \neq Number of holes
Not used practically usually	Used practically
Fermi energy level lies in the middle of valance band & conduction band	Fermi energy level shifts towards the valance band or conduction band


sharafat.ali@ieee.org

Extrinsic Semiconductors

- **N type**

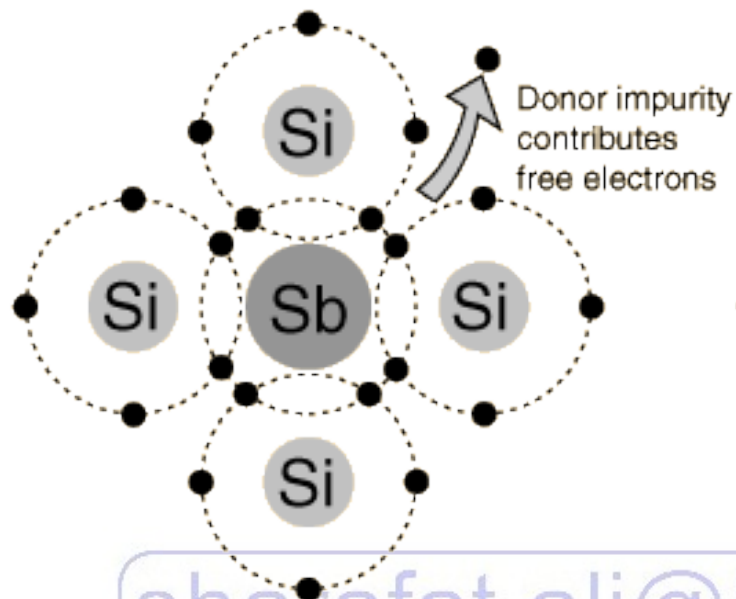


- **P type**

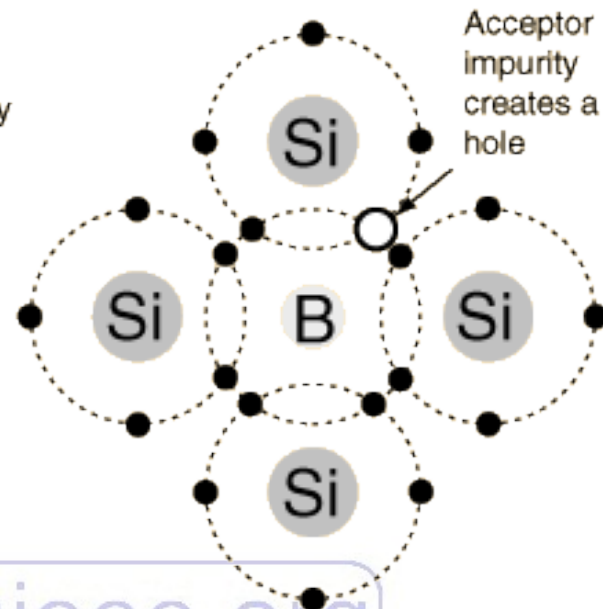

sharafat.ali@ieee.org


Majority & Minority Carriers

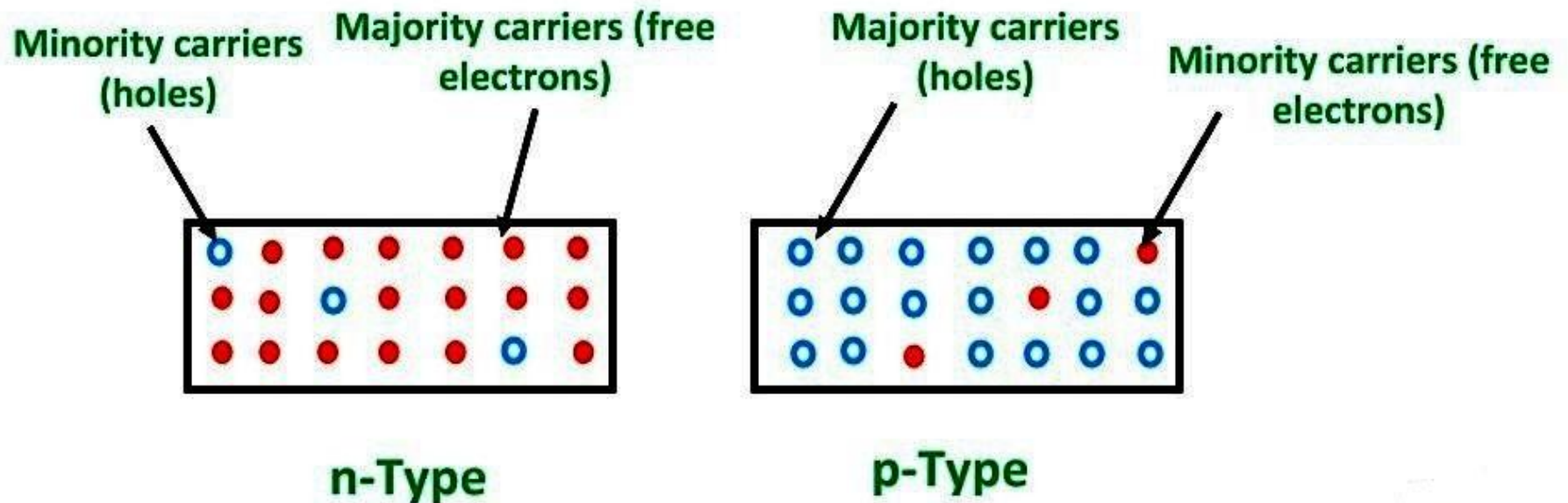


sharafat.ali@ieee.org

P-N Junction

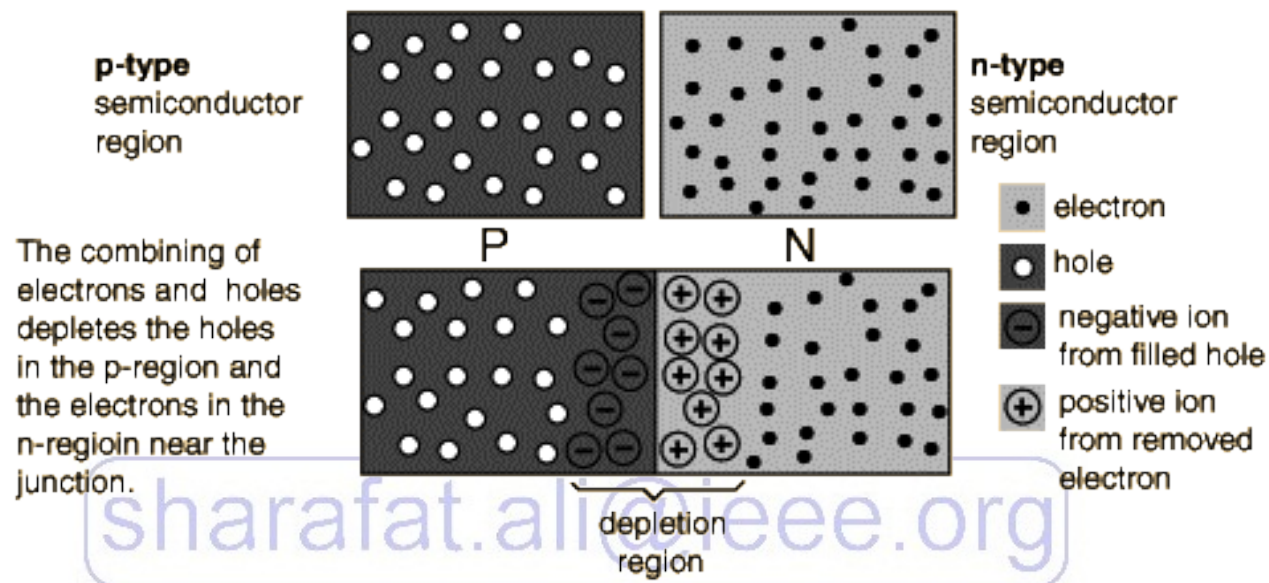When one side of an intrinsic semiconductor is doped with acceptor i.e, one side is made p-type by doping with n-type material, a *P-N junction* diode is formed. This is a two terminal device. The *P-N junctions* are formed by joining n-type and p-type semiconductor materials.




P-N Junction

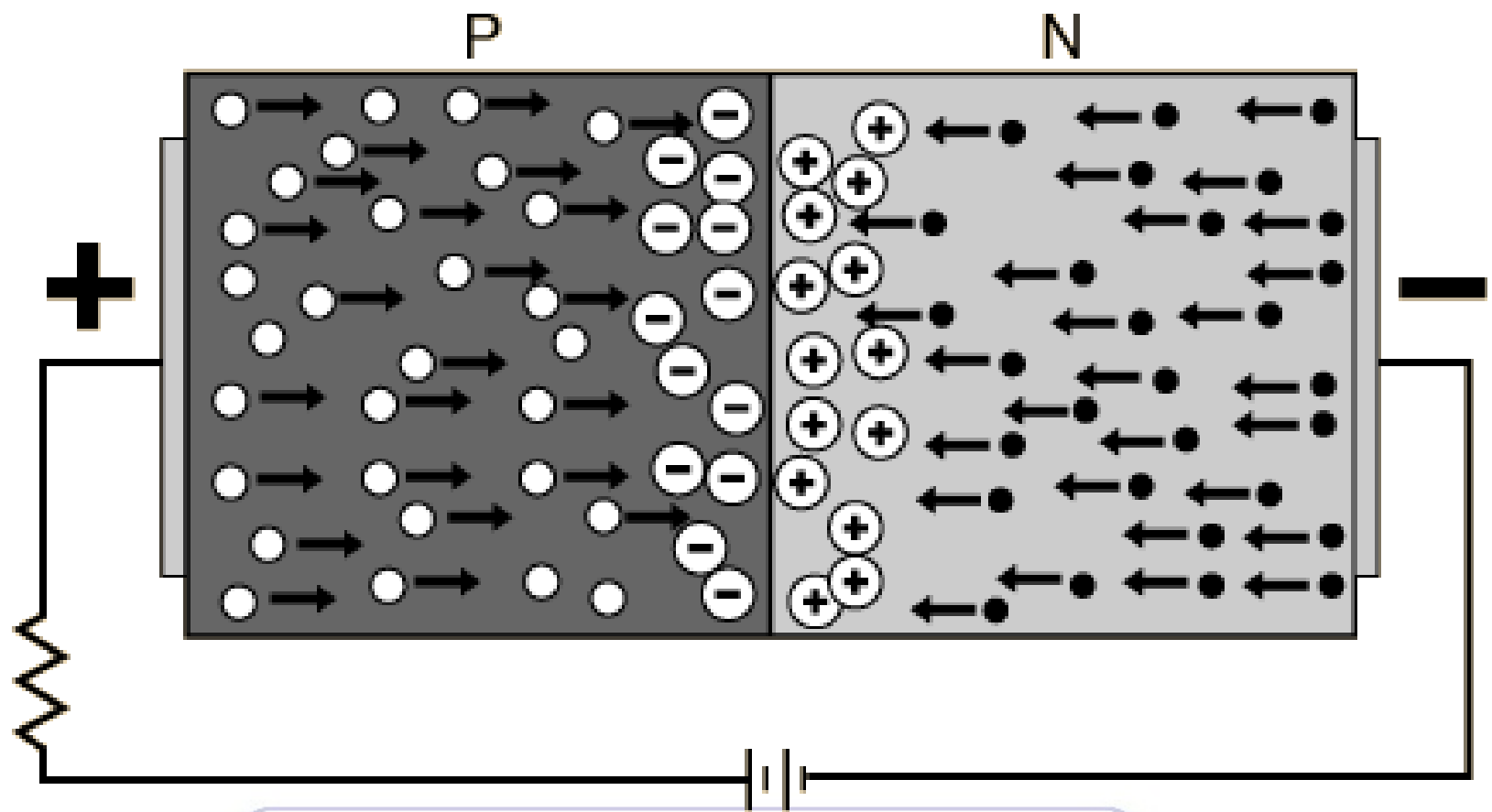

sharafat.ali@ieee.org


Depletion Region

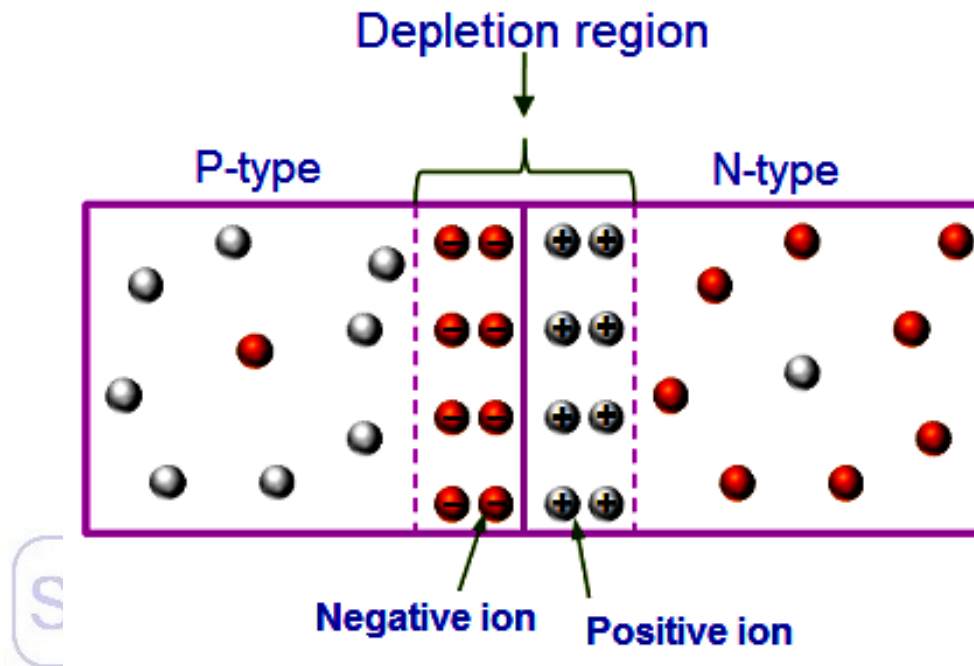Depletion region or depletion layer is a region in a P-N junction diode where no mobile charge carriers are present. Depletion layer acts like a barrier that opposes the flow of electrons from n-side and holes from p-side.




Depletion Region

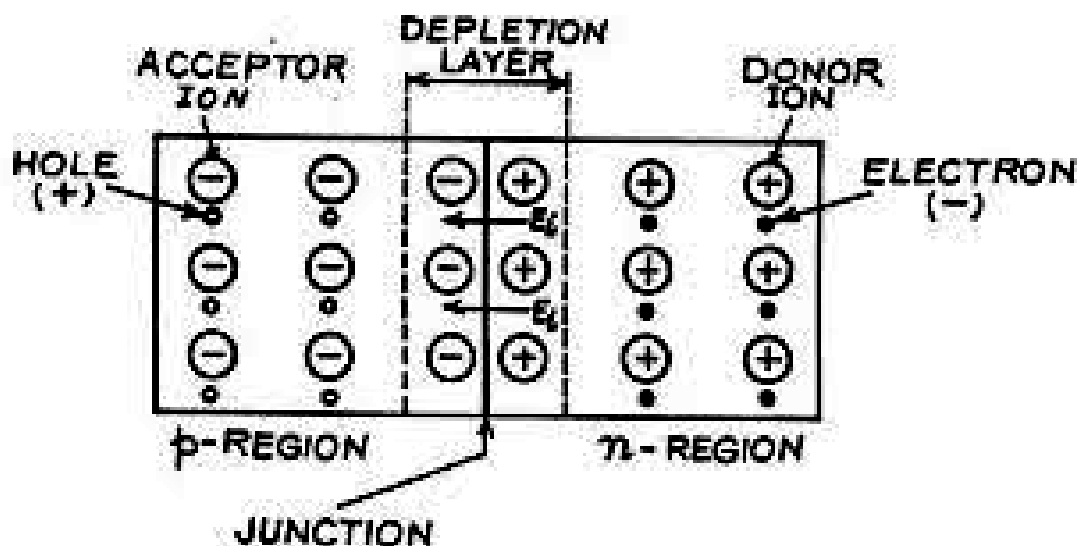The depletion region is also called as depletion zone, depletion layer, space charge region, or space charge layer. The depletion region acts like a wall between p-type and n-type semiconductor and prevents further flow of free electrons and holes.




Junction / Barrier Voltage (V_B)

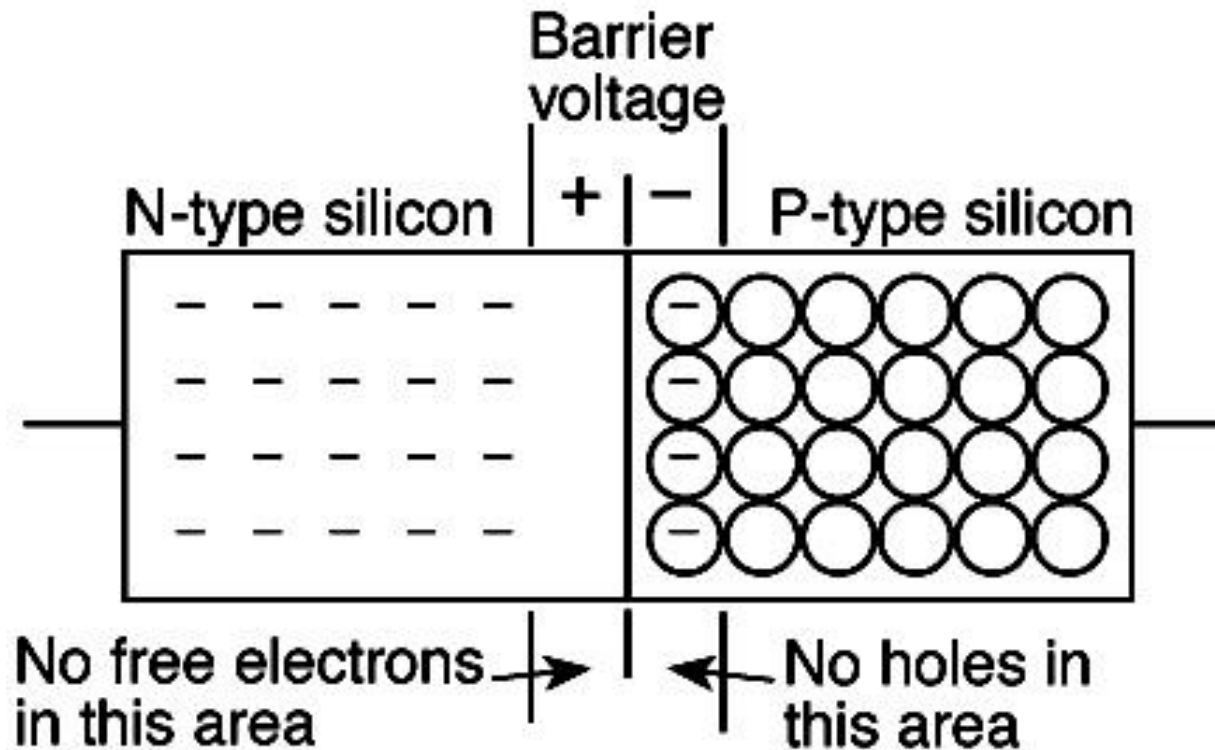The barrier voltage is the amount of electromotive force required to start current through the P-N junction.




Forward Bias in P-N Junction



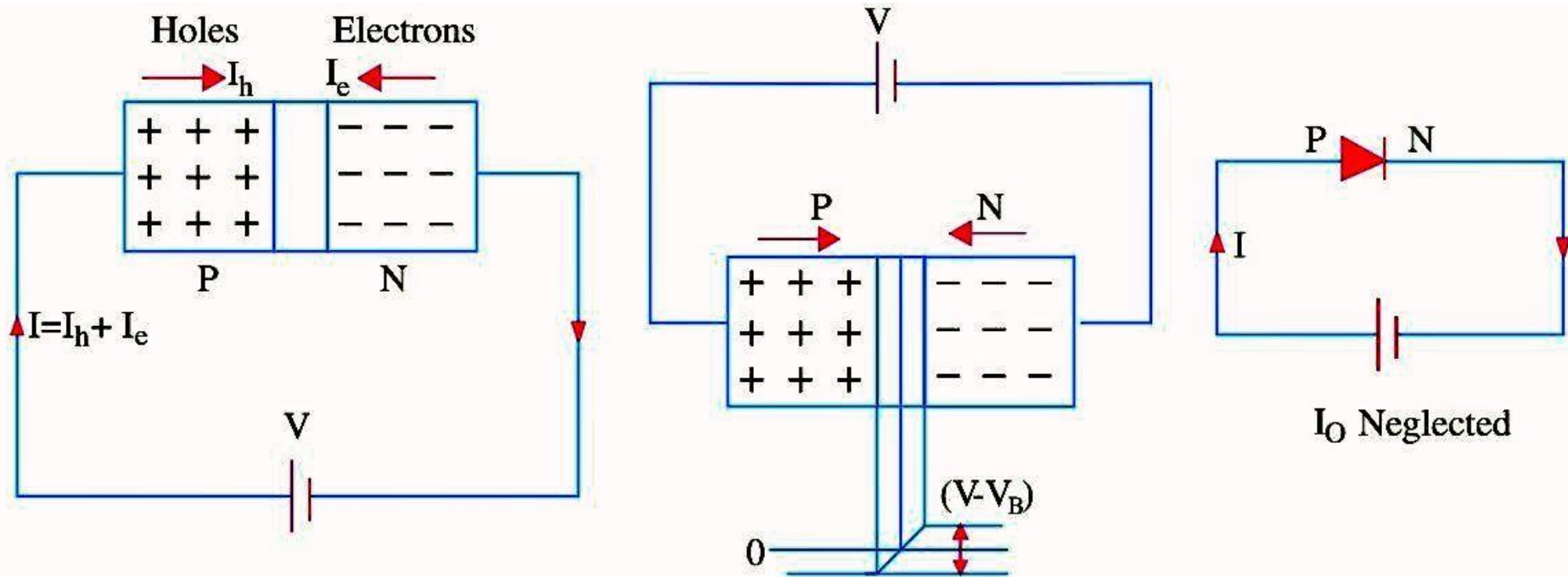


sharafat.ali@ieee.org

Forward V/I Characteristics

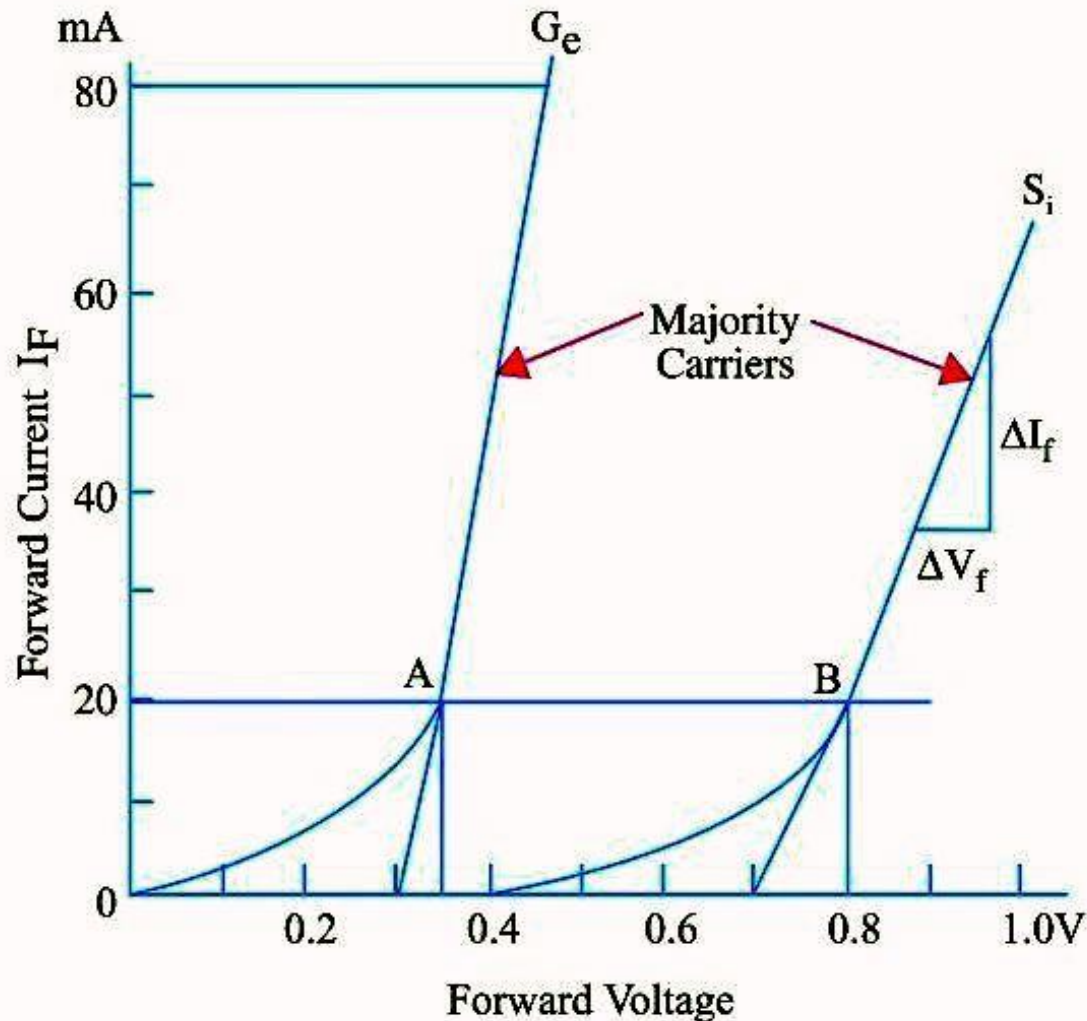


Reverse Bias in P-N Junction

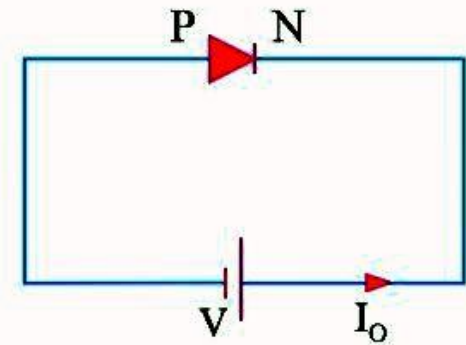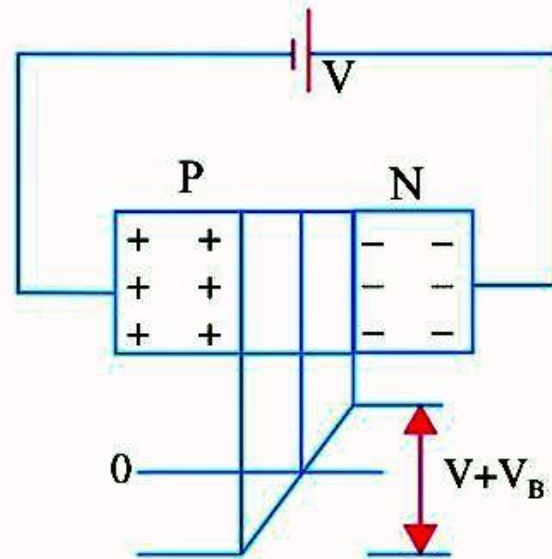
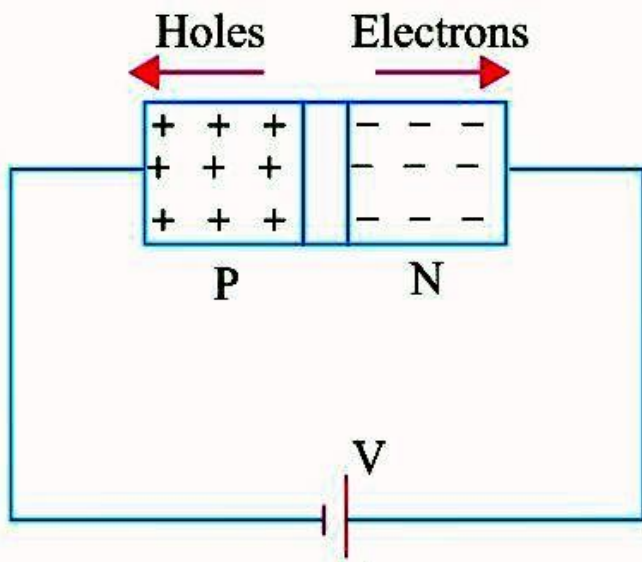


sharafat.ali@ieee.org

Reverse V/I Characteristics

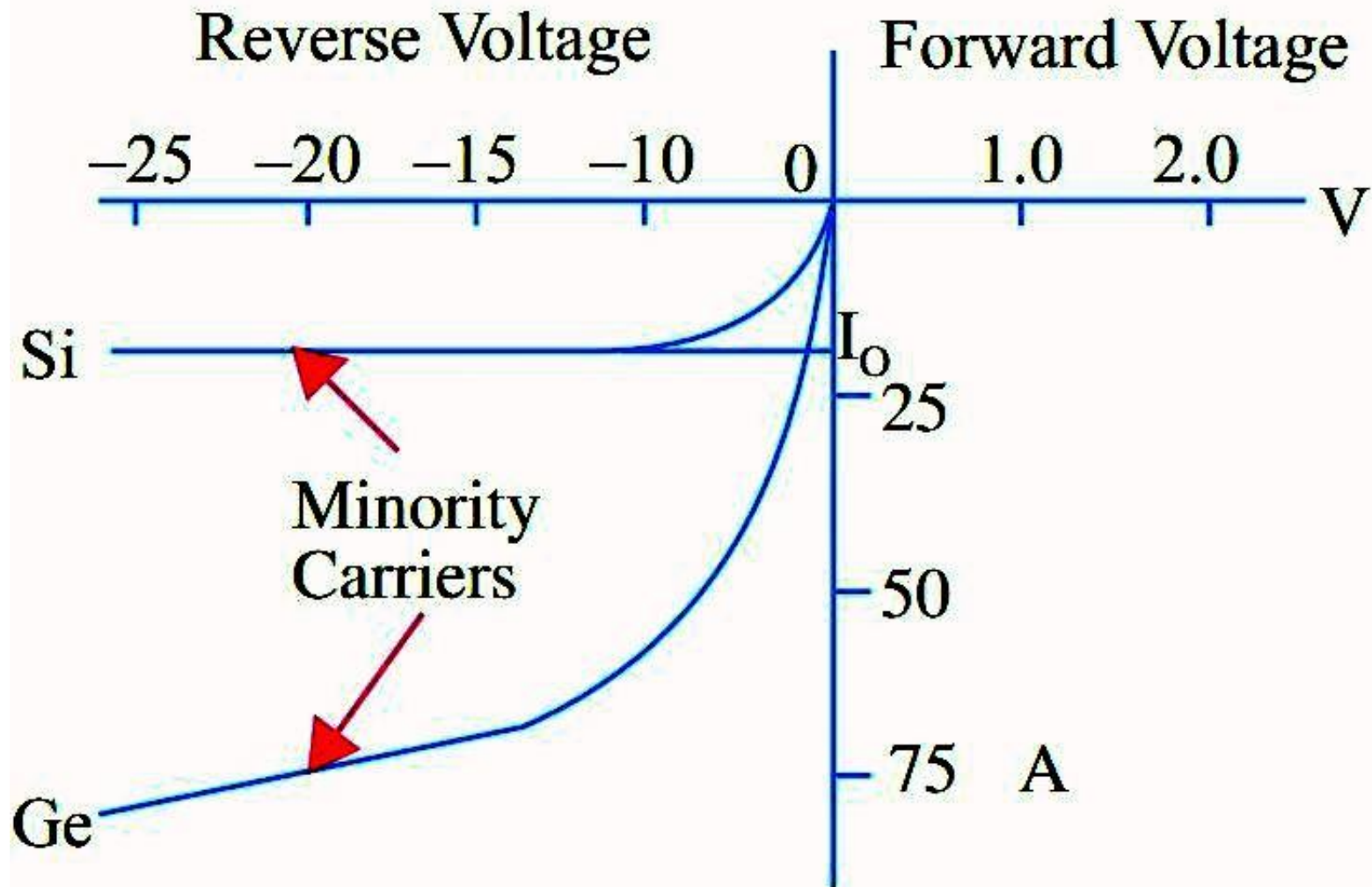

P-N Junction Diode

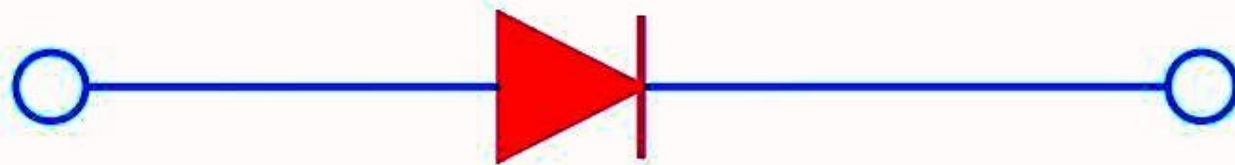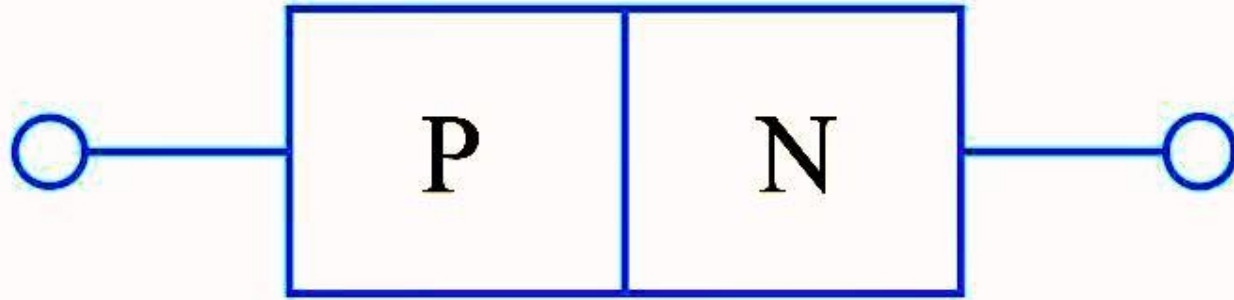


Anode

Cathode


sharatat.ali@ieee.org

P-N Junction Diode

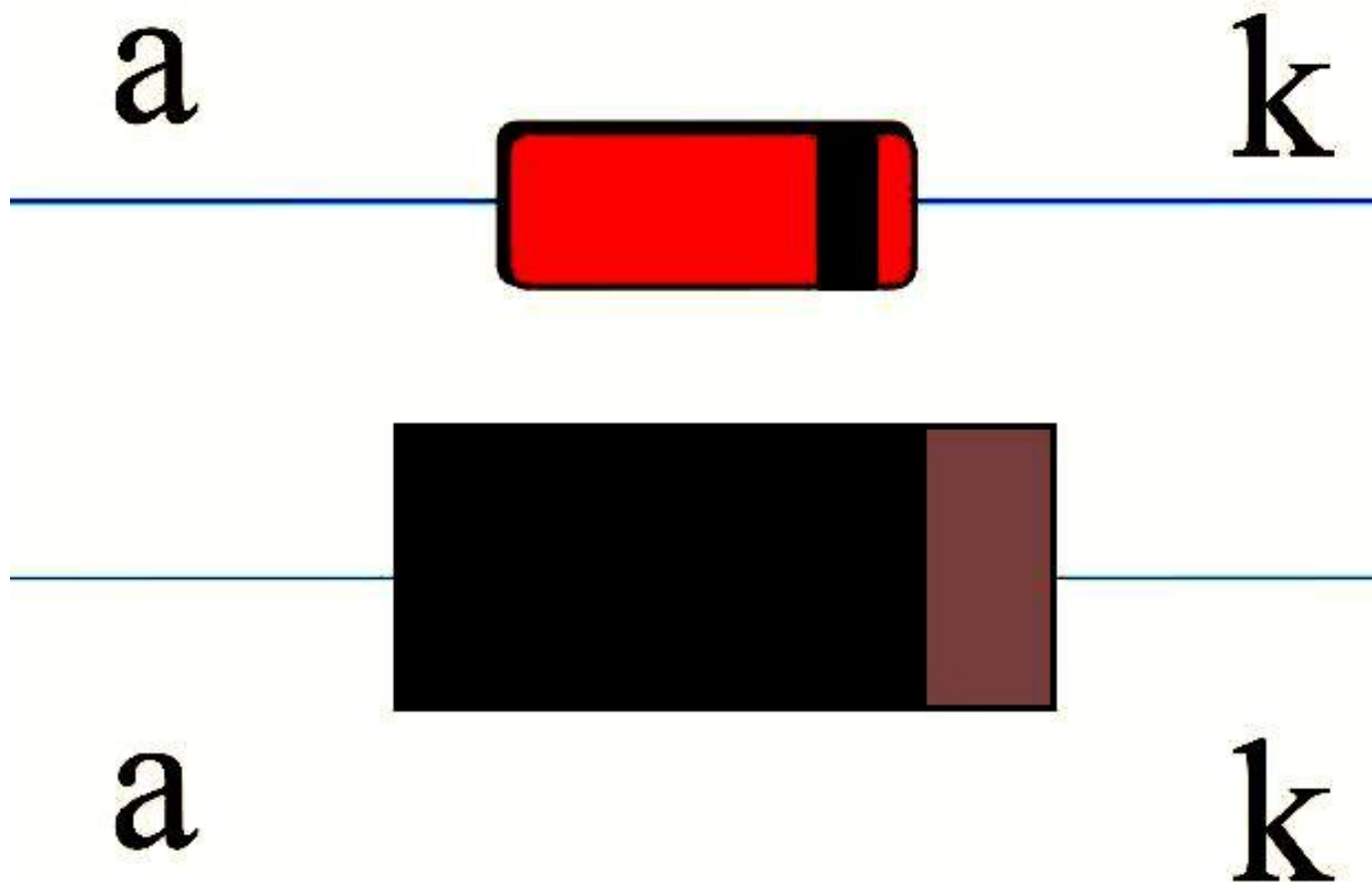

shafaral.al@ieee.org

P-N Junction Diode


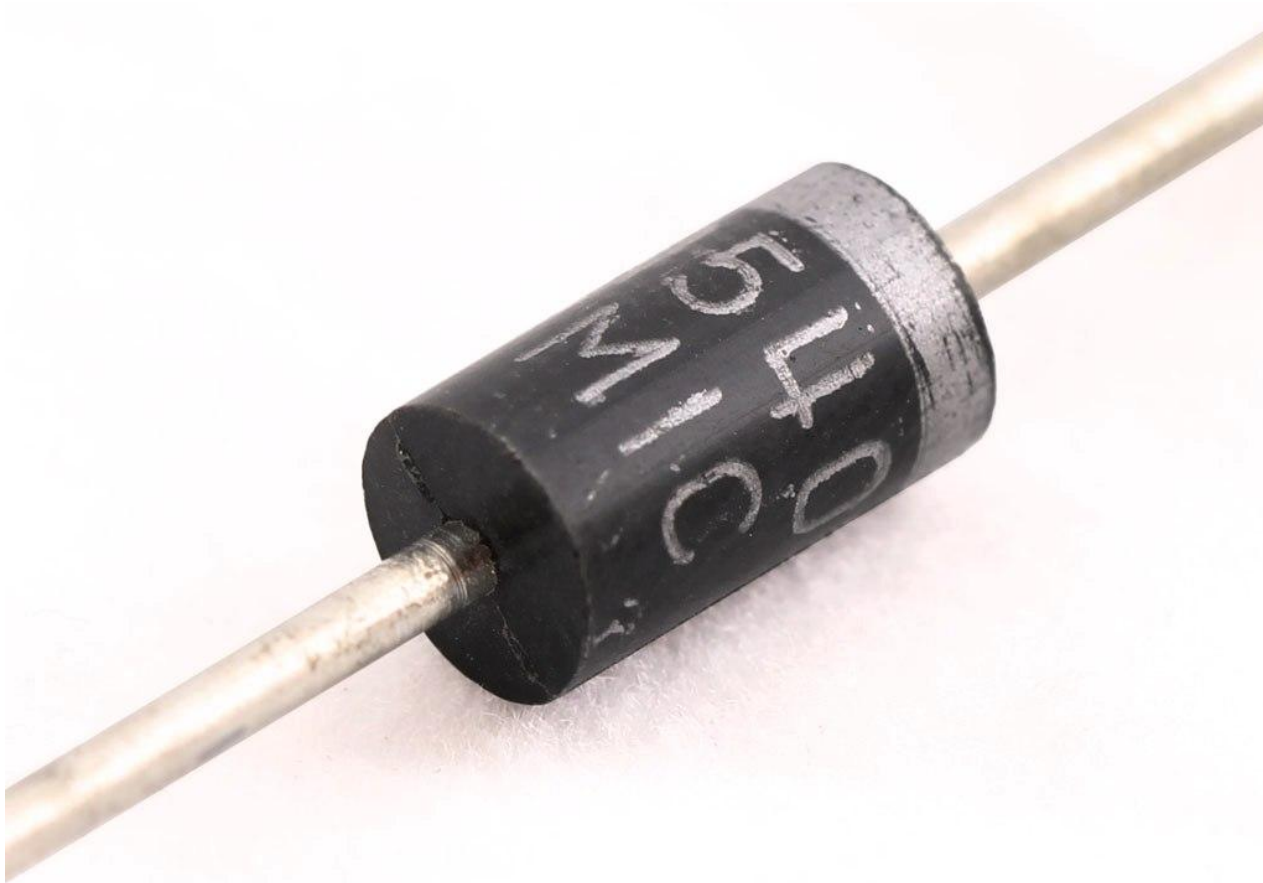


shaharad.ah@1000.org


Applications of P-N Junction Diode:

- As power or rectifier diodes. They convert ac current into dc current for dc power supplies of electronic circuits.
- As signal diodes in communication circuits for modulation and demodulation of small signals.
- As Zener diodes in voltage stabilizing circuits.
- As Varactor diodes—for use in voltage-controlled tuning circuits as may be found in radio and TV receivers.
- In logic circuits used in computers.

Forward & Reverse Biased Diode

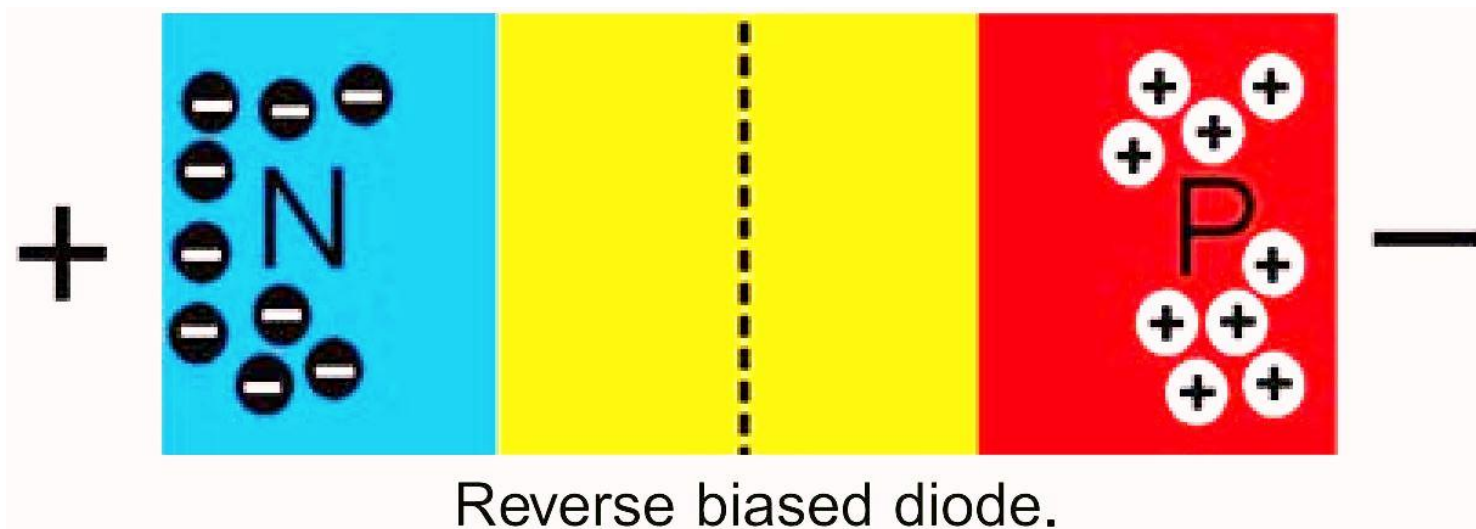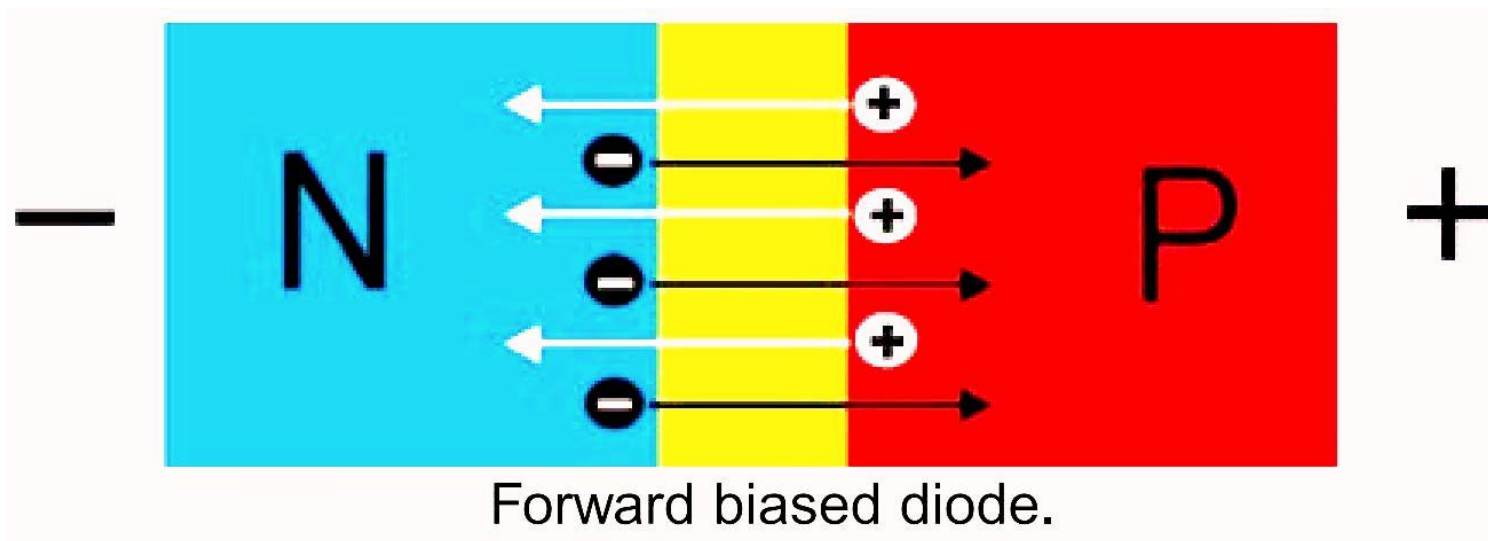


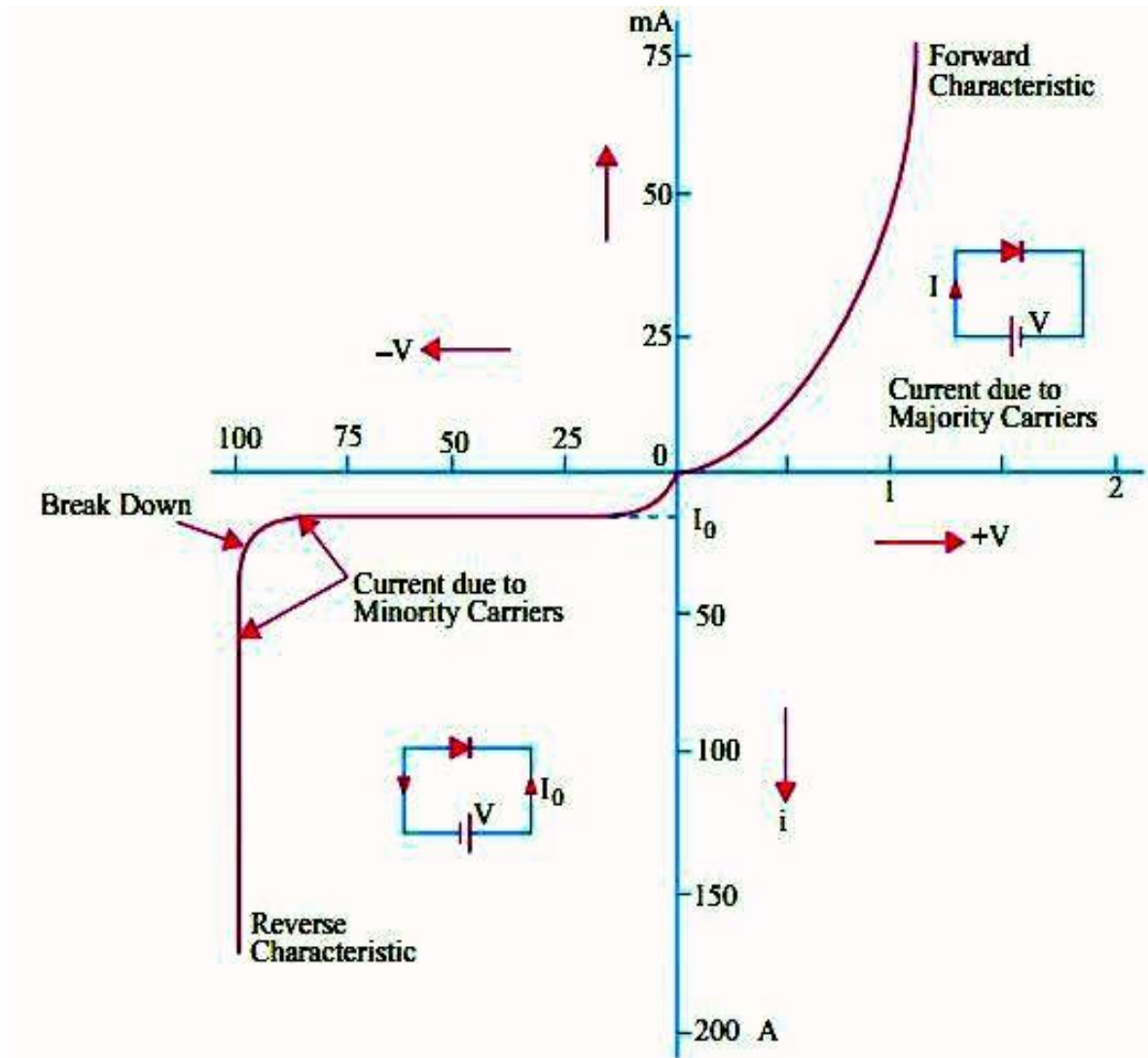V/I Characteristic or Static Characteristic



Practice Math Problem

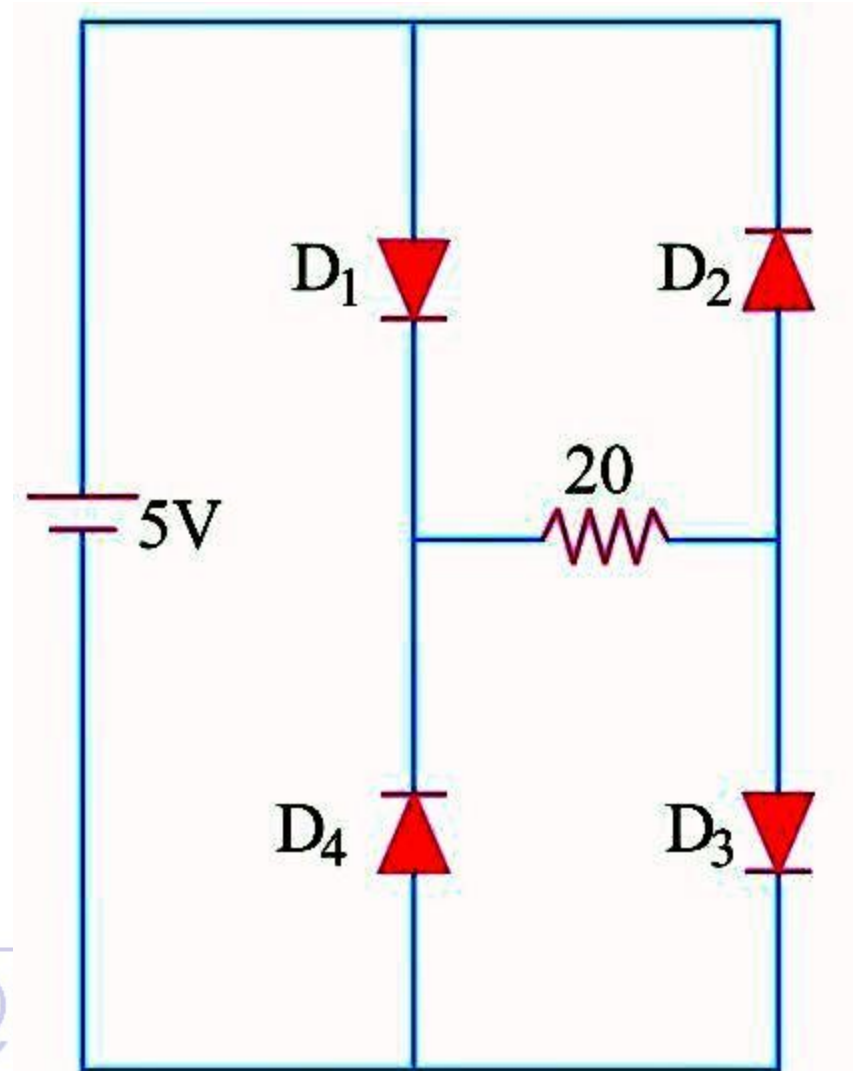Find the current through the $20\ \Omega$ resistor shown in Fig. 52.6 (a). Each silicon diode has a barrier potential of 0.7 V and a dynamic resistance of $2\ \Omega$. Use the diode equivalent circuit technique.



sharafat.ali@


Practice Math Problem

D_1 and D_3 are forward-biased by 5 V battery whereas D_2 and D_4 are reverse-biased

$$V_{\text{net}} = 5 - 0.7 - 0.7 = 3.6 \text{ V}$$

$$R_T = 2 + 20 + 2 = 24 \Omega$$

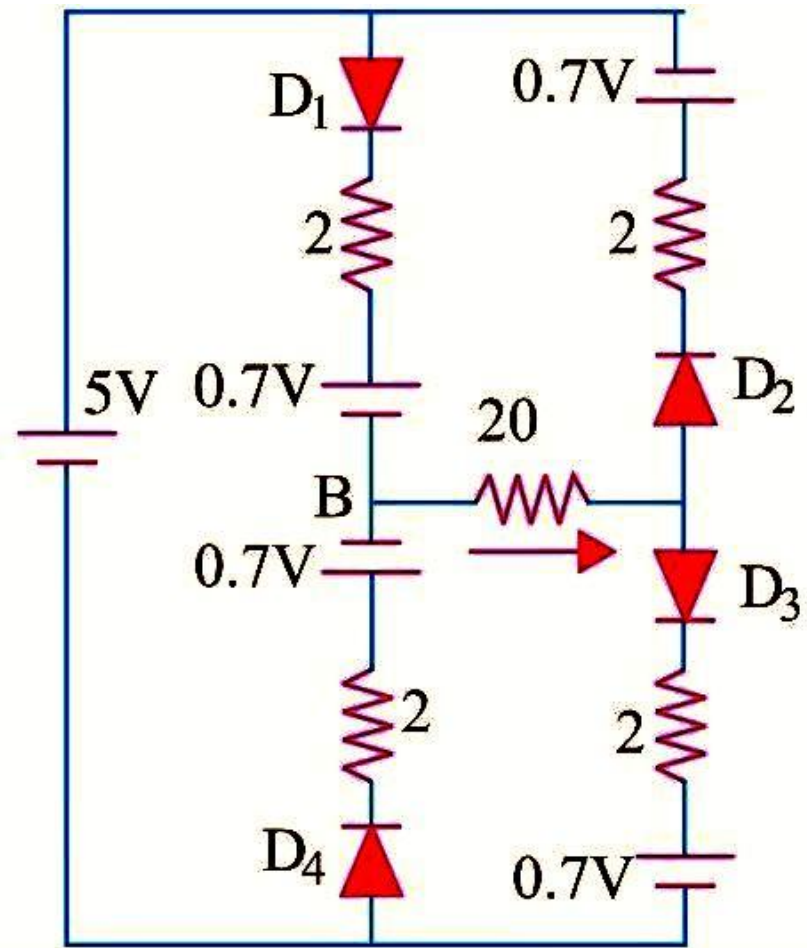
$$I = V_{\text{net}}/R_T = 3.6/24 = 0.15 \text{ A}$$




sharafat.ali@iitb.ac.in

Zener Diode

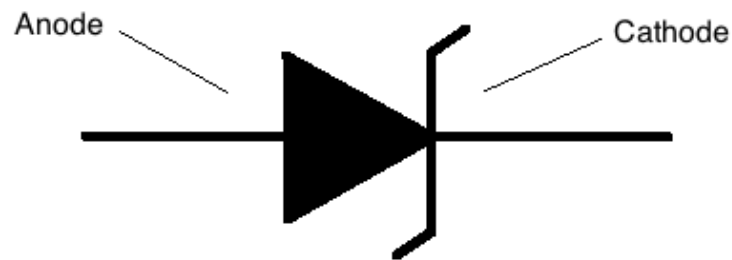A semiconductor diode in which at a critical reverse voltage a large reverse current can flow.




V/I Characteristic of Zener Diode

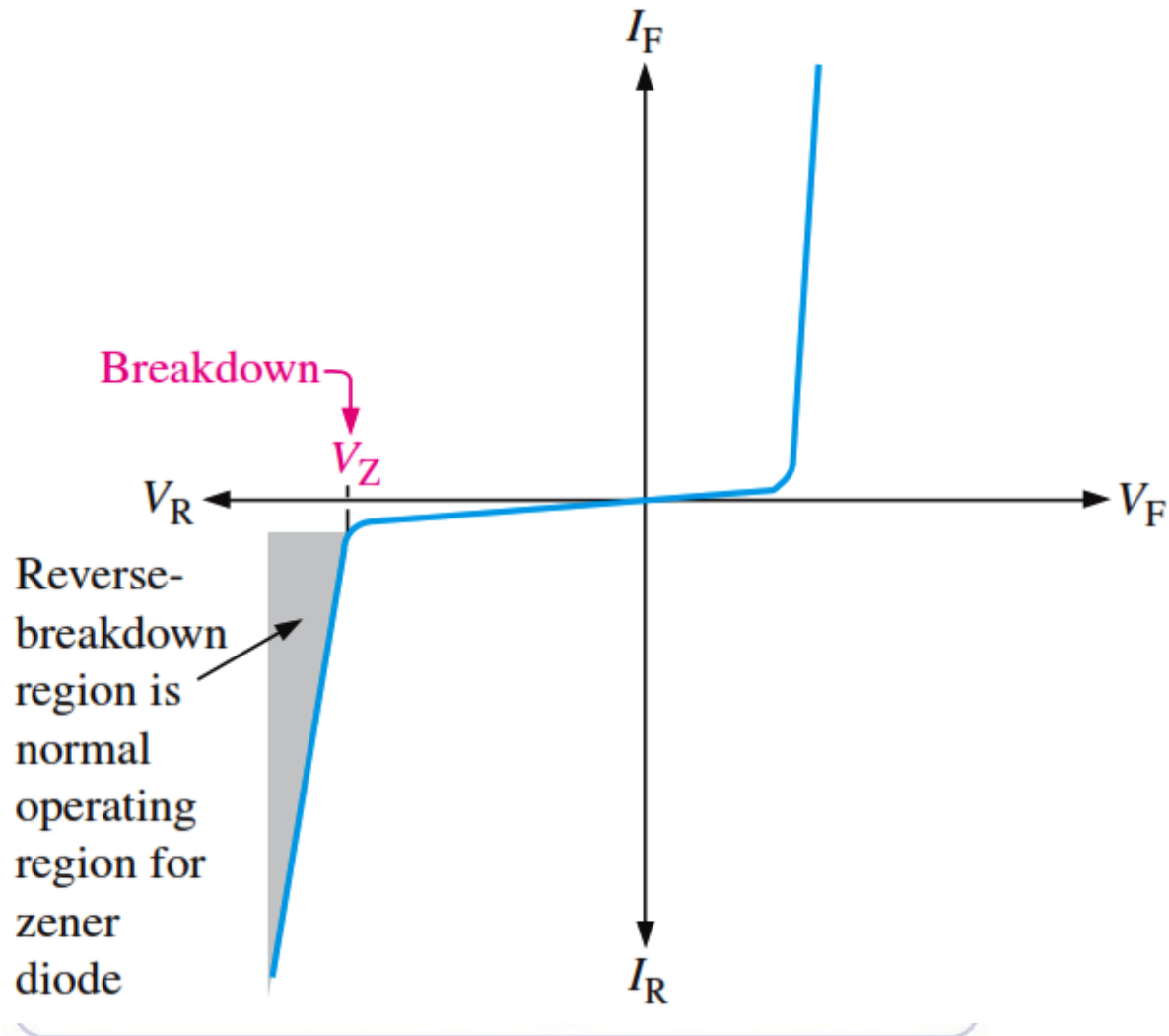


Peak Inverse Voltage (PIV) / Peak Reverse Voltage (PRV):

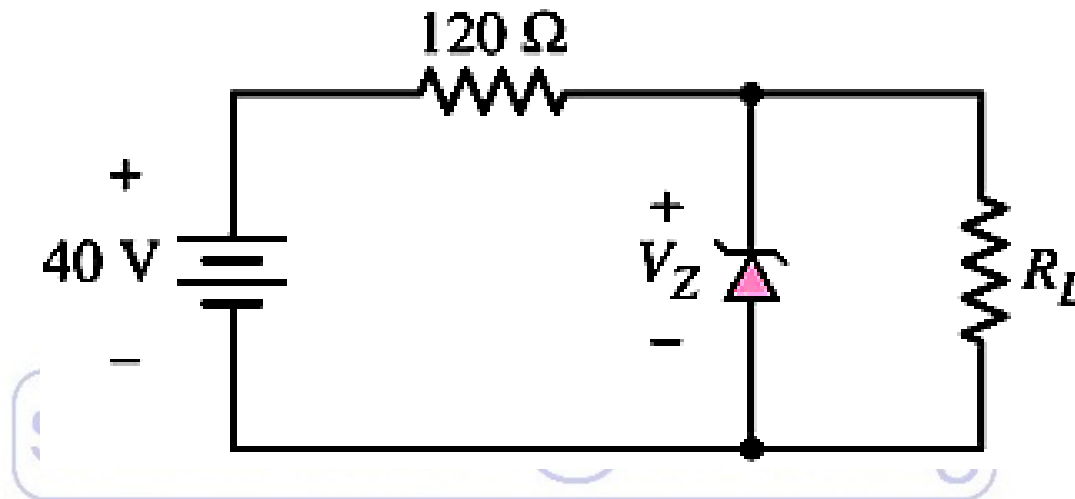The maximum reverse biased potential that can be applied before entering the Zener region is called Peak Inverse Voltage (PIV) / Peak Reverse Voltage (PRV).



Voltage Regulation using Zener Diode

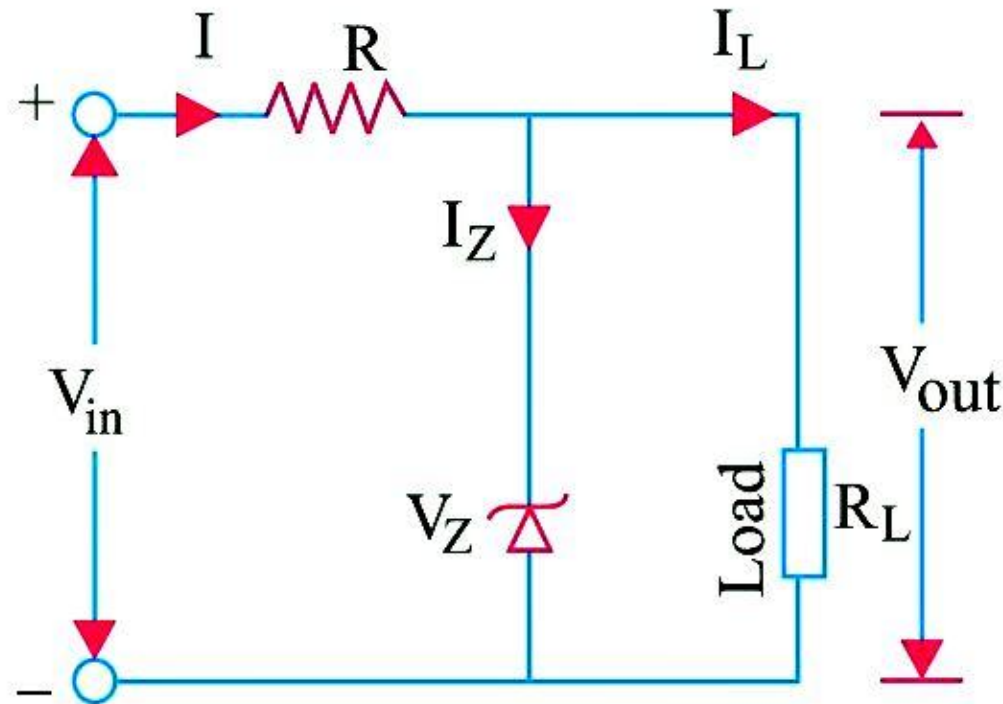


$$R = \frac{V_{in} - V_{out}}{I_{Zmax}}$$

shara


org

Ideal Diode

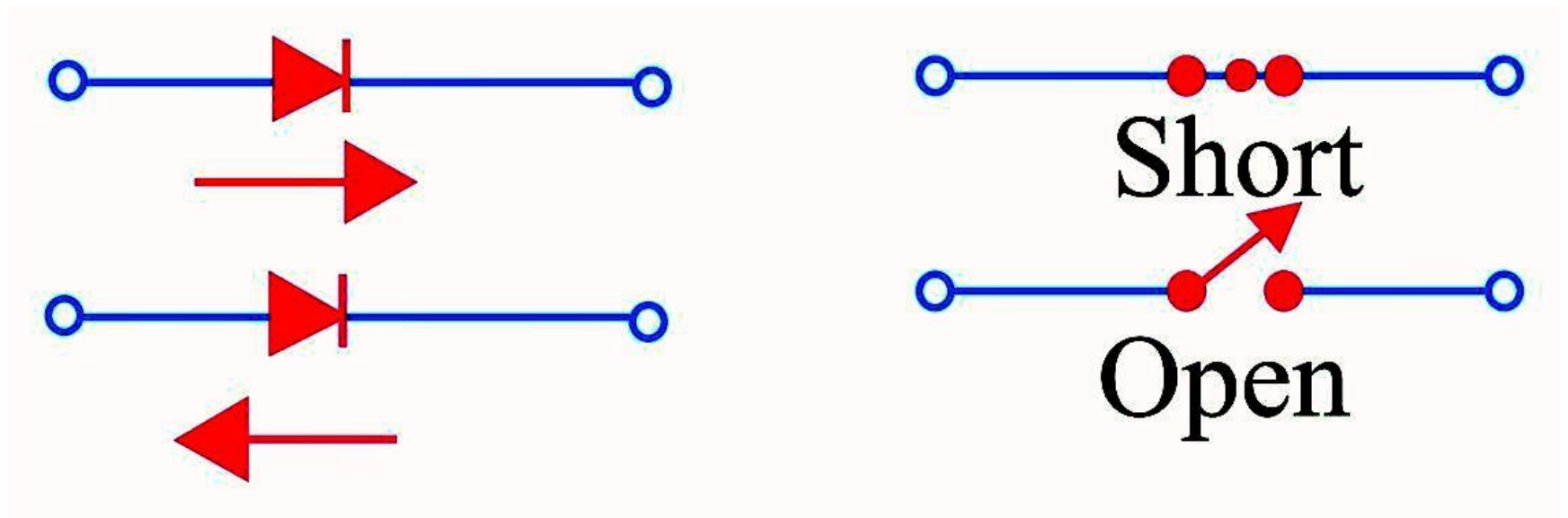


sharafat.ali@ieee.org

Rectifier

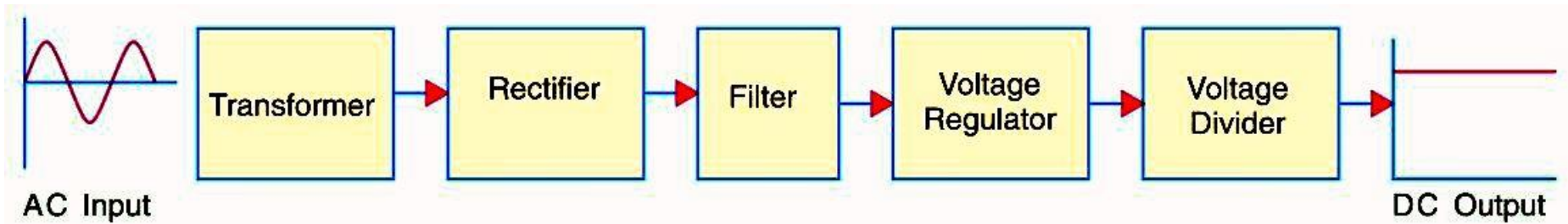



sharafat.ali@ieee.org

Real Diode

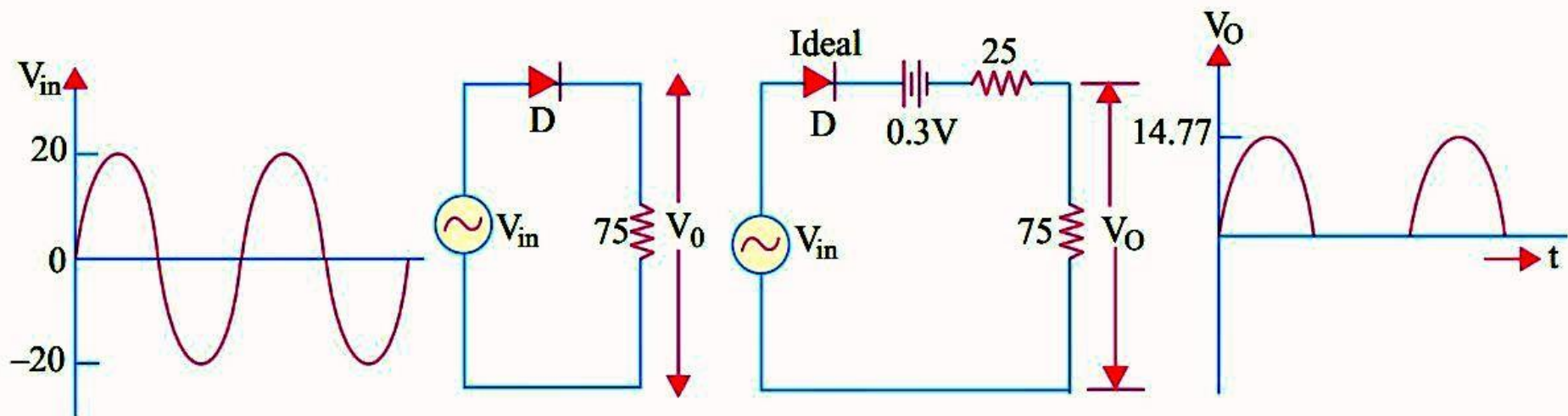

sharafat.ali@ieee.org

Single Phase Half Wave Rectifier

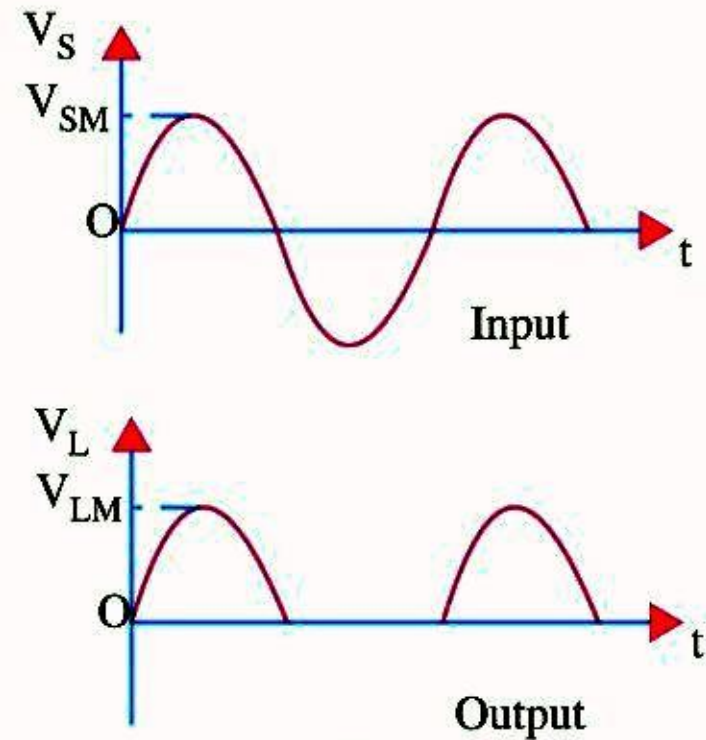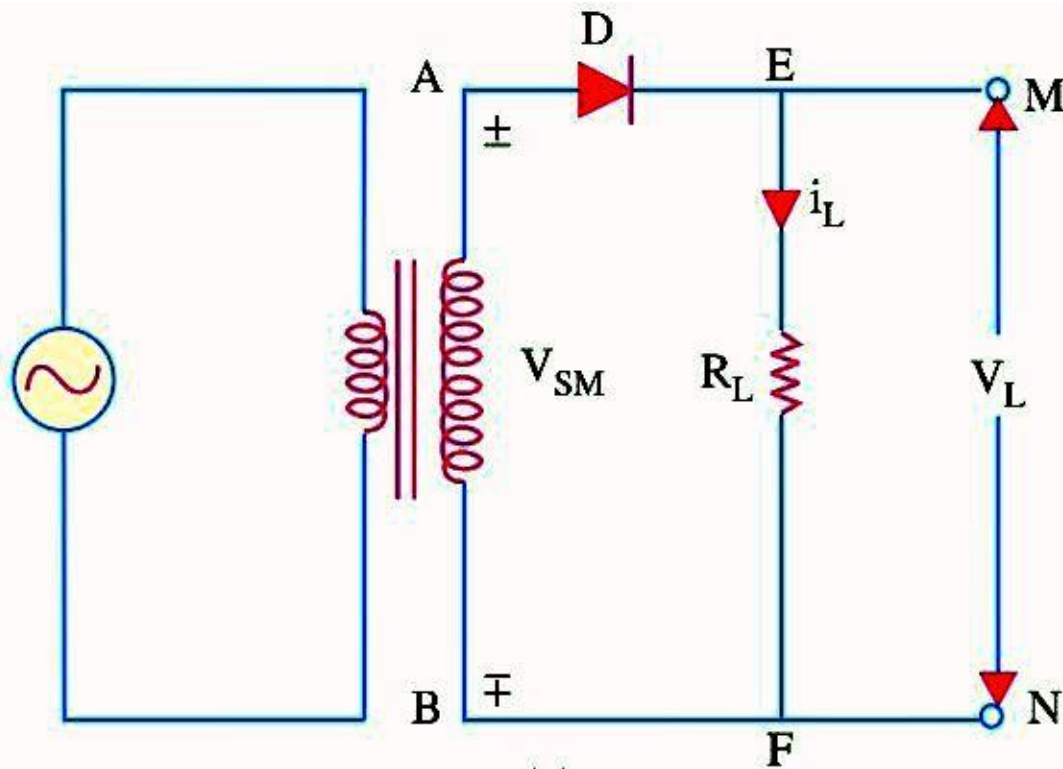

sharafat.ali@ieee.org

Single Phase Half Wave Rectifier

- **Average and RMS Values**

V_{sm} = maximum value of transformer secondary voltage

V_s = rms value of secondary voltage

V_{LM} = maximum value of load voltage

= V_{sm} - diode drop - secondary resistance drop

V_L = rms value of load voltage

I_L = rms value of load current

$V_{L(dc)}$ = average value of load voltage

$I_{L(dc)}$ = average value of load current

I_{LM} = maximum value of load current

R_L = load resistance

R_s = transformer secondary resistance

r_d = diode forward resistance

$R_0 = R_s + r_d$

sharafat.ali@ieee.org

Single Phase Half Wave Rectifier

- **Average and RMS Values**

$$I_{LM} = (V_{sm} - V_B) / (R_S + r_d + R_L) = (V_{sm} - V_B) / (R_0 + R_L)$$

$$V_{LM} = I_{LM} \cdot R_L$$

$$V_{L(dc)} = V_{LM} / \pi = 0.318 V_{LM}$$

$$I_{L(dc)} = I_{LM} / \pi = 0.318 I_{LM}$$

$$I_L = 0.5 I_{LM} = 0.5 V_{LM} / R_L$$

sharafat.ali@ieee.org

Single Phase Half Wave Rectifier

- **Efficiency**

$\eta = P_{dc}/P_{in}$ = power in the load/input power

$$P_{dc} = I_{L(dc)}^2 R_L = (I_{LM}/\pi)^2 \cdot R_L = I_{LM}^2 \cdot R_L / \pi^2$$

$$P_{in} = I_L^2 (R_L + R_0) = (I_{LM}/2)^2 (R_L + R_0) = I_{LM}^2 (R_L + R_0)/4$$

$$\eta = P_{dc}/P_{in} = (4/\pi^2) R_L / (R_L + R_0) = 0.406 / (1 + R_0/R_L)$$

(I_L = rms value of load current)

If R_0 is neglected $\eta = 40.6\%$. Obviously, it is the maximum possible efficiency of a half-wave rectifier.

sharafat.ali@ieee.org

Single Phase Half Wave Rectifier

- **Frequency Components of H.W. Rectified Voltage and Current**

The rms (or effective) value of the total load current is given by:

$$I_L = \sqrt{I_{L(dc)}^2 + I_{L(ac)}^2} = \sqrt{I_{L(dc)}^2 + (I_{L1}^2 + I_{L2}^2 + I_{L3}^2 + \dots)}$$

The rms (or effective) value of entire load voltage is given by:

$$V = \sqrt{V_{L(dc)}^2 + V_{L(ac)}^2} = \sqrt{V_{L(dc)}^2 + V_{L1}^2 + V_{L2}^2 + V_{L3}^2 + \dots}$$

Single Phase Half Wave Rectifier

- **Ripple Factor**

γ = rms value of ac component/dc value of load voltage =

$$V_{L(ac)}/V_{L(dc)} = V_{r(rms)}/V_{L(dc)}$$

γ = rms value of ac component/dc value of load current

$$= I_{L(ac)}/I_{L(dc)}$$

We know, $I_{L(ac)} = \sqrt{I_L^2 - I_{L(dc)}^2}$

$$\gamma = I_{L(ac)}/I_{L(dc)} = \sqrt{I_L^2 - I_{L(dc)}^2}/I_{L(dc)} = \sqrt{(I_L/I_{L(dc)})^2 - 1}$$

Again, $I_L/I_{L(dc)} = \text{form factor } K_f$

Thus, $\gamma = \sqrt{K_f^2 - 1}$ (In this case of Half-Wave rectifies with resistive load but no filter $K_f = \pi/2 = 1.57$)

$$\gamma = \sqrt{1.57^2 - 1} = 1.21$$

sharafat.ali@ieee.org

Single Phase Half Wave Rectifier

- **Peak Inverse Voltage (PIV)**

It is the maximum voltage that occurs across the rectifying diode *in the reverse direction*.

$$PIV = V_{SM}$$

sharafat.ali@ieee.org

Single Phase Half Wave Rectifier

- **Transformer Utilization Factor (TUF)**

TUF = dc power delivered to the load /ac rating of
transformer secondary

$$= P_{dc}/P_{ac.rated}$$

$$= P_{dc}/P_{in.rated}$$

sharafat.ali@ieee.org

Single Phase Half Wave Rectifier

- Transformer Utilization Factor (TUF)

$$\begin{aligned}\text{Now, } P_{dc} &= V_{L(dc)} \cdot I_{L(dc)} \\ &= V_{LM}/\pi \cdot V_{LM}/R_L \\ &= V_{LM}^2 / \pi R_L \\ &= V_{sm}^2 / \pi R_L \quad ; \text{ if drop over } R_0 \text{ is neglected}\end{aligned}$$

$$\begin{aligned}\text{Again, } P_{ac.rated} &= V_{sm}/\sqrt{2} \cdot I_{LM}/2 \\ &= V_{sm}/\sqrt{2} \cdot V_{LM}/2R_L \\ &= V_{sm}/2\sqrt{2}R_L\end{aligned}$$

$$\text{Thus, TUF} = (V_{sm}^2 / \pi R_L) / (V_{sm}^2 / 2\sqrt{2}R_L) = 2\sqrt{2}/\pi = 0.287$$

Practice Problem for HW Rectifier

A half-wave rectifier using silicon diode has a secondary emf of 14.14 V (rms) with a resistance of $0.2\ \Omega$. The diode has a forward resistance of $0.05\ \Omega$ and a threshold voltage of 0.7 V. If load resistance is $10\ \Omega$, determine:

- (i) dc load current
- (ii) dc load voltage
- (iii) voltage regulation
- (iv) efficiency

sharafat.ali@ieee.org

Practice Problem for HW Rectifier

Solution.

$$V_{sm} = \sqrt{2} \times 14.14 = 20 \text{ V}, R_0 = 0.2 + 0.05 = 0.25 \Omega$$

$$(i) \quad I_{LM} = \frac{V_{sm} - V_B}{R_0 + R_L} = \frac{20 - 0.7}{10.25} = 1.88 \text{ A}; I_{L(dc)} = \frac{I_{LM}}{\pi} = \frac{1.88}{\pi} = \mathbf{0.6 \text{ A}}$$



$$(ii) \quad V_{L(dc)} = I_{L(dc)} \cdot R_L = 0.6 \times 10 = \mathbf{6 \text{ V}}$$

$$(iii) \quad V_R = R_0/R_L = 0.25/10 = 0.025 \quad \text{or} \quad \mathbf{2.5\%}$$

$$(iv) \quad \eta = \frac{40.6}{1 + 0.25/10} = \mathbf{39.6\%}$$




sharafat.ali@ieee.org

Single Phase Full Wave Rectifier

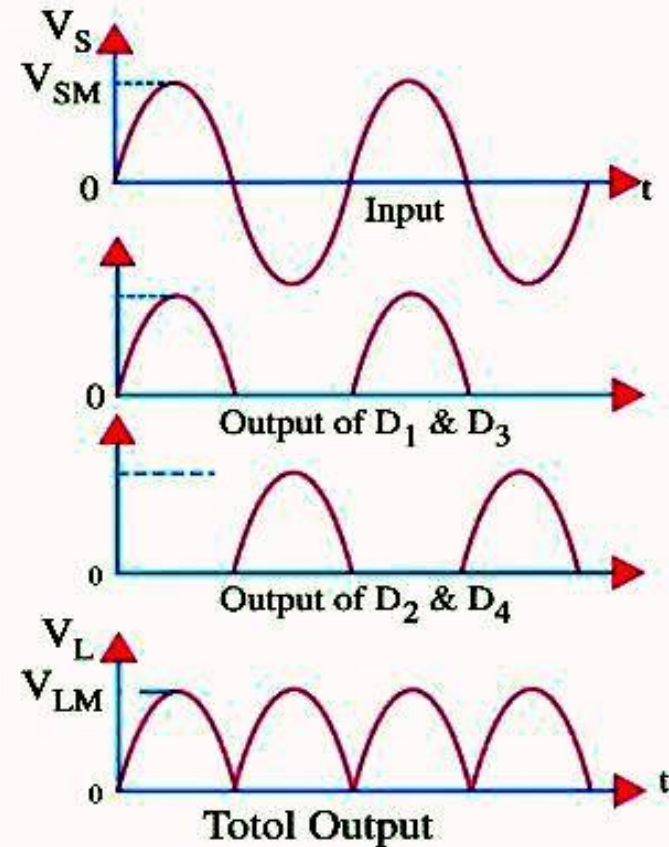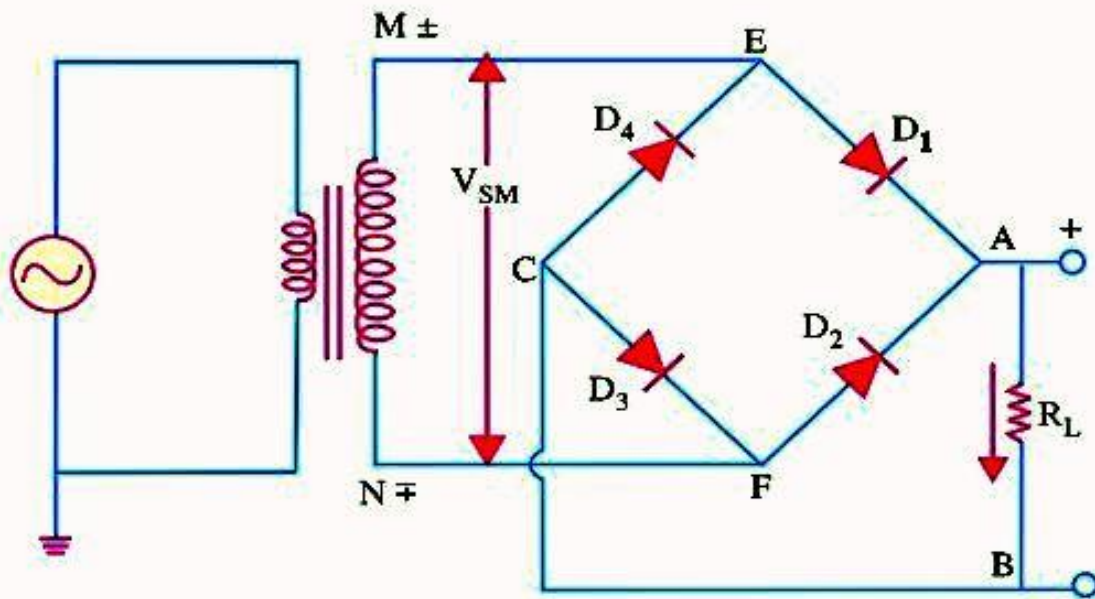

sharafat.ali@ieee.org

Single Phase Full Wave Rectifier

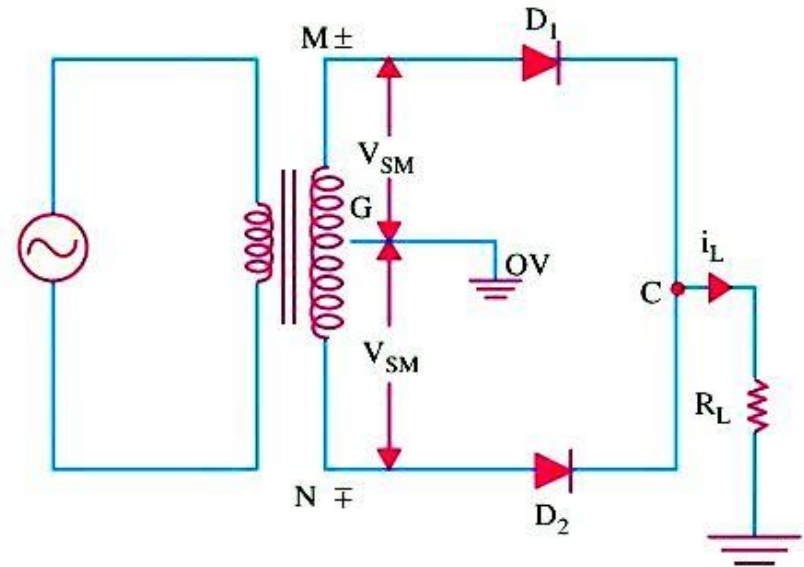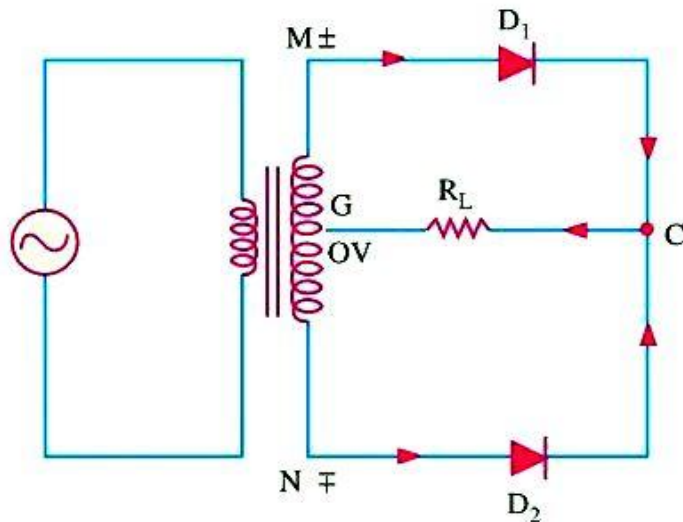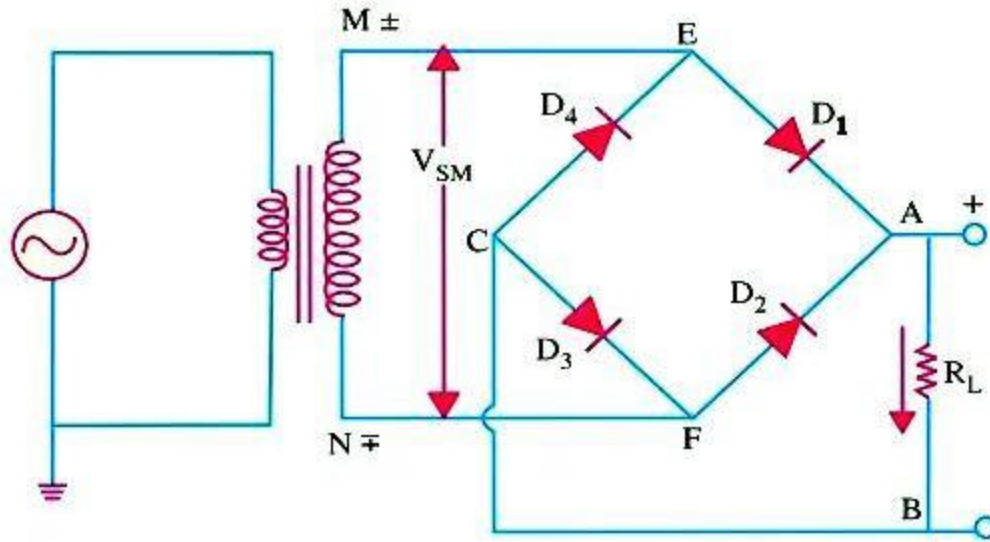

Centre-tapped Full-wave Rectifier

Single Phase Full Wave Rectifier

- Average and RMS Values**

$$\begin{aligned}V_L &= V_{LM}/\sqrt{2} = 0.707 V_{LM}; V_{L(dc)} = 2 V_{LM}/\pi = 0.636 V \\V_{L(ac)} &= \text{rms value of ac components in the output voltage} \\&= \sqrt{V_L^2 - V_{L(dc)}^2} \\I_{LM} &= \frac{V_{LM}}{R_L}; I_L = \frac{I_{LM}}{\sqrt{2}} = 0.707 I_{LM} \\I_{L(dc)} &= \frac{2 I_{LM}}{\pi} = 0.636 I_{LM}; I_{L(ac)} = \sqrt{I_L^2 - I_{L(dc)}^2}\end{aligned}$$

sharafat.ali@ieee.org

Single Phase Full Wave Rectifier

- Efficiency

$$P_{in} = I_L^2 (R_0 + R_L) = \left(\frac{I_{LM}}{\sqrt{2}} \right)^2 (R_0 + R_L) = \frac{1}{2} I_{LM}^2 (R_0 + R_L)$$

$$P_{dc} = I_{L(dc)}^2 (R_0 + R_L) = \left(\frac{2 I_{LM}}{\pi} \right)^2 (R_0 + R_L) = \frac{4 I_{LM}^2}{\pi^2} (R_0 + R_L)$$

$$\eta = \frac{P_{dc}}{P_{in}} = \left(\frac{8}{\pi^2} \right) \left(\frac{R_L}{R_0 + R_L} \right) = \frac{0.812}{(1 + R_0 / R_L)} = \frac{81.2\%}{(1 + R_0 / R_L)}$$

sharafat.ali@ieee.org

Single Phase Full Wave Rectifier

- Frequency Components

$$V_L = V_{LM} \left(\frac{2}{\pi} - \frac{4}{3\pi} \cos 2\omega t - \frac{4}{15\pi} \cos 4\omega t - \frac{4}{35} \cos 6\omega t - \dots \right)$$

$$V_{L(dc)} = \frac{2V_{LM}}{\pi}; V_{L1} = \frac{4V_{LM}}{\sqrt{2} \cdot 3\pi}, V_{L2} = \frac{4V_{LM}}{\sqrt{2} \cdot 15\pi} \text{ etc.}$$

$$V_{L(ac)} = \sqrt{V_{L1}^2 + V_{L2}^2} = \sqrt{\left(\frac{4V_{LM}}{\sqrt{2} \cdot 3\pi} \right)^2 + \left(\frac{4V_{LM}}{\sqrt{2} \cdot 15\pi} \right)^2} = 0.305 V_{LM}$$

$$I_{L(ac)} = I_{r(rms)} = \sqrt{I_{L1}^2 + I_{L2}^2} = 0.305 I_{LM}$$

sharatat.ali@ieee.org

Single Phase Full Wave Rectifier

- **Ripple Factor**



$$\gamma = \frac{V_{L(ac)}}{V_{L(dc)}} = \frac{V_{r(rms)}}{V_{L(rms)}} = \frac{0.305 V_{LM}}{0.636 V_{LM}} = 0.482$$

- **PIV**

$$PIV = 2 V_{sm}$$



sharafat.ali@ieee.org

Full Wave Bridge Rectifier

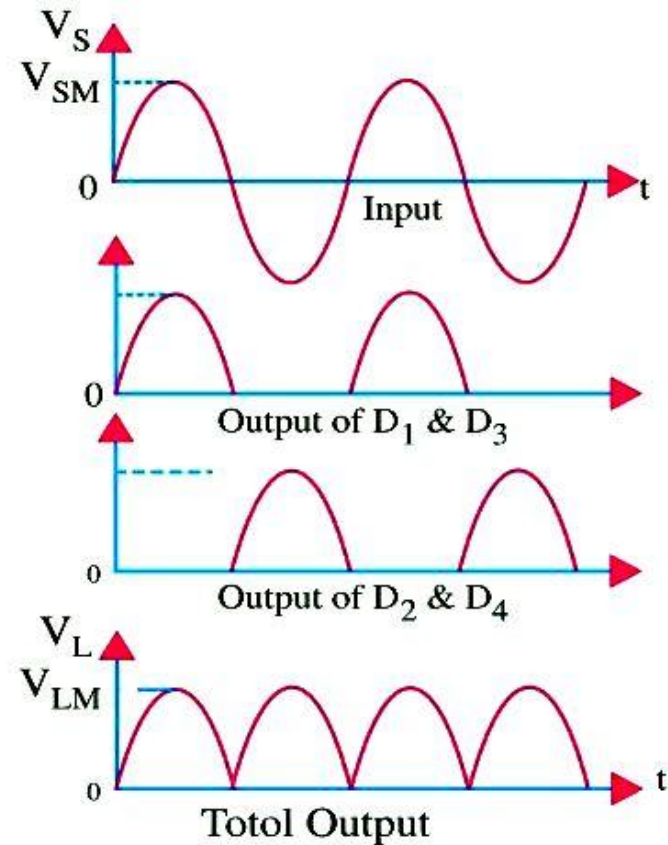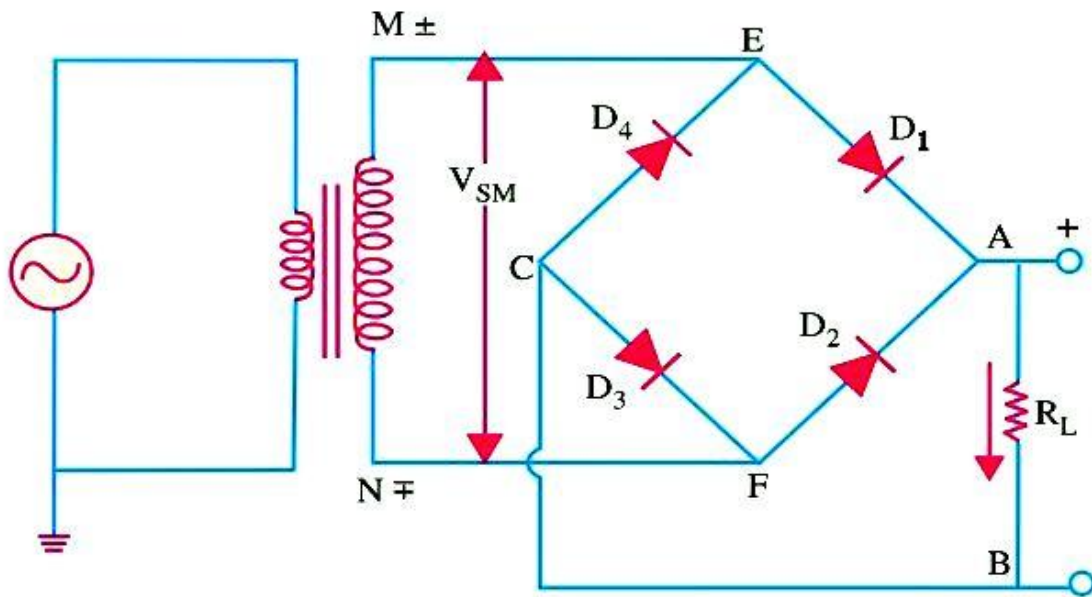

Full Wave Bridge Rectifier Four Discrete Diodes

Full Wave Bridge Rectifier

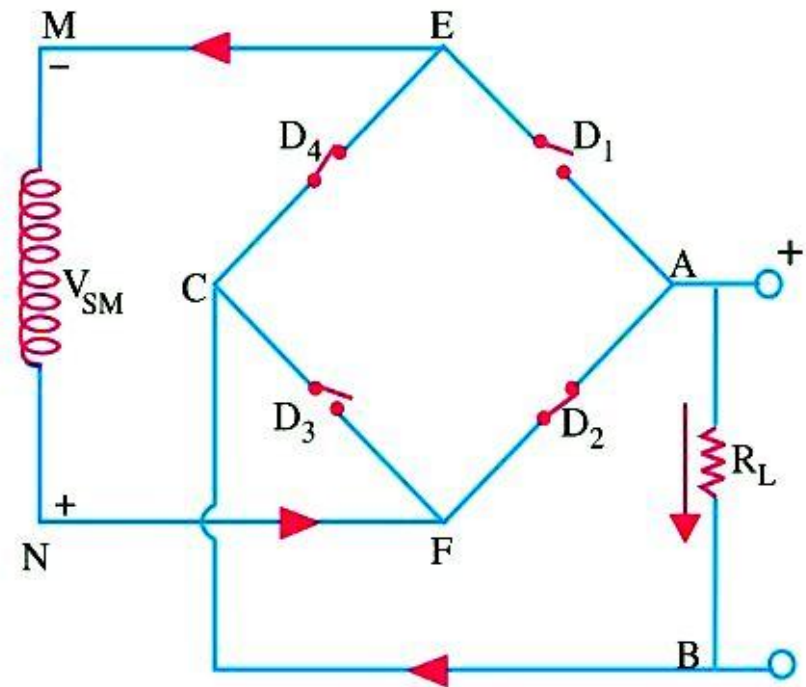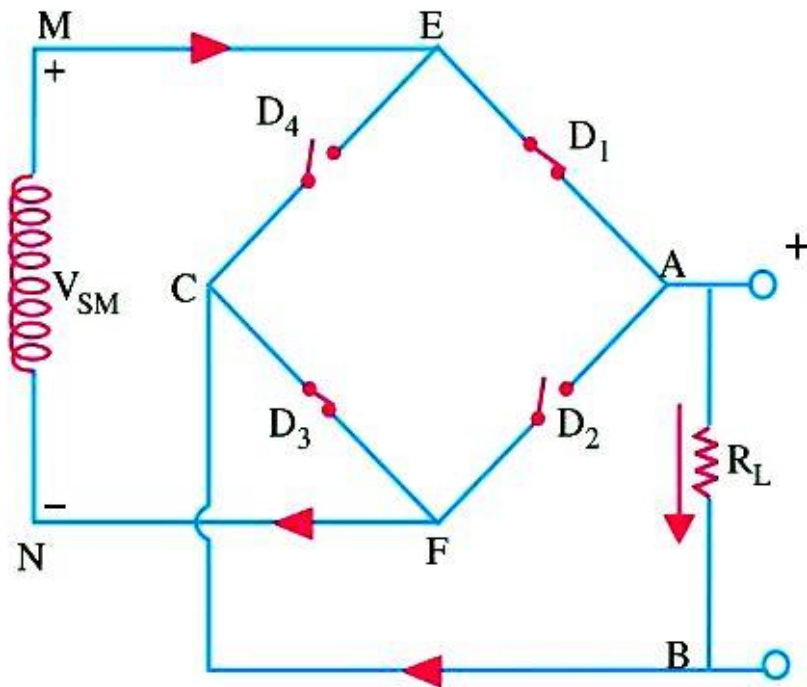

sharafat.ali@ieee.org

Full Wave Bridge Rectifier

Advantages of Full Wave Bridge Rectifier Four Discrete Diodes:

- no centre-tap is required on the transformer
- much smaller transformers are required
- it is suitable for high-voltage applications
- it has less *PIV* rating per diode

sharafat.ali@ieee.org