

Circuit

Circuit \rightarrow ৫ টি element যাকে

- I. voltage source
 - II. Current
 - III. Resistor
 - IV. Inductor
 - V. Capacitor
- (source / load)

① Active element \rightarrow যে নিজে কাজ করতে পারে

② Passive element \rightarrow Active-র সহায় হিসেবে নিয়োজিত


* Resistance \rightarrow $\frac{V}{I} \rightarrow \Omega / \text{ohm}$

* Inductor \rightarrow $\frac{1}{\omega L} \rightarrow \text{Henrey} / H$

* Capacitor \rightarrow $\frac{C}{\omega} \rightarrow \text{farade} / F$

① voltage source $\begin{cases} AC \rightarrow \frac{P.I}{\sqrt{2}} V_{ac} \\ DC \rightarrow + \text{ } \ominus V_{ac} \end{cases}$

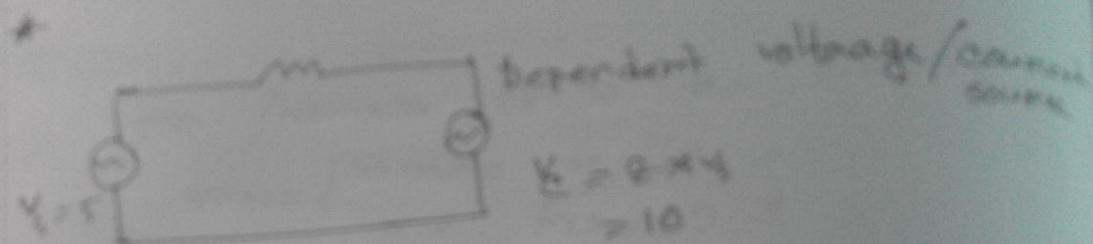② Current source $\begin{cases} AC \rightarrow \text{Amps} / A \\ DC \rightarrow \text{Amps} / A \end{cases}$



- * $\Delta n = 1 \times 10^{16}$
 $\Delta p = 1 \times 10^{17}$
 $\Delta b = 1 \times 10^{-12}$
 $\Delta m = 1 \times 10^{-3}$
 $\Delta k = 1 \times 10^3$
 $\Delta v = 10 \times 10^6$

n-type:

- I. અકાર્ણકી ઘોડ
- II. As doping
- III. ધન ધારક ના negative ફ્રી charge
- IV. 3 ઈલેક્ટ્રોન




P-type:

- I. વિઘટકી ઘોડ
- II. Al doping
- III. positive ના ધન ધારક HOLE ફ્રી
- IV. 3 ઈલેક્ટ્રોન

Diode: P & n - type এর সমন্বয়ে
 গঠিত। AC থেকে DC to converts করে-
 Rectifiers.

* Working principle P-N Junction diode:

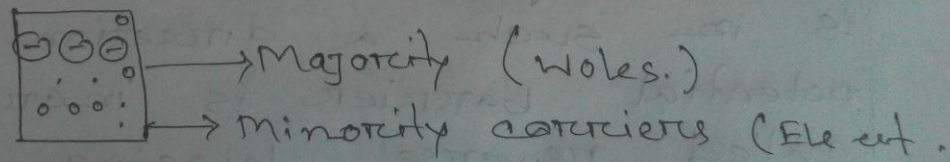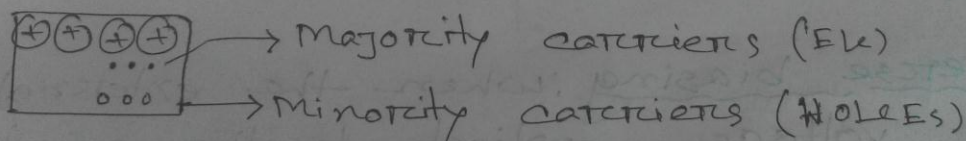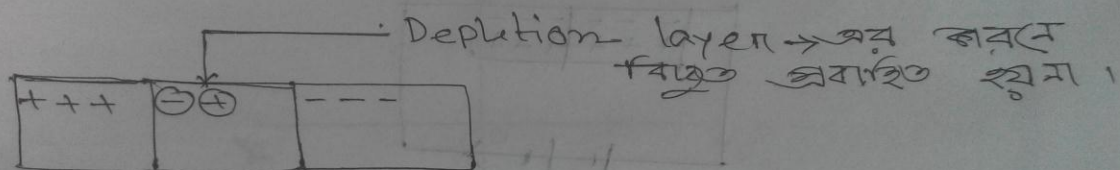
- I. Majority carrier
- II. Minority carrier.




P-type.

Biasing a pn junction:

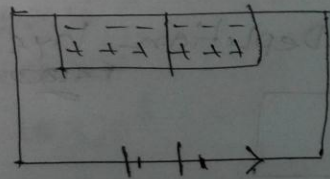① Forward biasing: When external d.c. voltage applied to the junction is in such a direction that it reduces the potential barrier, thus permitting current flow, it is called forward biasing.



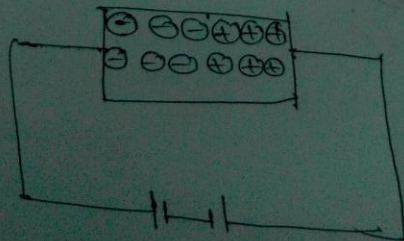
Reverse biasing: When the external d.c. voltage applied to the junction is in such a direction that potential barrier is increased it is called reverse biasing.




* characteristics current of P-N Junction diode or, VI characteristic curve.

On, volt.

Ideal diode / Practical diode

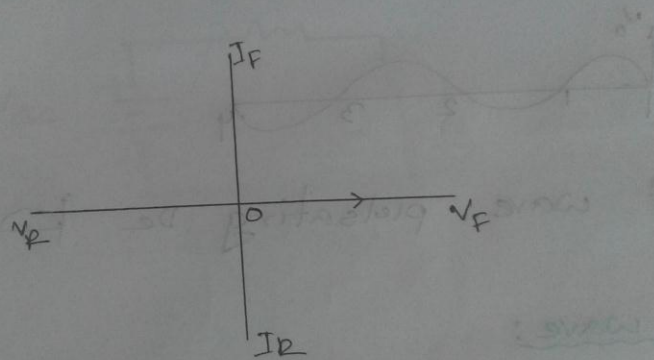

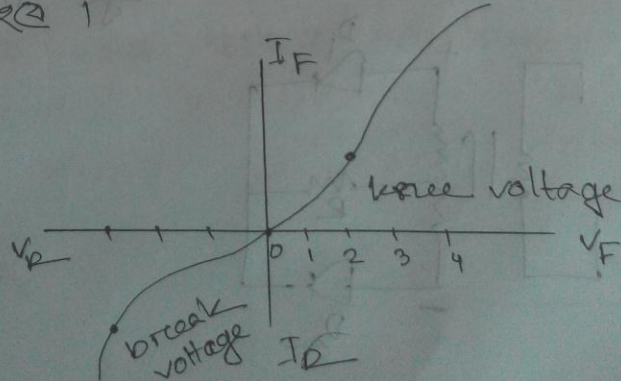0 থেকে সাল্পাত V_F এর পক্ষে বাড়লে current flow হানি হবে।





PIV: Peak Inverse voltage or voltage এর কারণে diode যাবে না।

* Knee voltage: It is the forward voltage at which the current through the junction starts to increase rapidly.

Walt wave


* Diode

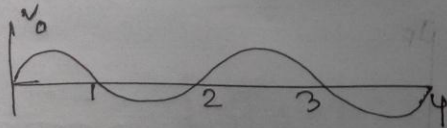

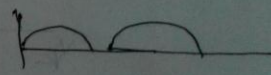Walt wave, pulsating DC 

Full wave:

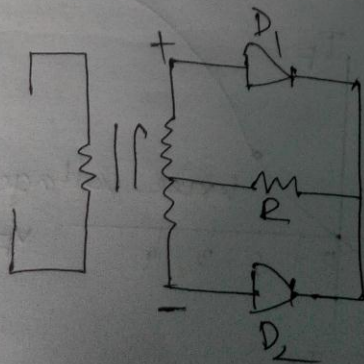
1. Center full wave rectifier
2. full wave bridge rectifier.





Resistor:

$$V = V_{dc}$$

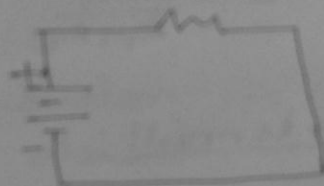


Resistor.

$$I \propto V$$


$$I = \frac{1}{R} \times V$$

$$I = GV \quad [G = \frac{1}{R} \text{ mho/V/segment}]$$

++ / -- চার্ক এর দ্বারা voltage.

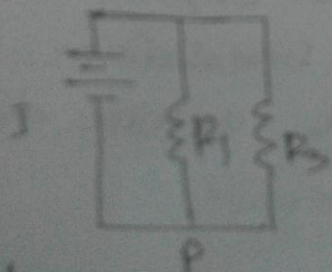

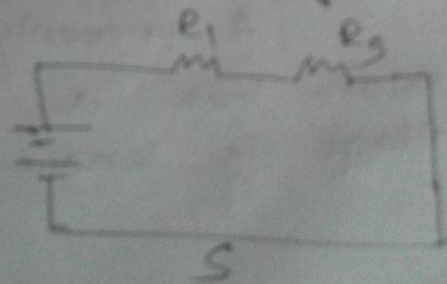
$$\frac{1}{R_P} = \frac{1}{R_1} + \frac{1}{R_2}$$



$$R_T = R_1 + R_2$$

* Current divider rule:

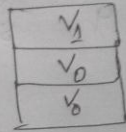

$$V = V_1 = V_2$$

$$I_1 = \frac{I \times R_2}{R_1 + R_2}$$

$$I_2 = \frac{I \times R_1}{R_1 + R_2}$$

voltage divider rule:


$$I = I_1 = I_2$$

$$V_1 = \frac{V \times R_1}{R_1 + R_2}$$

$$V_2 = \frac{V \times R_2}{R_1 + R_2}$$

Zenar Diode:

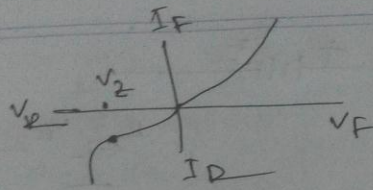A properly doped crystal diode which has a sharp breakdown voltage is known as a zenar diode




$$R = \frac{E_i - E_o}{(I_Z)_{\min} + (I)_{\max}}$$

$$= \frac{(13 - 10)}{(15 + 85)} = \frac{3}{100} = 30 \Omega$$

* A semiconductor is a substance which has almost filled valence band and nearly empty conduction band with a very small energy gap separating the two.


KVL and KCL:

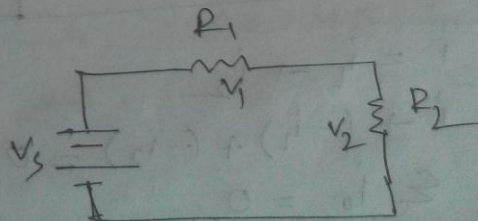

$$V_S = V_1 + V_2$$

$$V_S = (-V_1) + (-V_2) = 0$$

$$\sum V_i = 0$$

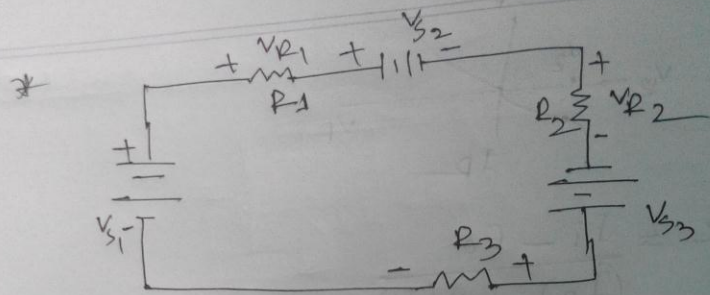


$$* V_{s1} + (-V_{s2}) + V_{s3} = V_{R1} + V_{R2} + V_{R3}$$

$$\rightarrow V_{s1} - V_{s2} + V_{s3} = V_{R1} + V_{R2} + V_{R3}$$

$$\Rightarrow V_{s1} - V_{s2} + V_{s3} - V_{R1} - V_{R2} - V_{R3} = 0$$

KCL:

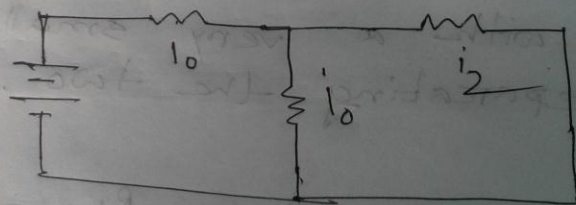


$$i = i_1 + i_2$$

$$i + (-i_1) + (-i_2) = 0$$

$$\Sigma i_0 = 0$$

KCL:

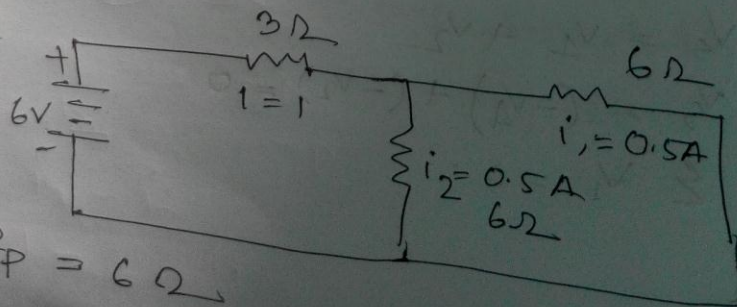

$$R_P = 6 \Omega$$


$$V_S = 6V$$

$$i = 6/6 = 1 \text{ A}$$

$$1 \text{ A} = 0.5 + 0.5 \\ = 1 \text{ A}$$

KVL:
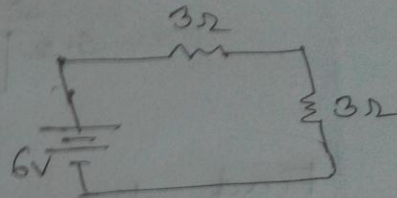
$$6 \text{ V} = IR_1 + IR_2 \\ = 1 \times 3 + 1 \times 3 \\ = 6 \text{ V}$$



$$V = IR$$


$$V = IR$$

* Resistance \rightarrow উল্টো হয় (+ হলে N) (- হলে P) $e+$ থেকে $e-$ থেকে

A Resistance \rightarrow উল্টো হয় (+ হলে N) $e+$ থেকে (বিক্রম হলে) (- হলে P) $e-$ থেকে (কম হলে)।

voltage rise = voltage drop
source = voltage drop

MESW Analysis:

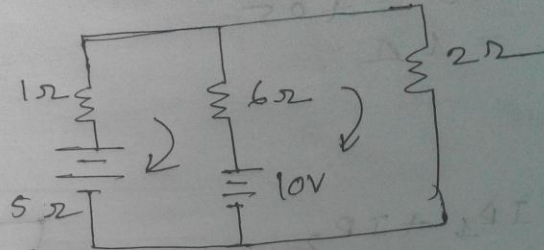

Find the current in each branch

Loop 1 = KVL:

voltage rais = voltage drop

$$5 - 10 = i_1 \times 1 + (i_1 - i_2) \times 6$$

$$-5 = 7i_1 - 6i_2 \quad \text{--- (I)}$$

Loop 2 = KVL:

$$10 \text{ V} = 6(i_2 - i_1) + 2i_2$$

$$10 \text{ V} = -6i_1 + 8i_2 \quad \text{--- (II)}$$

$$\textcircled{I} \quad 3 \quad \textcircled{II} \Rightarrow$$


$$i_1 = 1 \text{ Amp}$$

$$i_2 = 2 \text{ Amp}$$

$$\therefore i_1 - i_2$$

$$1 - 2 = -1 \text{ Amp}$$

MATH:

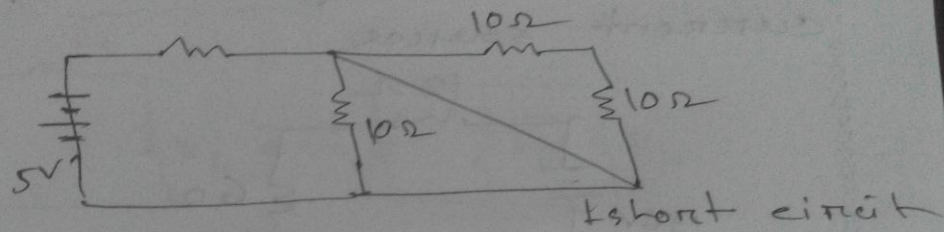

Find current I .

* $V = I \times R$

$I = \frac{V}{R}$

$= \frac{-5}{5}$


$= 1 \text{ Amp}$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$


* $V = \frac{V}{R}$

$= \frac{5}{10}$

$= 0.5$

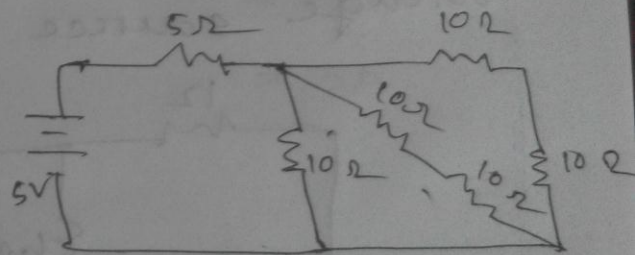


Super position theorem:

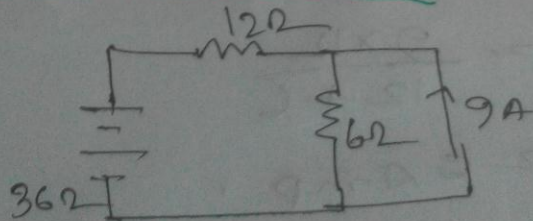

$I = I_1 + I_2$

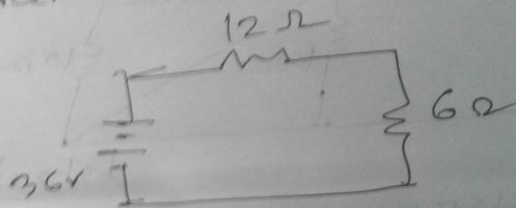① Consider voltage source \Rightarrow open
current source




$$I = \frac{V}{R_1}$$

$$= \frac{36}{12 + 6}$$

$$= 2 \text{ Amp}$$

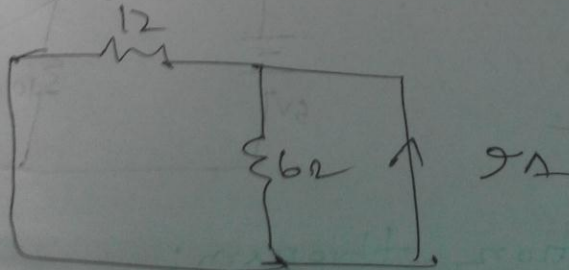② Consider current source \Rightarrow
voltage source short circuited



$$I_2 = \frac{9 \times 12}{12 + 6}$$



$$= 8 \text{ Amp}$$

$$\therefore I = I_1 + I_2$$

$$= 2 + 6$$

$$= 8 \text{ Amp}$$

Source conversion:

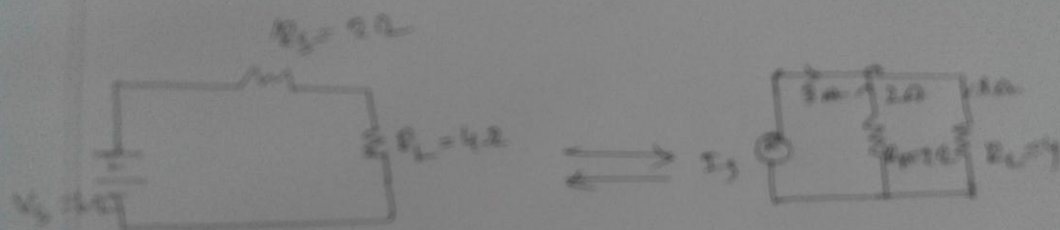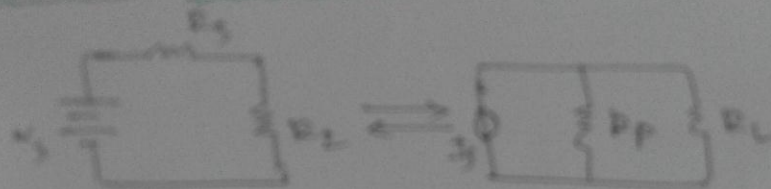

$$I_L = \frac{V_s}{R_s + R_L}$$

$$= \frac{24}{3 + 4}$$

$$= 1A$$

$$I_s = \frac{V_s}{R_s}$$

$$= \frac{24}{3}$$

$$= 3A$$