

# Electrical Circuit and Electronics


## Filters

[sharafat.ali@ieee.org](mailto:sharafat.ali@ieee.org)

# Reference Books Recommended

- **Introductory Circuit Analysis**  
- *Robert L. Boylestad*

sharafat.ali@ieo

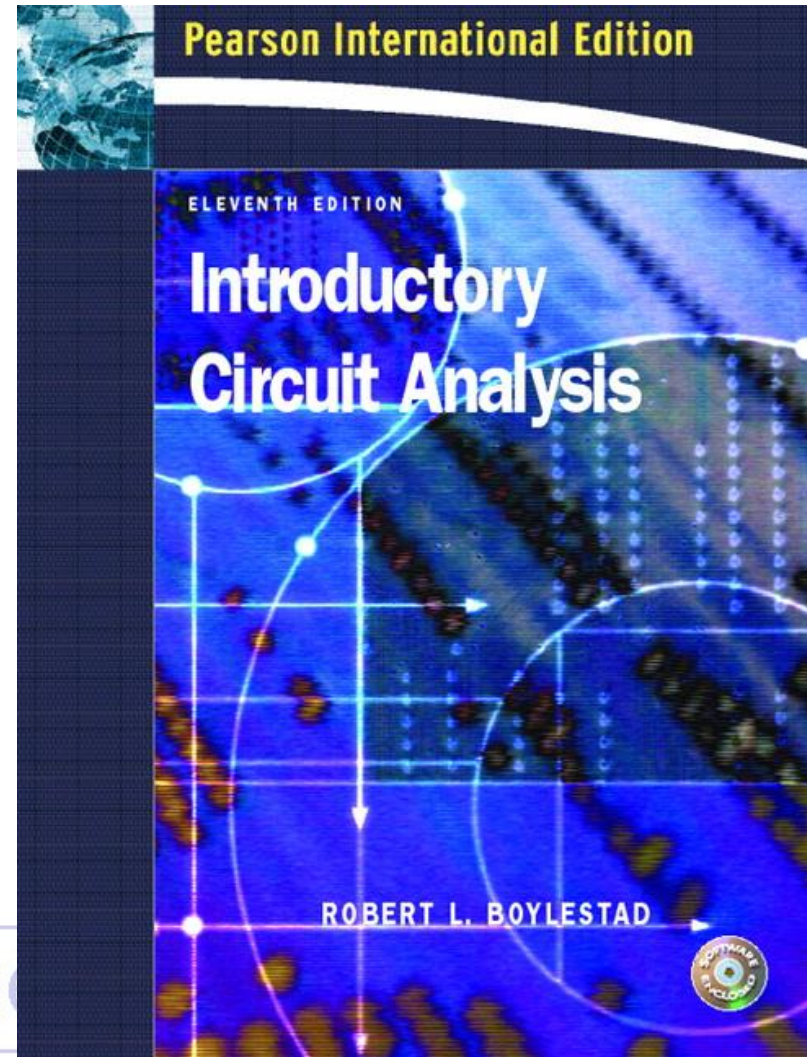

**Any combination of passive ( $R$ ,  $L$ , and  $C$ ) and/or active (transistors or operational amplifiers) elements designed to select or reject a band of frequencies is called a filter.**

- ❑ **Passive filters** are those filters composed of series or parallel combinations of  $R$ ,  $L$ , and  $C$  elements
- ❑ **Active filters** are filters that employ active devices such as transistors and operational amplifiers in combination with  $R$ ,  $L$ , and  $C$  elements


[sharafat.ali@ieee.org](mailto:sharafat.ali@ieee.org)

All filters belong to the four broad categories of:

- **low-pass**
- **high-pass**
- **pass-band**
- **stop-band**


[sharafat.ali@ieee.org](mailto:sharafat.ali@ieee.org)

# Low Pass Filter

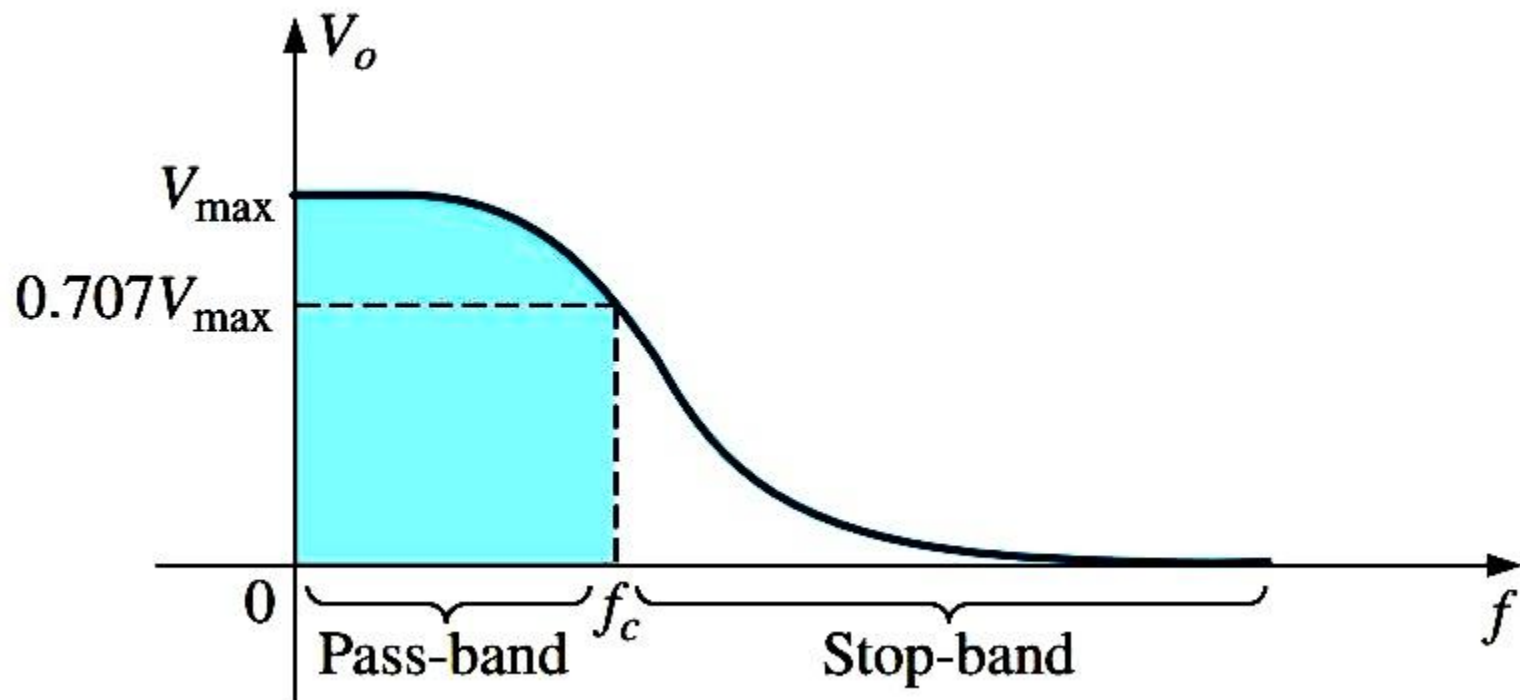


[sharafat.ali@ieee.org](mailto:sharafat.ali@ieee.org)

# High Pass Filter

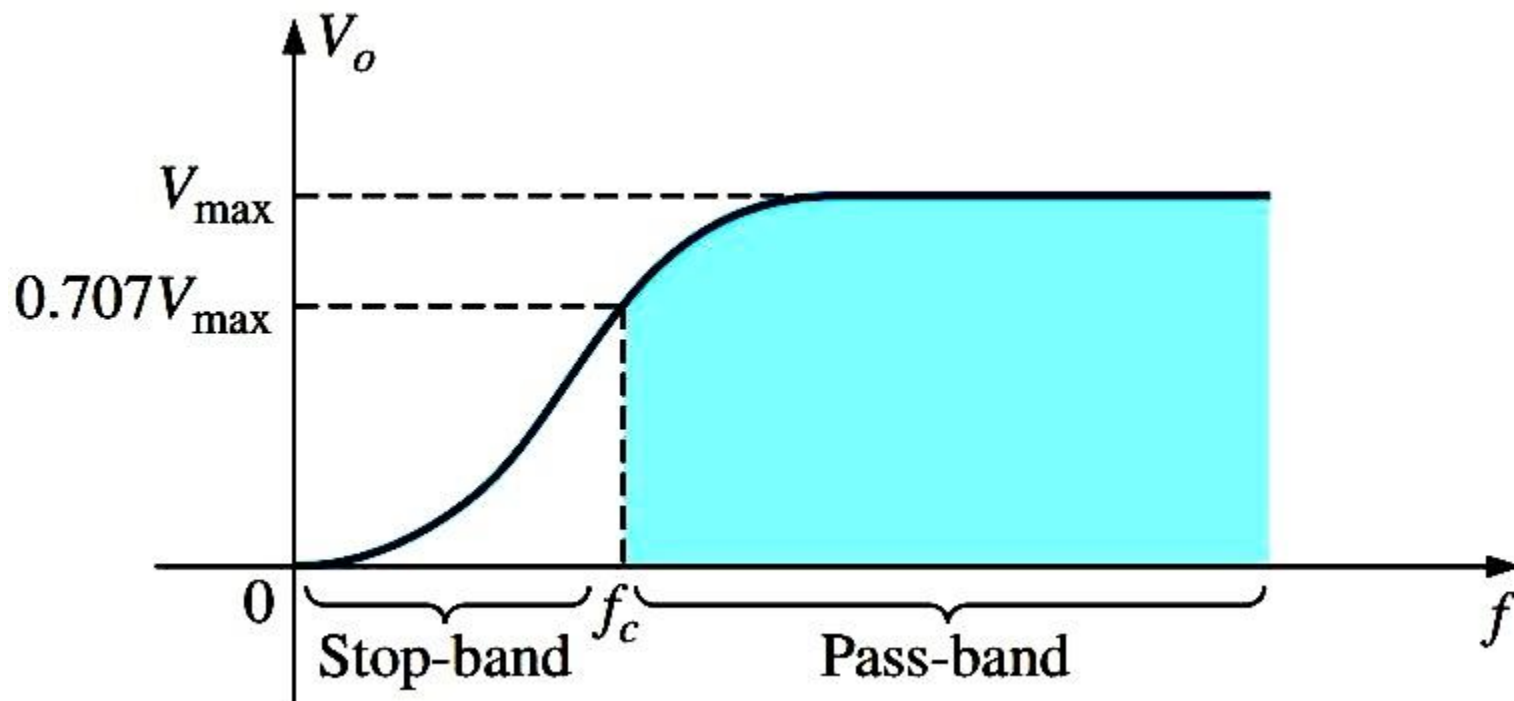

[sharafat.ali@ieee.org](mailto:sharafat.ali@ieee.org)


# Band Pass Filter

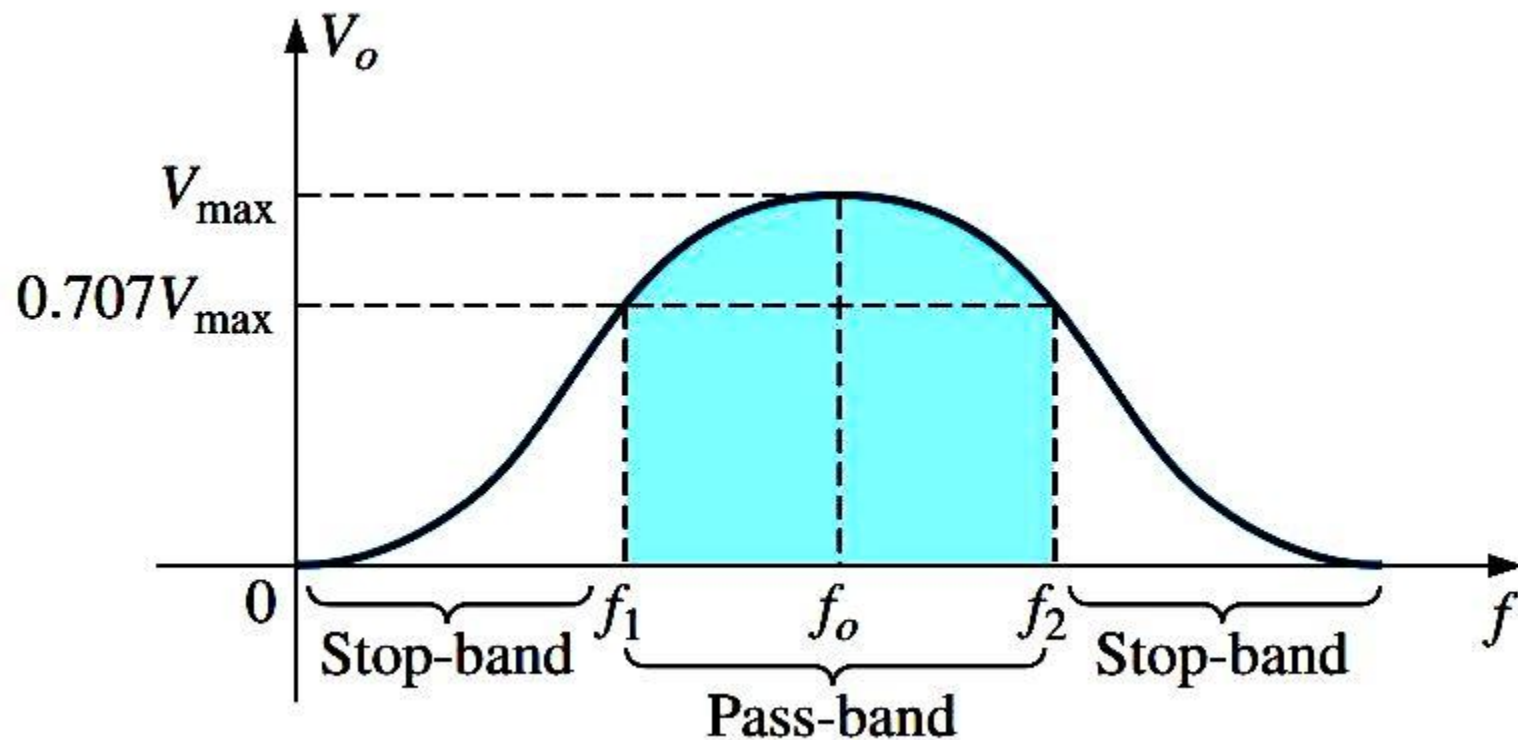

[[sharafat.ali@ieee.org](mailto:sharafat.ali@ieee.org)]




# Stop Band Filter

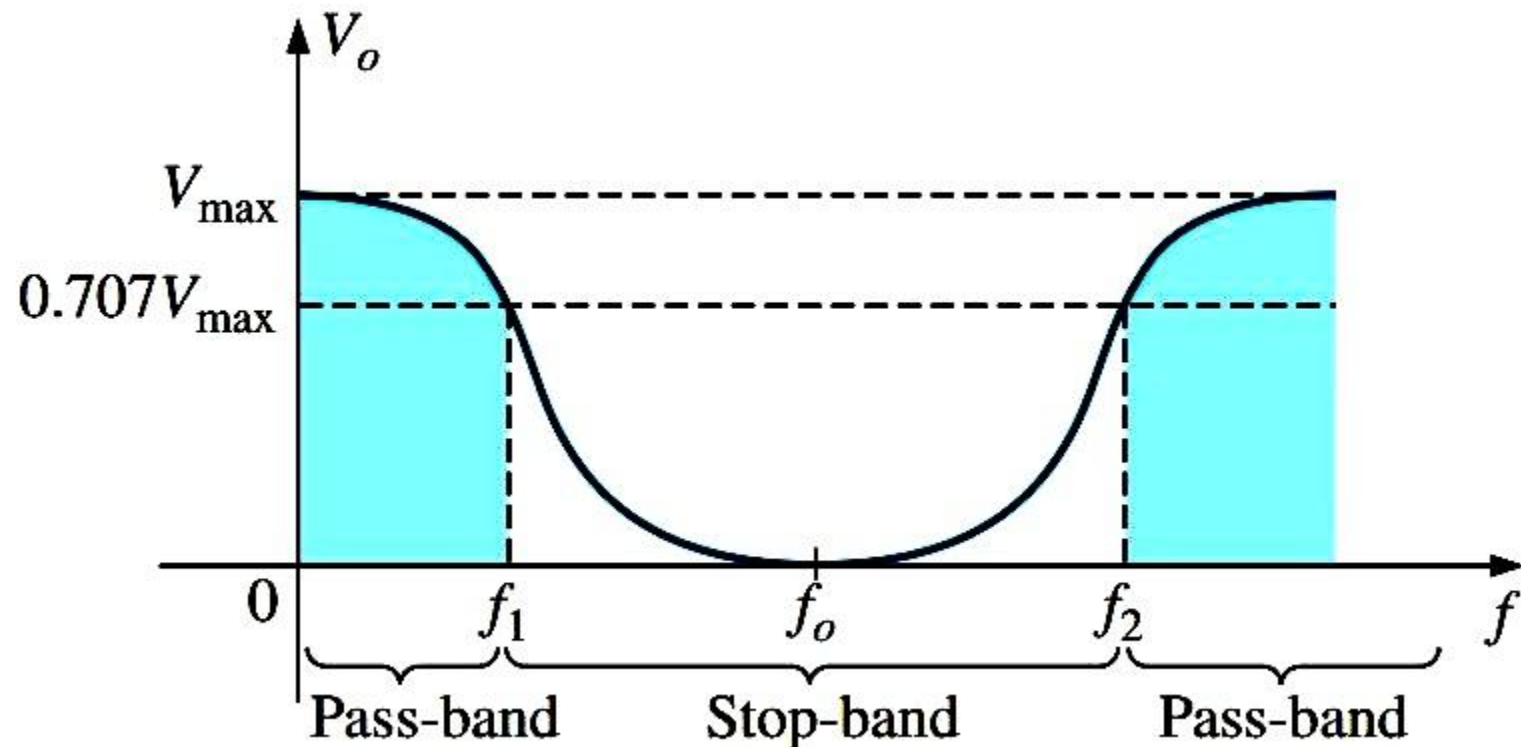

[[sharafat.ali@ieee.org](mailto:sharafat.ali@ieee.org)]



# R-C Low Pass Filter

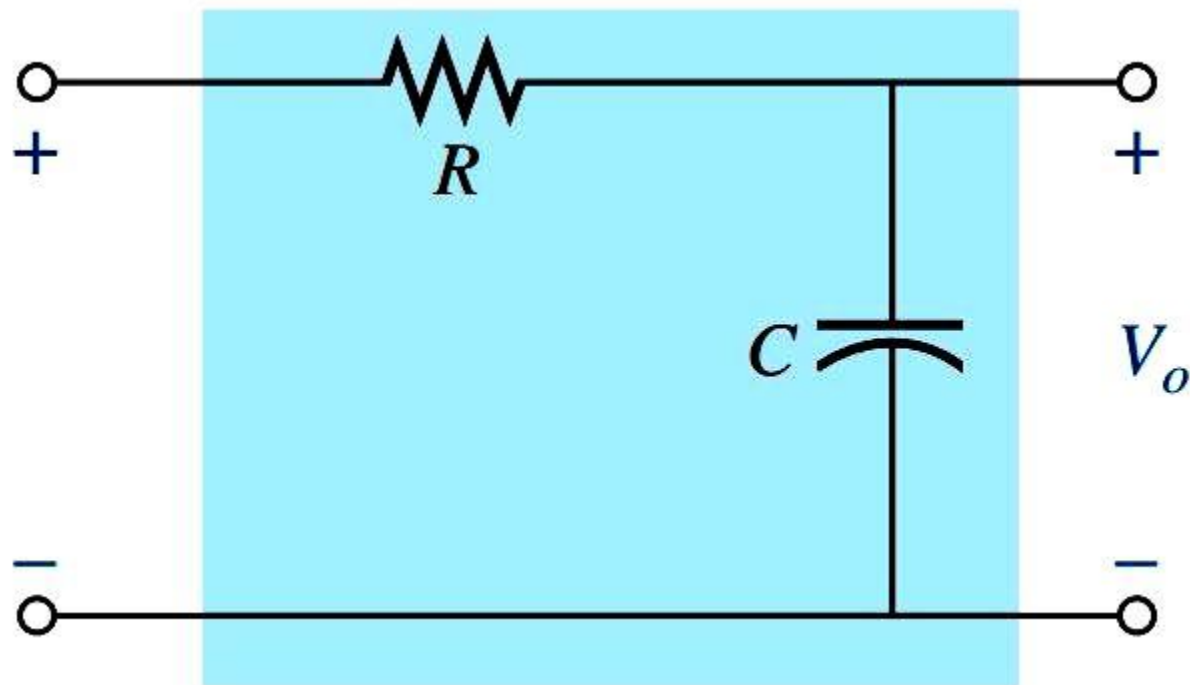


[sharafat.ali@ieee.org](mailto:sharafat.ali@ieee.org)
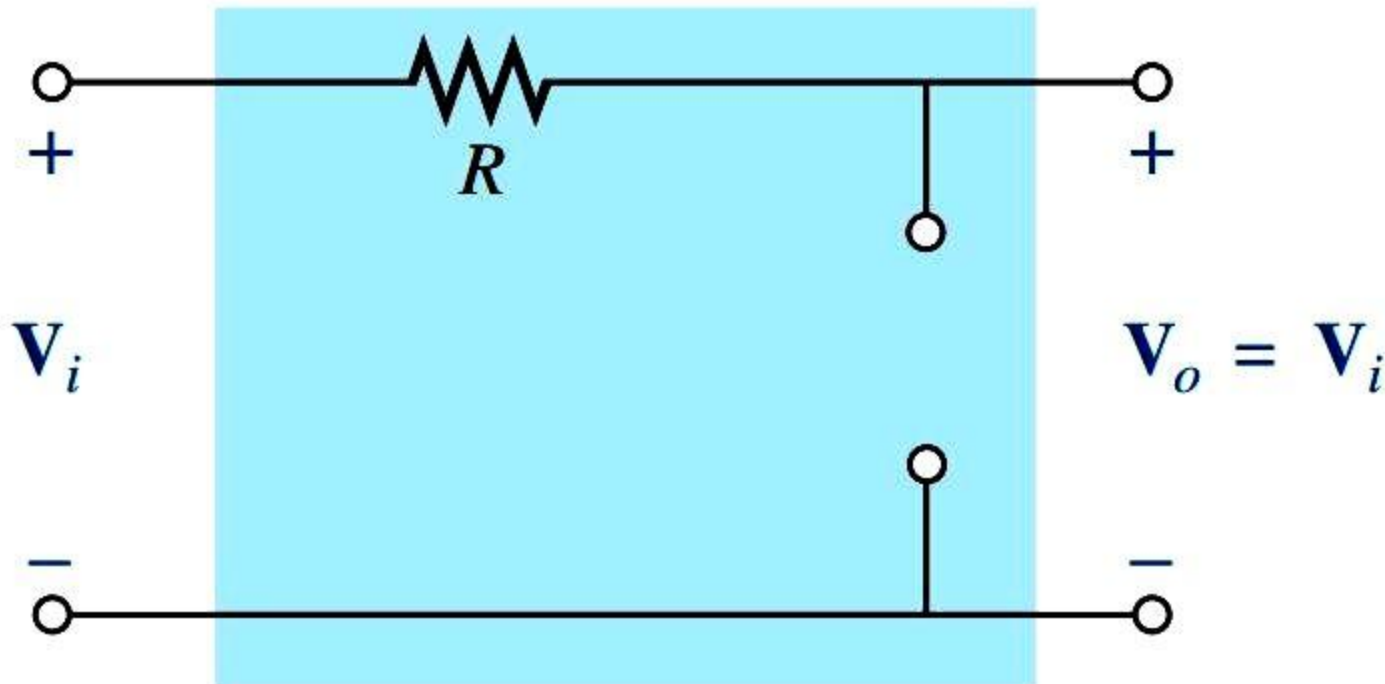
# R-C Low Pass Filter

At  $f = 0$  Hz,


$$X_C = \frac{1}{2\pi fC} = \infty \Omega$$



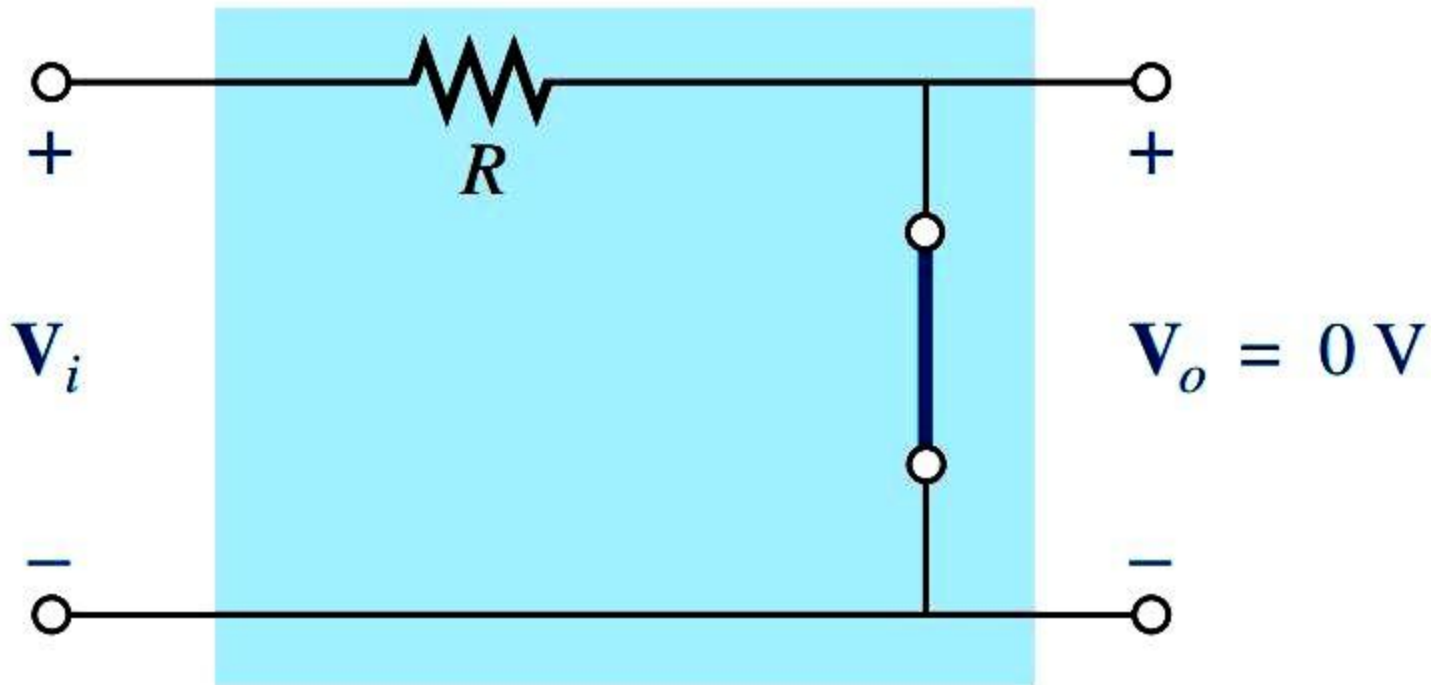
# R-C Low Pass Filter

At very high frequencies, the reactance is


$$X_C = \frac{1}{2\pi fC} \cong 0 \Omega$$



# R-C Low Pass Filter

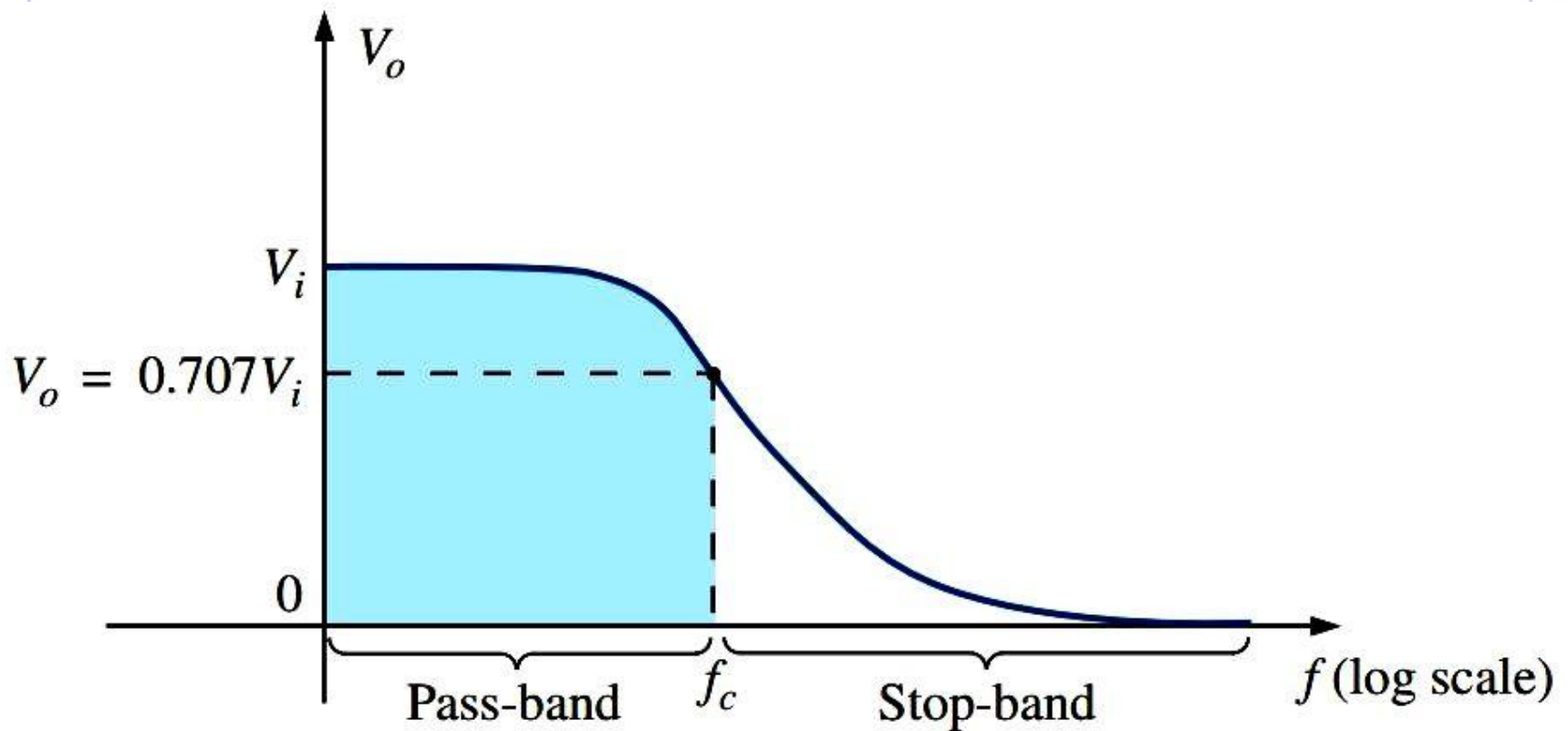

# R-C Low Pass Filter

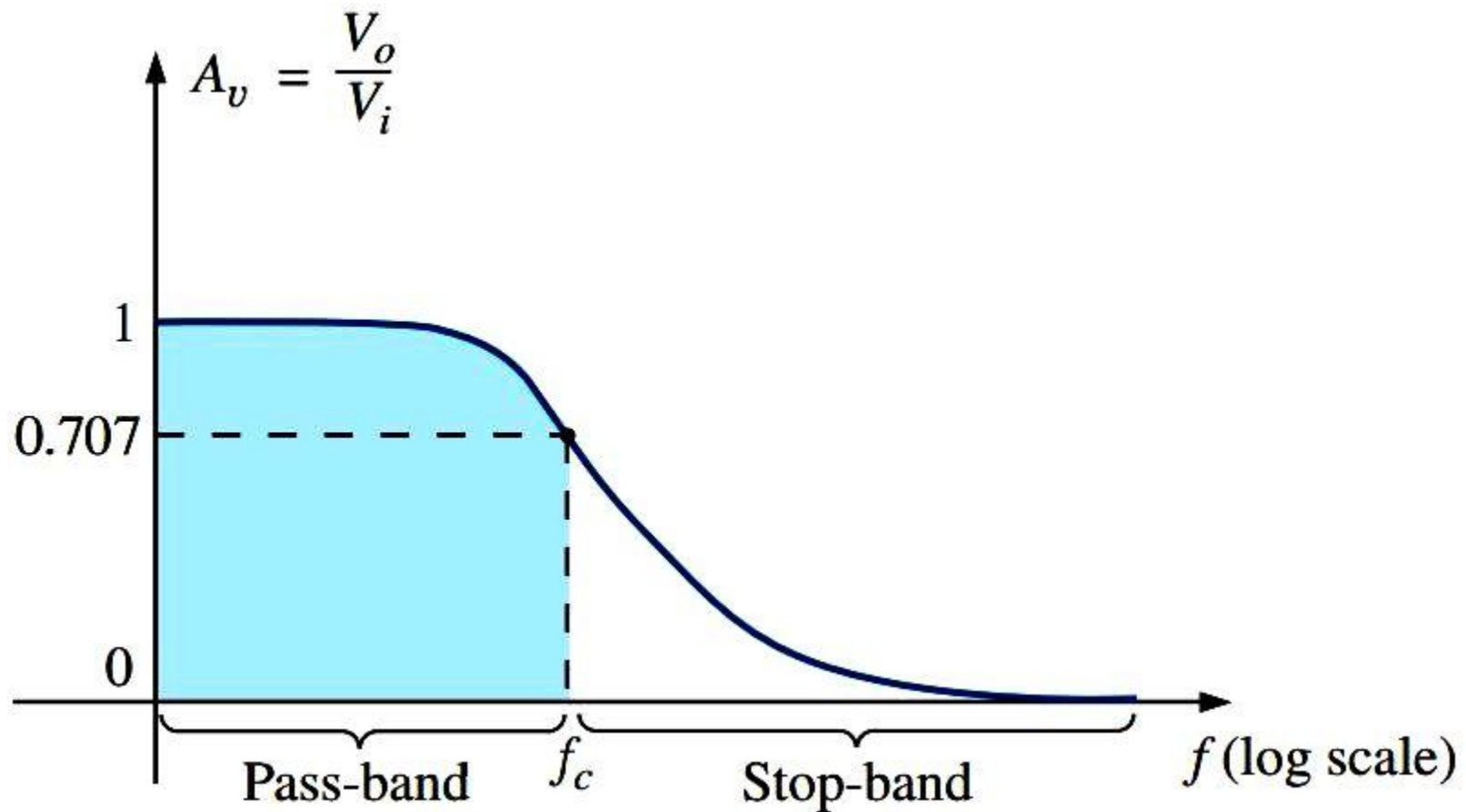

# R-C Low Pass Filter

$$\mathbf{V}_o = \frac{X_C \angle -90^\circ \mathbf{V}_i}{R - jX_C}$$

$$\mathbf{A}_v = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{X_C \angle -90^\circ}{R - jX_C} = \frac{X_C \angle -90^\circ}{\sqrt{R^2 + X_C^2} \angle -\tan^{-1}(X_C/R)}$$

$$\mathbf{A}_v = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{X_C}{\sqrt{R^2 + X_C^2}} \angle -90^\circ + \tan^{-1} \left( \frac{X_C}{R} \right)$$

[shafiqat.al@ieee.org](mailto:shafiqat.al@ieee.org)

# R-C Low Pass Filter

$$A_v = \frac{V_o}{V_i} = \frac{X_C}{\sqrt{R^2 + X_C^2}} = \frac{1}{\sqrt{\left(\frac{R}{X_C}\right)^2 + 1}}$$

$$\theta = -90^\circ + \tan^{-1} \frac{X_C}{R} = -\tan^{-1} \frac{R}{X_C}$$

[sharafat.ali@ieee.org](mailto:sharafat.ali@ieee.org)



# R-C Low Pass Filter

For the special frequency at which  $X_C = R$

The frequency at which  $X_C = R$  is the critical or cutoff frequency

$$A_v = \frac{V_o}{V_i} = \frac{1}{\sqrt{\left(\frac{R}{X_C}\right)^2 + 1}} = \frac{1}{\sqrt{1 + 1}} = \frac{1}{\sqrt{2}} = 0.707$$

$$\frac{1}{2\pi f_c C} = R$$

$$\text{sharafa} \quad \boxed{f_c = \frac{1}{2\pi RC}} \quad \text{e.org}$$

# R-C Low Pass Filter

$$\mathbf{V}_o = \left[ \frac{X_C}{\sqrt{R^2 + X_C^2}} \angle \theta \right] \mathbf{V}_i = \left[ \frac{X_C}{\sqrt{R^2 + X_C^2}} \angle \theta \right] V_i \angle 0^\circ$$

$$\mathbf{V}_o = \frac{X_C V_i}{\sqrt{R^2 + X_C^2}} \angle \theta$$


$$f_c = \frac{1}{2\pi RC}$$

For  $f < f_c$ ,  $V_o > 0.707V_i$

whereas for  $f > f_c$ ,  $V_o < 0.707V_i$

At  $f_c$ ,  $\mathbf{V}_o$  lags  $\mathbf{V}_i$  by  $45^\circ$

# R-C Low Pass Filter

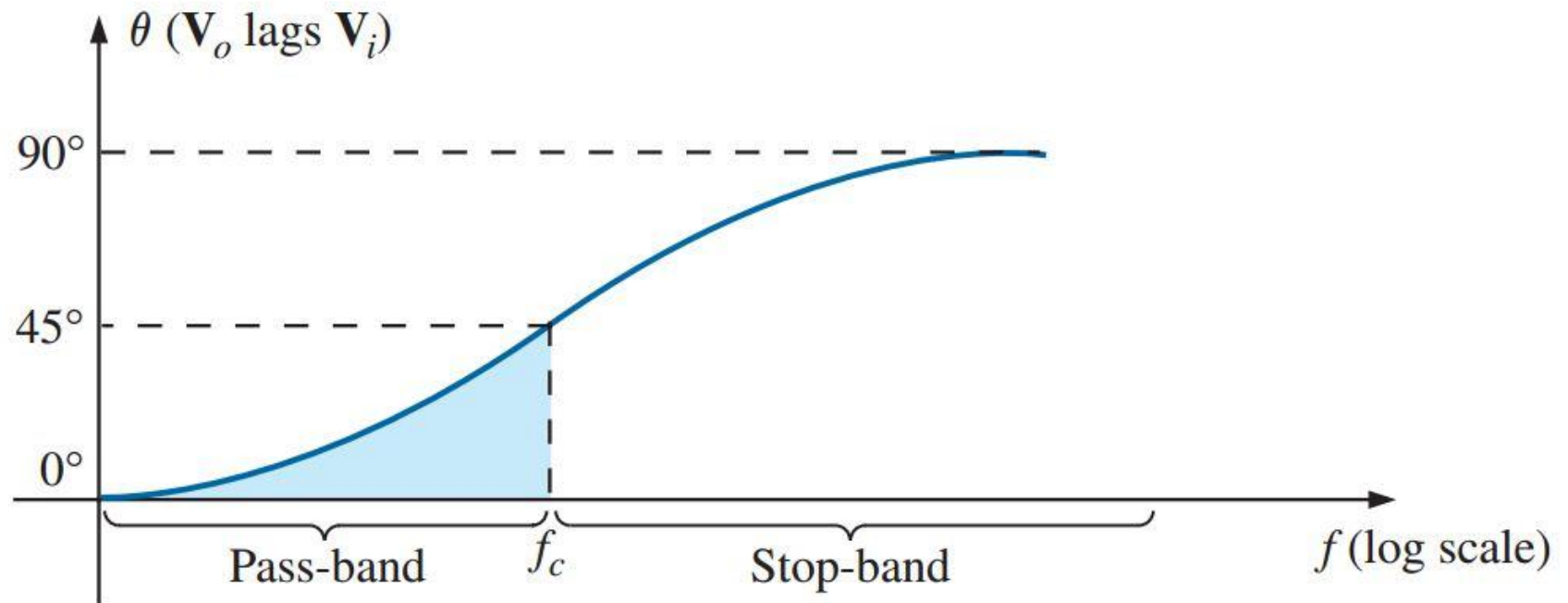


[sharafat.ali@ieee.org](mailto:sharafat.ali@ieee.org)

# R-C Low Pass Filter
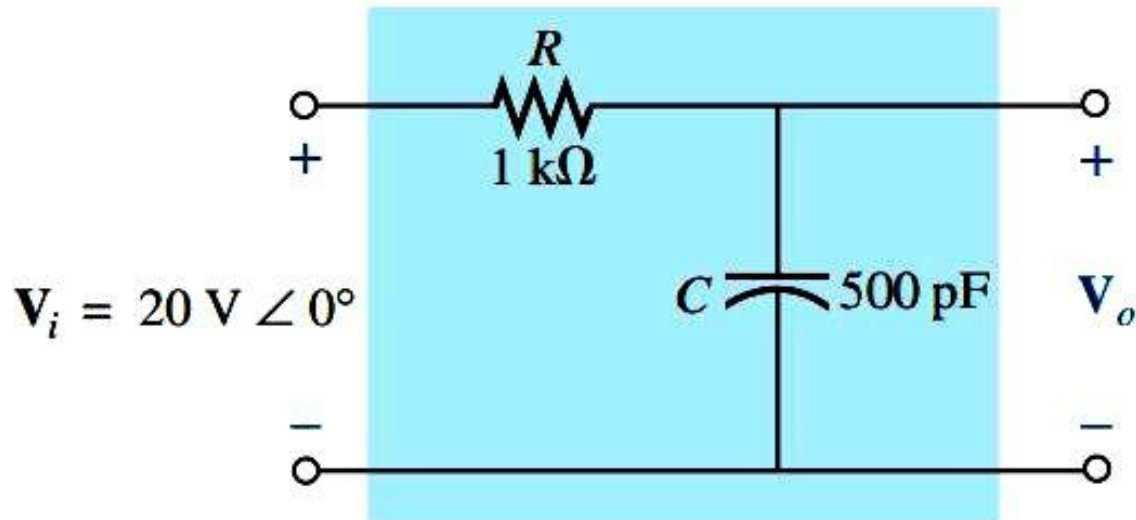
## EXAMPLE

- Sketch the output voltage  $V_o$  versus frequency for the low-pass  $R$ - $C$  filter in Fig.
- Determine the voltage  $V_o$  at  $f = 100$  kHz and 1 MHz, and compare the results to the results obtained from the curve in part (a).
- Sketch the normalized gain  $A_v = V_o/V_i$ .



# R-C Low Pass Filter

a.

$$f_c = \frac{1}{2\pi RC} = \frac{1}{2\pi(1 \text{ k}\Omega)(500 \text{ pF})} = \mathbf{318.31 \text{ kHz}}$$

At  $f_c$ ,  $V_o = 0.707(20 \text{ V}) = 14.14 \text{ V}$ . See Fig.


b.

$$V_o = \frac{V_i}{\sqrt{\left(\frac{R}{X_C}\right)^2 + 1}}$$

At  $f = 100 \text{ kHz}$ :

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(100 \text{ kHz})(500 \text{ pF})} = 3.18 \text{ k}\Omega$$

# R-C Low Pass Filter

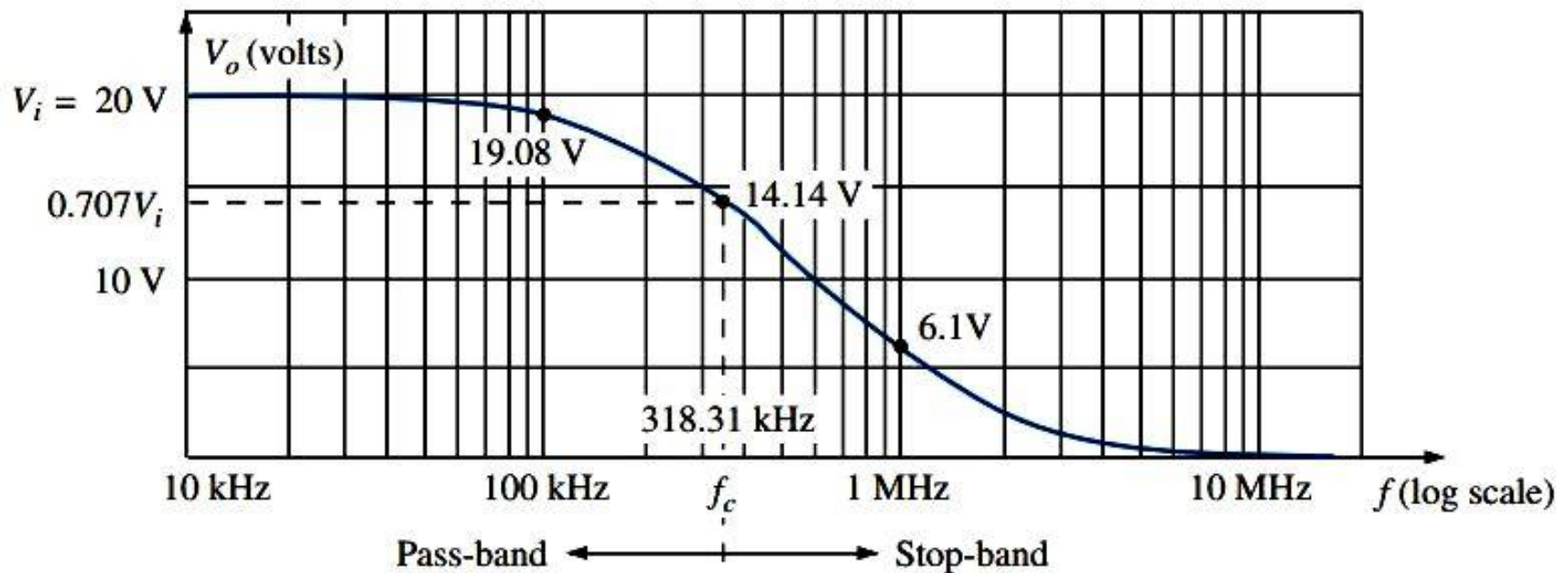

[sharafat.ali@ieee.org](mailto:sharafat.ali@ieee.org)

# R-C Low Pass Filter

and 
$$V_o = \frac{20 \text{ V}}{\sqrt{\left(\frac{1 \text{ k}\Omega}{3.18 \text{ k}\Omega}\right)^2 + 1}} = \mathbf{19.08 \text{ V}}$$


At  $f = 1 \text{ MHz}$ :

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(1 \text{ MHz})(500 \text{ pF})} = 0.32 \text{ k}\Omega$$

and 
$$V_o = \frac{20 \text{ V}}{\sqrt{\left(\frac{1 \text{ k}\Omega}{0.32 \text{ k}\Omega}\right)^2 + 1}} = \mathbf{6.1 \text{ V}}$$




# R-C Low Pass Filter

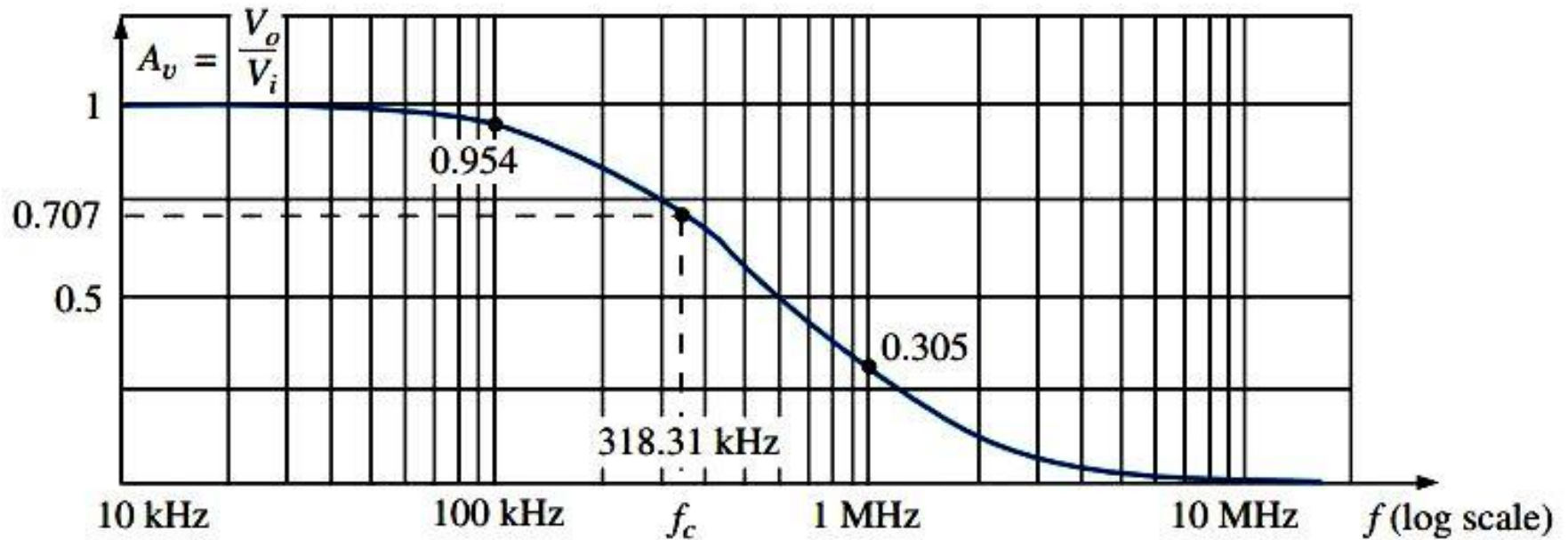

[sharafat.ali@ieee.org](mailto:sharafat.ali@ieee.org)


# R-L Low Pass Filter

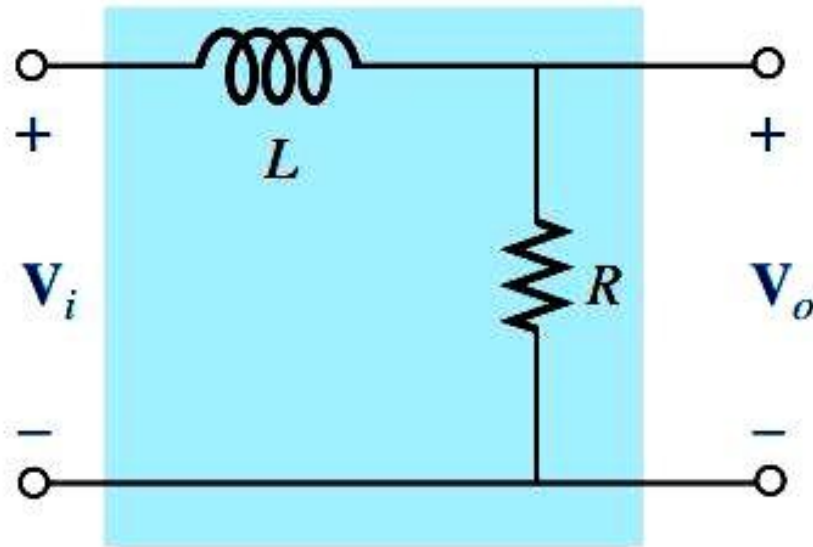

$$f_c = \frac{R}{2\pi L}$$


sharafat.ali@ieee.org

# R-C High Pass Filter

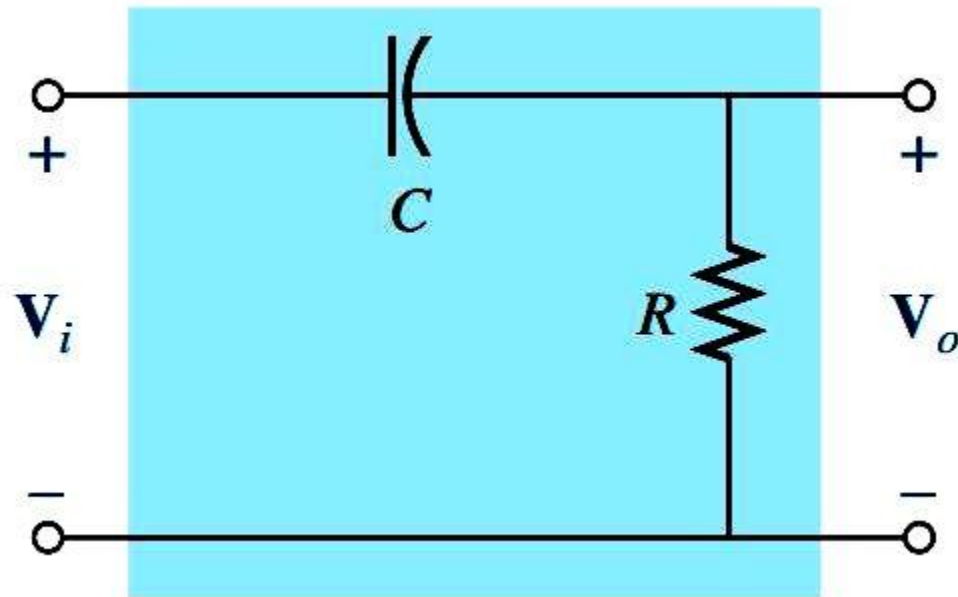

[sharafat.ali@ieee.org](mailto:sharafat.ali@ieee.org)


# R-C High Pass Filter

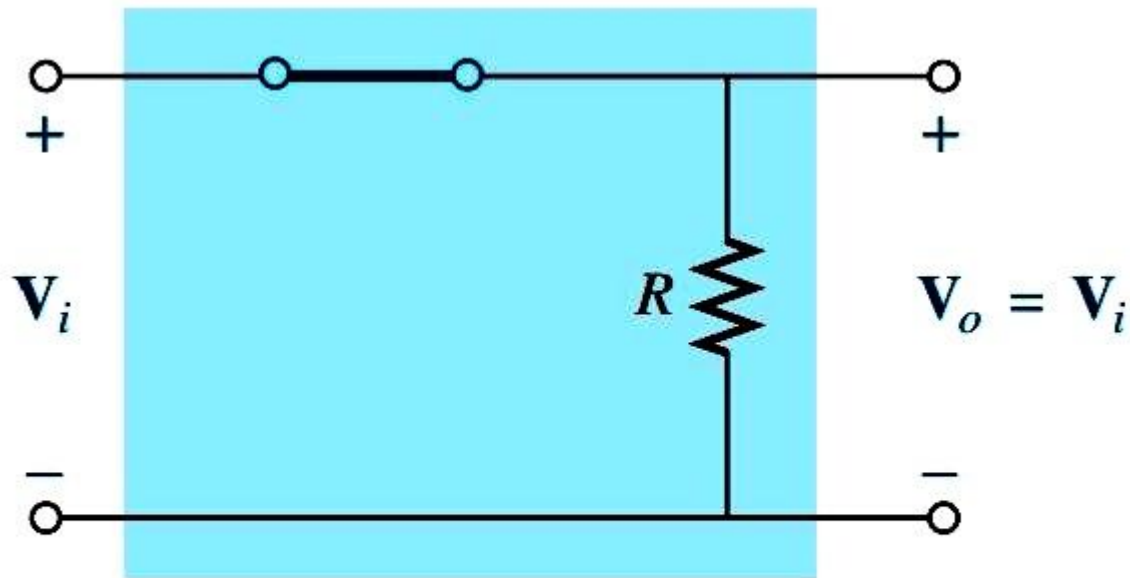

*R-C high-pass filter at very high frequencies*

[sharafat.ali@ieee.org](mailto:sharafat.ali@ieee.org)


# R-C High Pass Filter

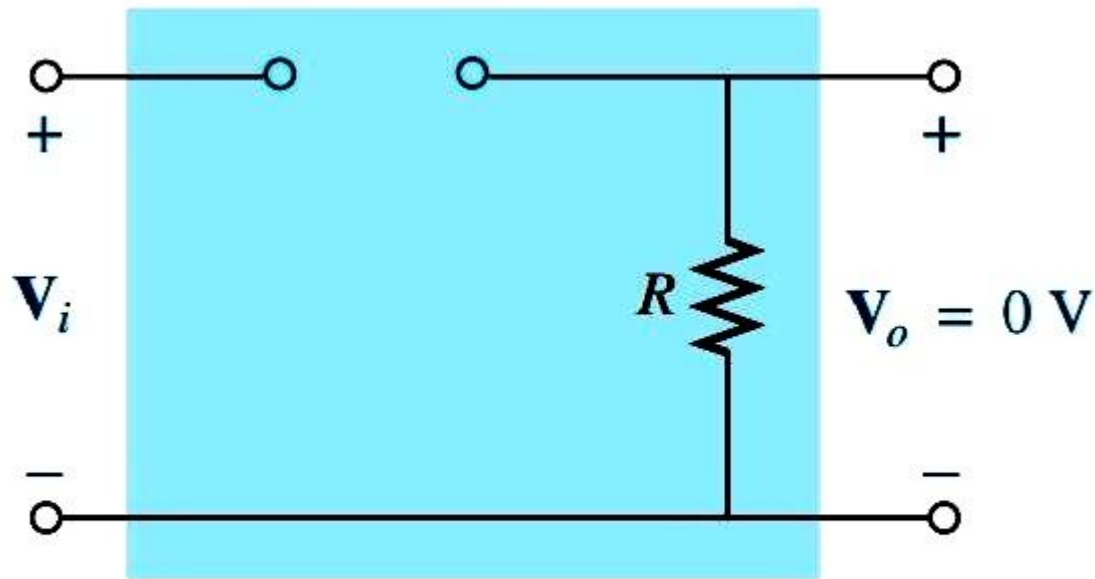

*R-C high-pass filter at  $f = 0\text{ Hz}$*


[sharafat.ali@ieee.org](mailto:sharafat.ali@ieee.org)

# R-C High Pass Filter

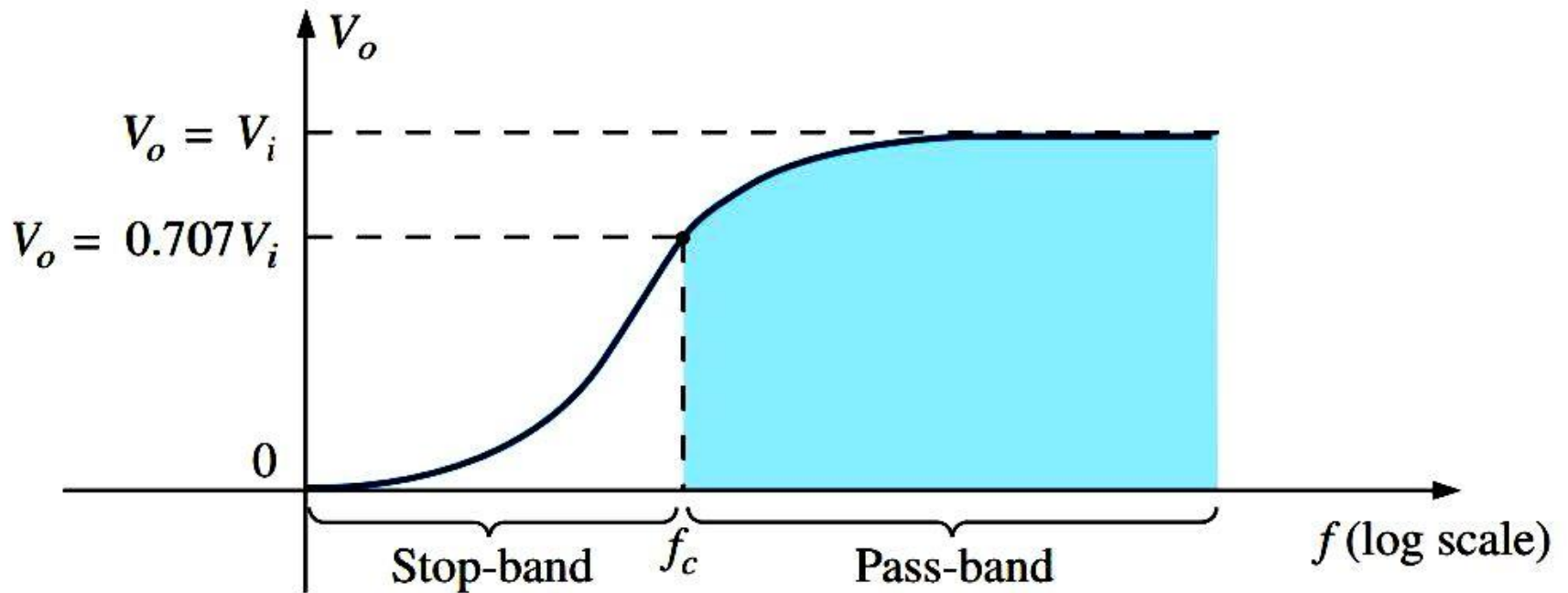

[sharafat.ali@ieee.org](mailto:sharafat.ali@ieee.org)

# R-C High Pass Filter

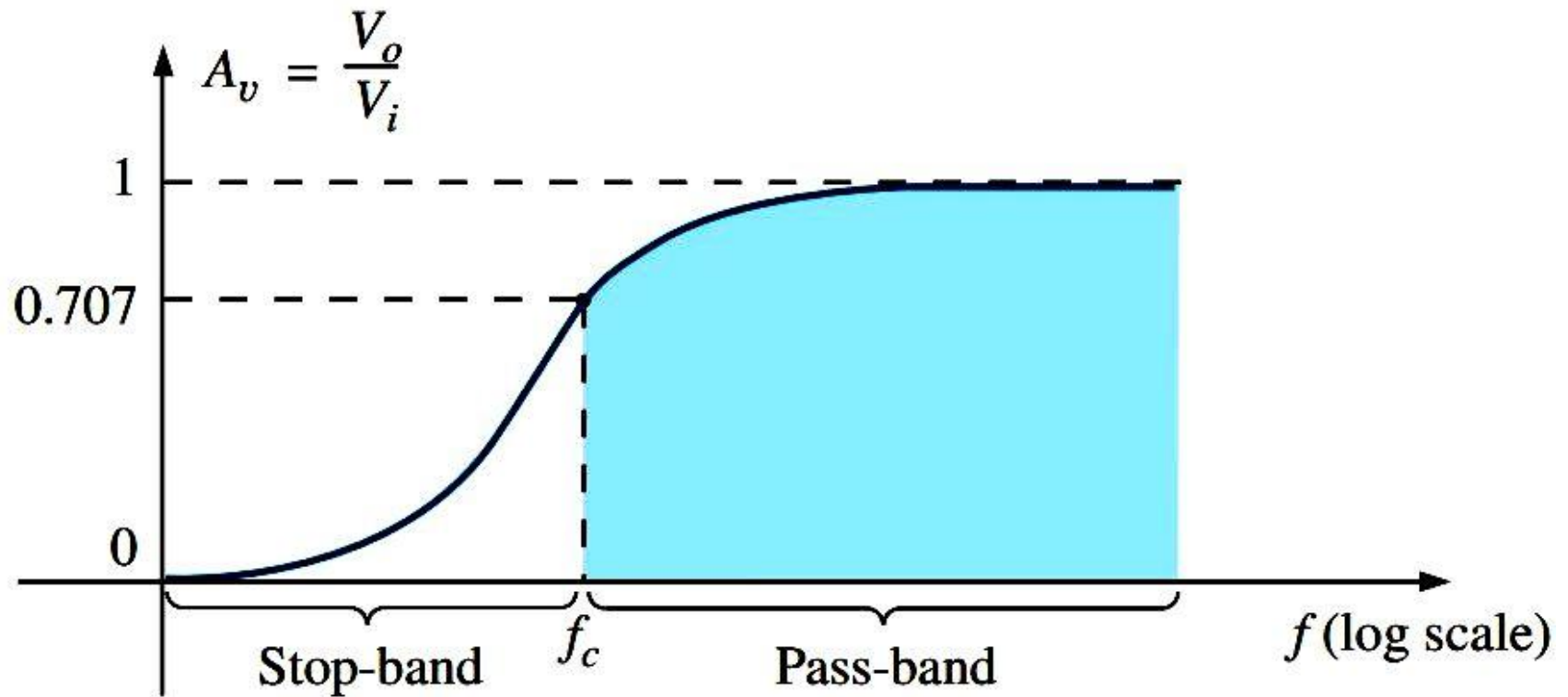

[sharafat.ali@ieee.org](mailto:sharafat.ali@ieee.org)



# R-C High Pass Filter

$$\mathbf{V}_o = \frac{R \angle 0^\circ \mathbf{V}_i}{R - j X_C}$$

$$\frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{R \angle 0^\circ}{R - j X_C} = \frac{R \angle 0^\circ}{\sqrt{R^2 + X_C^2} \angle -\tan^{-1}(X_C/R)}$$

$$\frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{R}{\sqrt{R^2 + X_C^2}} \angle \tan^{-1} (X_C/R)$$

[snaratat.all@ieee.org](mailto:snaratat.all@ieee.org)

# R-C High Pass Filter

$$A_v = \frac{V_o}{V_i} = \frac{R}{\sqrt{R^2 + X_C^2}} = \frac{1}{\sqrt{1 + \left(\frac{X_C}{R}\right)^2}}$$

$$\theta = \tan^{-1} \frac{X_C}{R}$$

[sharafat.ali@ieee.org](mailto:sharafat.ali@ieee.org)

# R-C High Pass Filter

For the frequency at which  $X_C = R$ , the magnitude becomes

$$\frac{V_o}{V_i} = \frac{1}{\sqrt{1 + \left(\frac{X_C}{R}\right)^2}} = \frac{1}{\sqrt{1 + 1}} = \frac{1}{\sqrt{2}} = 0.707$$

The frequency at which  $X_C = R$  is determined by

$$X_C = \frac{1}{2\pi f_c C} = R$$

$$f_c = \frac{1}{2\pi RC}$$

# R-C High Pass Filter

$$f_c = \frac{1}{2\pi RC}$$


For  $f < f_c$ ,  $V_o < 0.707V_i$

whereas for  $f > f_c$ ,  $V_o > 0.707V_i$

At  $f_c$ ,  $V_o$  leads  $V_i$  by  $45^\circ$

[sharafat.ali@ieee.org](mailto:sharafat.ali@ieee.org)

# R-C High Pass Filter

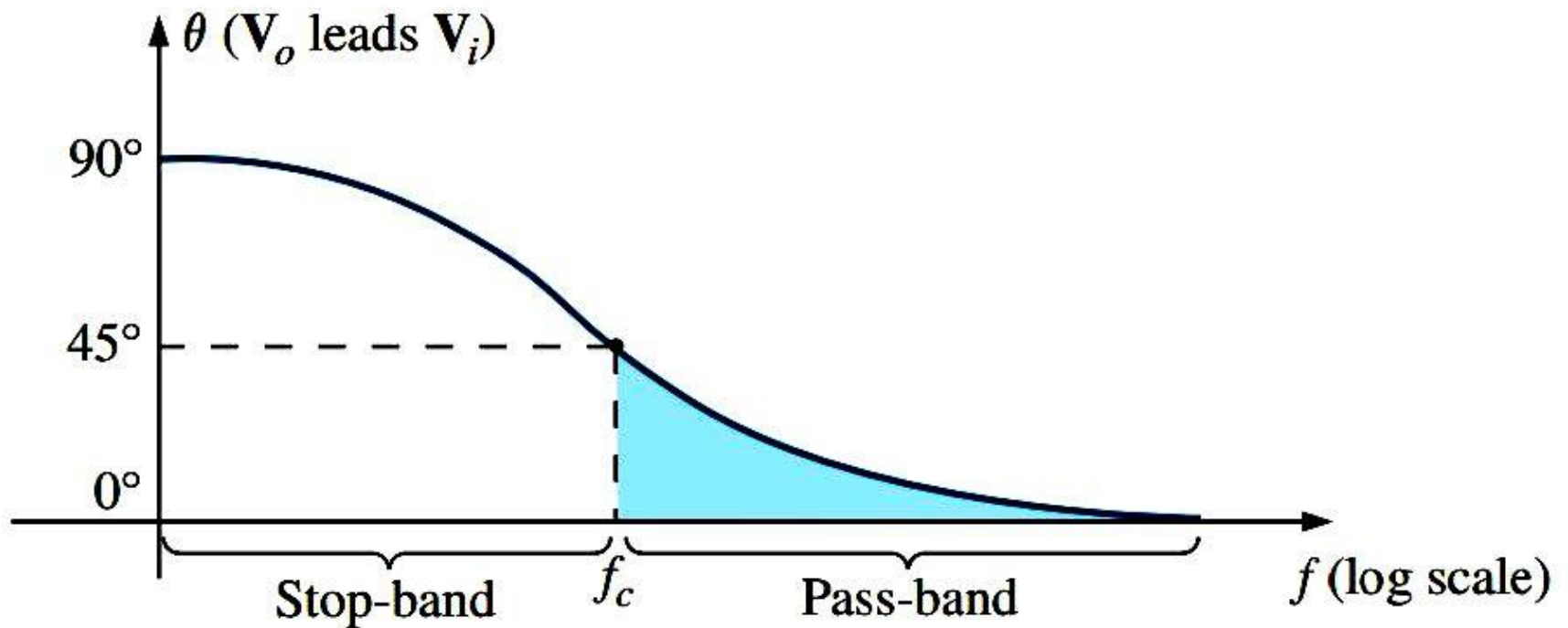

[sharafat.ali@ieee.org](mailto:sharafat.ali@ieee.org)

# R-C High Pass Filter

**EXAMPLE**      Given  $R = 20 \text{ k}\Omega$  and  $C = 1200 \text{ pF}$ :

- Sketch the normalized plot if the filter is used as both a high-pass and a low-pass filter.
- Sketch the phase plot for both filters in part (a).
- Determine the magnitude and phase of  $\mathbf{A}_v = \mathbf{V}_o/\mathbf{V}_i$  at  $f = \frac{1}{2}f_c$  for the high-pass filter.

sharafat.ali@ieee.org



# R-C High Pass Filter

$$\begin{aligned} \text{a. } f_c &= \frac{1}{2\pi RC} = \frac{1}{(2\pi)(20 \text{ k}\Omega)(1200 \text{ pF})} \\ &= \mathbf{6631.46 \text{ Hz}} \end{aligned}$$



The normalized plots appear in Fig. 1

b. The phase plots appear in Fig. 2



[sharafat.ali@ieee.org](mailto:sharafat.ali@ieee.org)



# R-C High Pass Filter

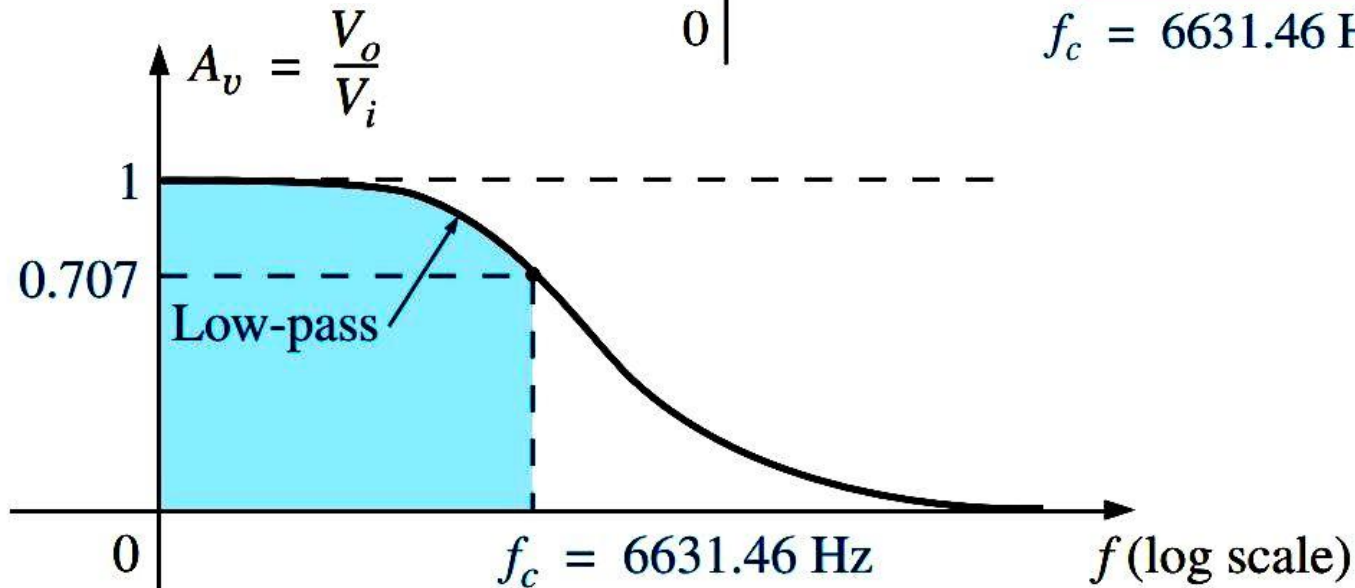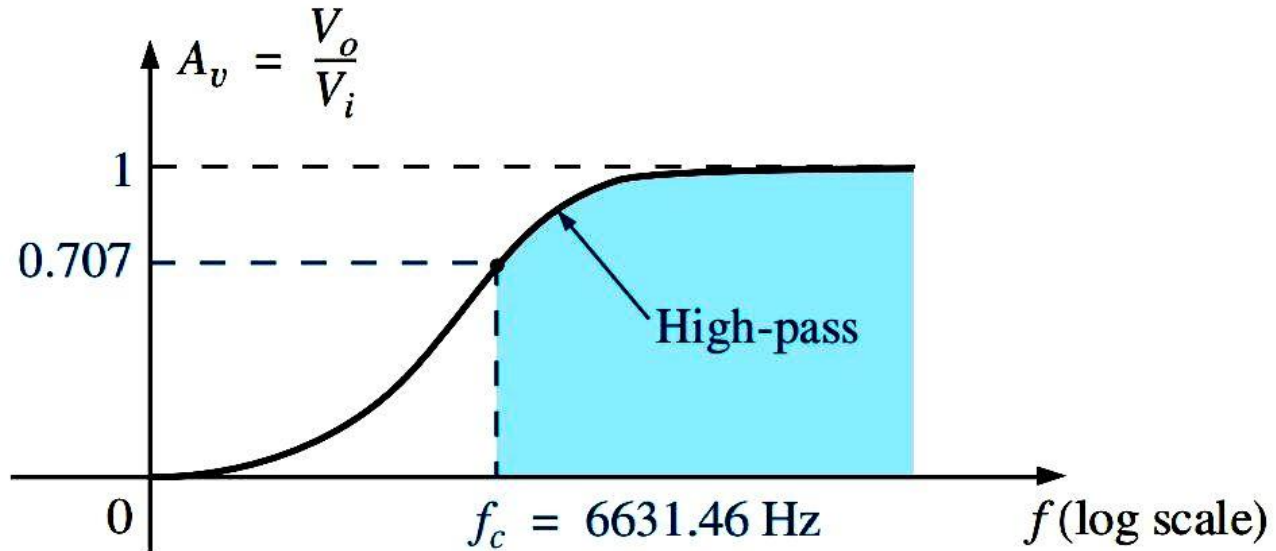

# R-C High Pass Filter

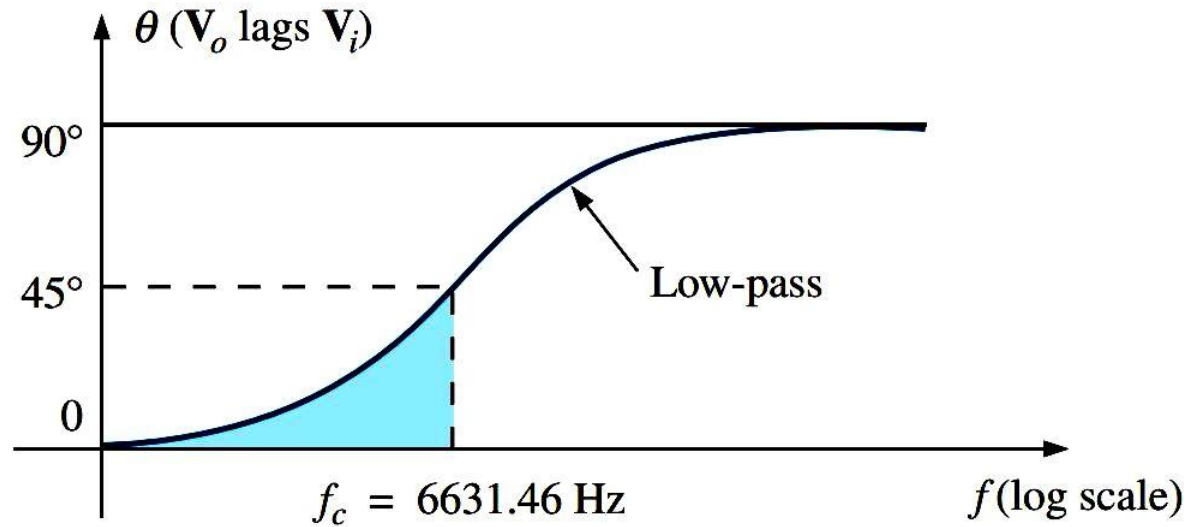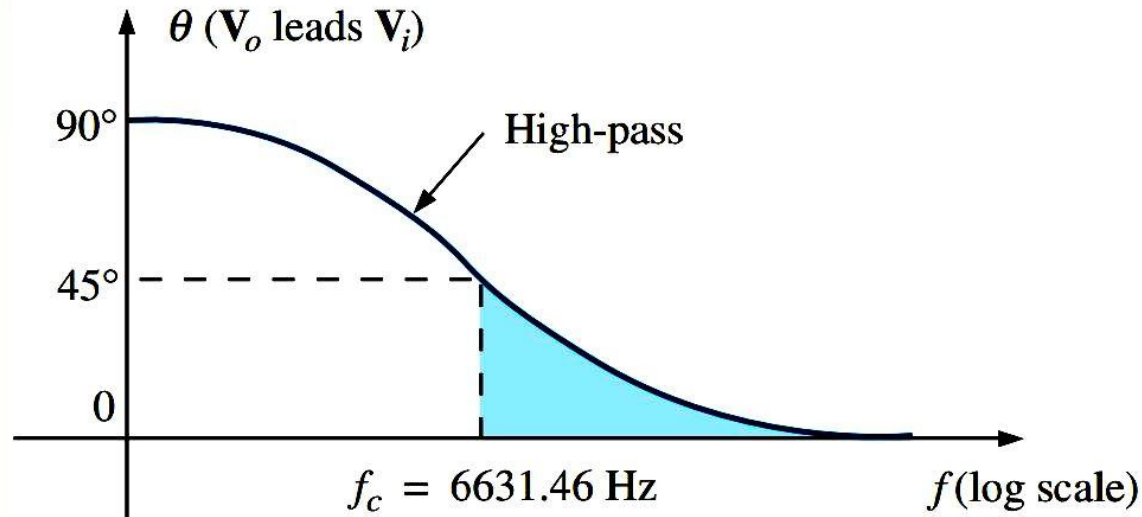

sharaf

# R-C High Pass Filter

$$\text{c. } f = \frac{1}{2} f_c = \frac{1}{2} (6631.46 \text{ Hz}) = 3315.73 \text{ Hz}$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{(2\pi)(3315.73 \text{ Hz})(1200 \text{ pF})}$$
$$\cong 40 \text{ k}\Omega$$

[sharafat.ali@ieee.org](mailto:sharafat.ali@ieee.org)

# R-C High Pass Filter

$$A_v = \frac{V_o}{V_i} = \frac{1}{\sqrt{1 + \left(\frac{X_C}{R}\right)^2}} = \frac{1}{\sqrt{1 + \left(\frac{40 \text{ k}\Omega}{20 \text{ k}\Omega}\right)^2}} = \frac{1}{\sqrt{1 + (2)^2}}$$
$$= \frac{1}{\sqrt{5}} = 0.4472$$


$$\theta = \tan^{-1} \frac{X_C}{R} = \tan^{-1} \frac{40 \text{ k}\Omega}{20 \text{ k}\Omega} = \tan^{-1} 2 = 63.43^\circ$$

and

$$\mathbf{A}_v = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \mathbf{0.447} \angle \mathbf{63.43^\circ}$$


[www.allaboutcircuits.org](http://www.allaboutcircuits.org)

# R-L High Pass Filter

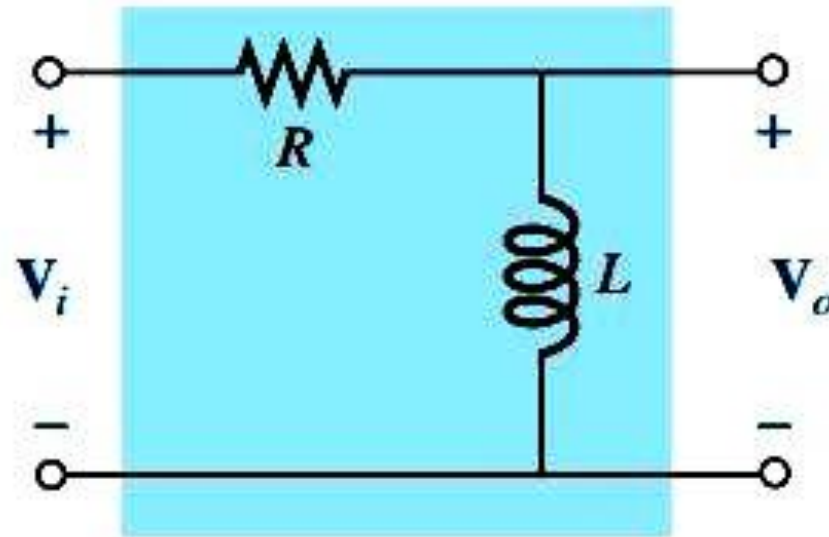


[sharafat.ali@ieee.org](mailto:sharafat.ali@ieee.org)

# Pass Band Filter

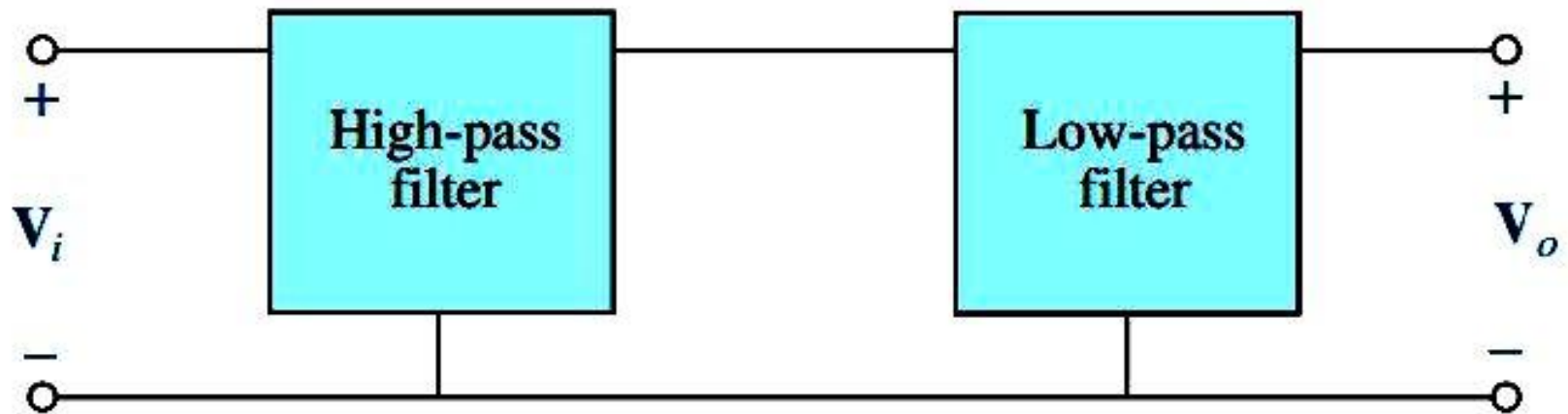

[sharafat.ali@ieee.org](mailto:sharafat.ali@ieee.org)


# Pass Band Filter

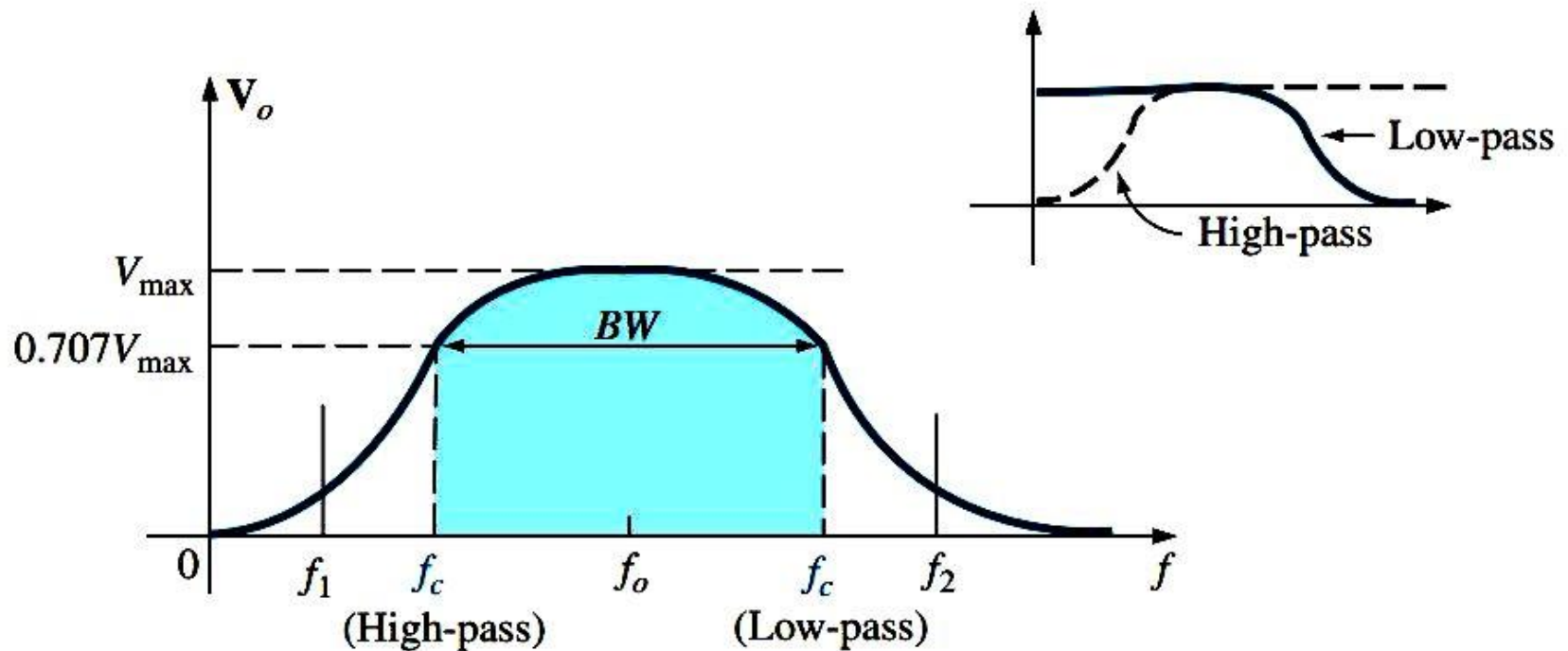

[sharafat.ali@ieee.org](mailto:sharafat.ali@ieee.org)



# Pass Band Filter

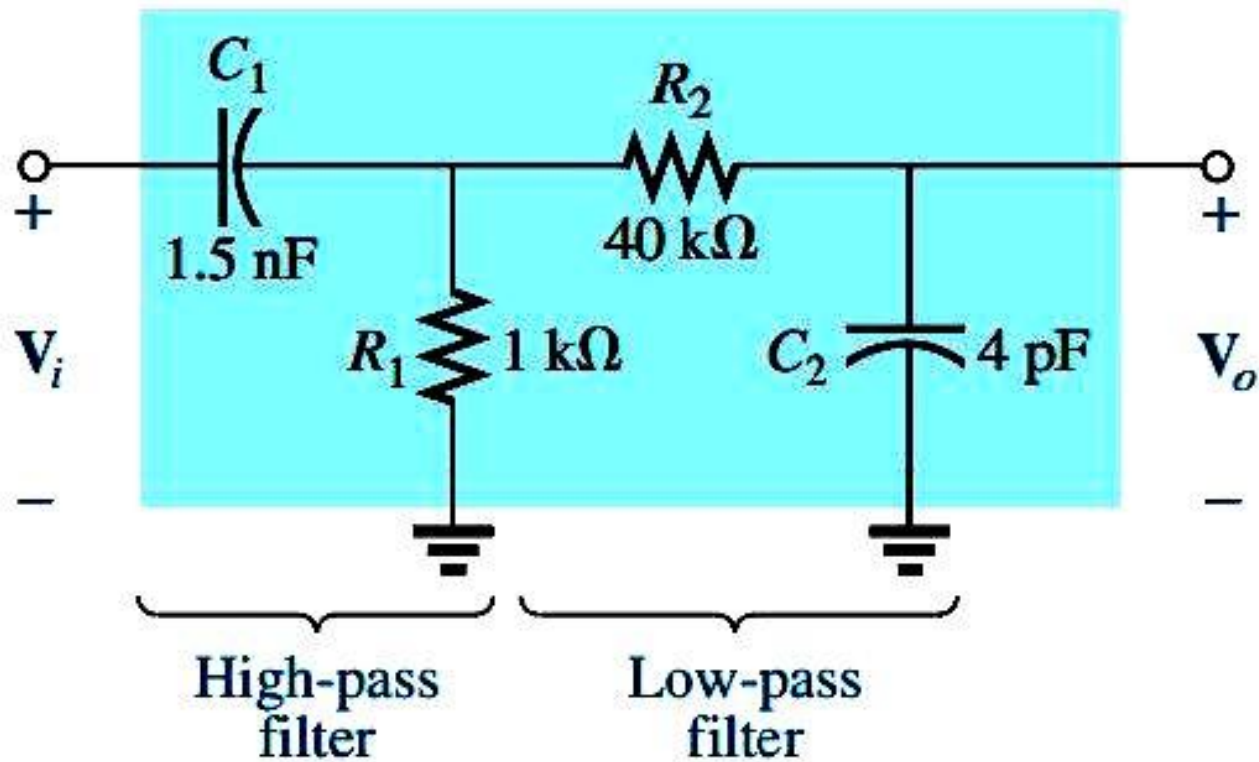


[sharatat.ali@ieee.org](mailto:sharatat.ali@ieee.org)

# Pass Band Filter
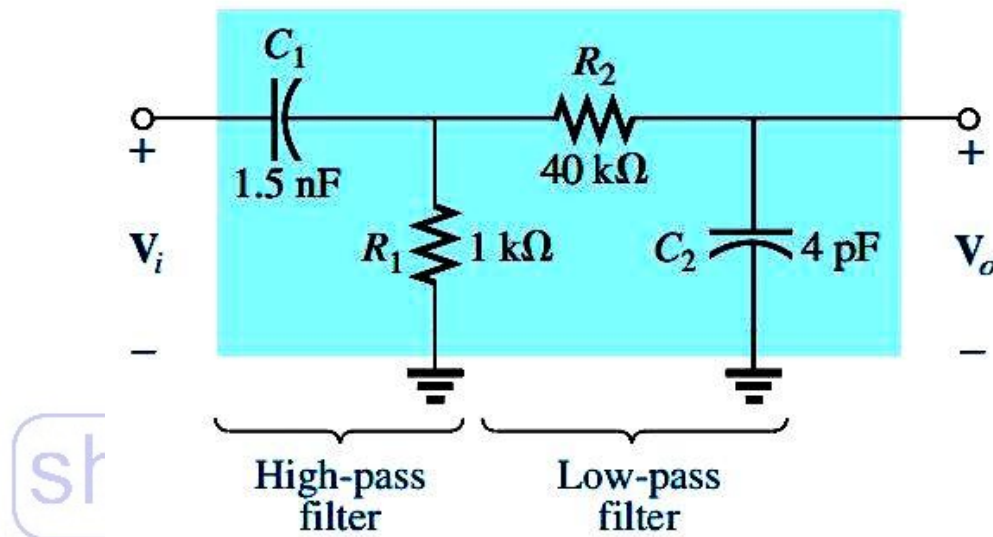
## EXAMPLE

For the pass-band filter in Fig.

- Determine the critical frequencies for the low- and high-pass filters.
- Using only the critical frequencies, sketch the response characteristics.
- Determine the actual value of  $V_o$  at the high-pass critical frequency calculated in part (a), and compare it to the level that defines the upper frequency for the pass-band.



# Pass Band Filter

a. High-pass filter:

$$f_c = \frac{1}{2\pi R_1 C_1} = \frac{1}{2\pi(1 \text{ k}\Omega)(1.5 \text{ nF})} = \mathbf{106.1 \text{ kHz}}$$


Low-pass filter:

$$f_c = \frac{1}{2\pi R_2 C_2} = \frac{1}{2\pi(40 \text{ k}\Omega)(4 \text{ pF})} = \mathbf{994.72 \text{ kHz}}$$

[sharafat.ali@ieee.org](mailto:sharafat.ali@ieee.org)

# Pass Band Filter

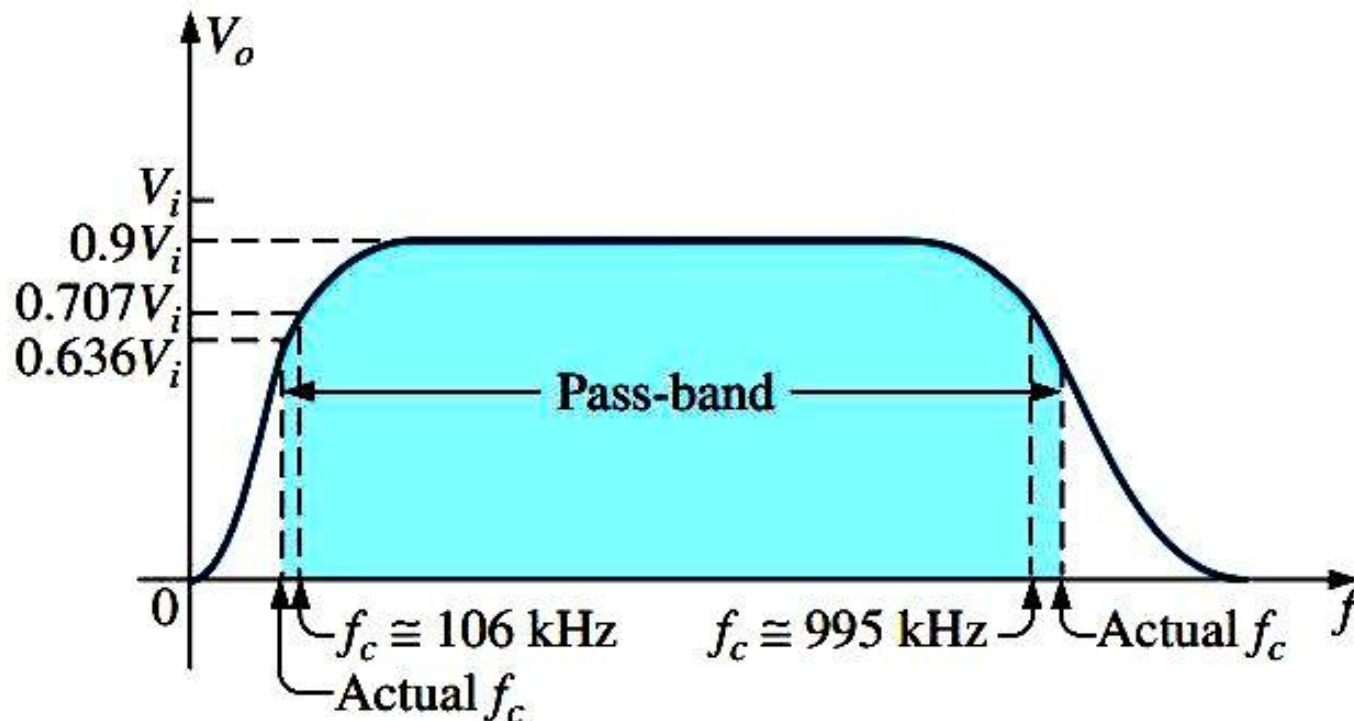- b. In the mid-region of the pass-band at about 500 kHz, an analysis of the network reveals that  $V_o \cong 0.9V_i$  as shown in Fig. bandwidth is therefore defined at a level of  $0.707(0.9V_i) = 0.636V_i$  as also shown in Fig.



c. At  $f = 994.72$  kHz,

$$X_{C_1} = \frac{1}{2\pi f C_1} \cong 107 \Omega$$

and 
$$X_{C_2} = \frac{1}{2\pi f C_2} = R_2 = 40 \text{ k}\Omega$$


resulting in the network in Fig.

The parallel combination  $R_1 \parallel (R_2 - jX_{C_2})$  is essentially  $0.976 \text{ k}\Omega \angle 0^\circ$  because the  $R_2 - X_{C_2}$  combination is so large compared to the parallel resistor  $R_1$ .

[snaratat.all@ieee.org](mailto:snaratat.all@ieee.org)



# Pass Band Filter

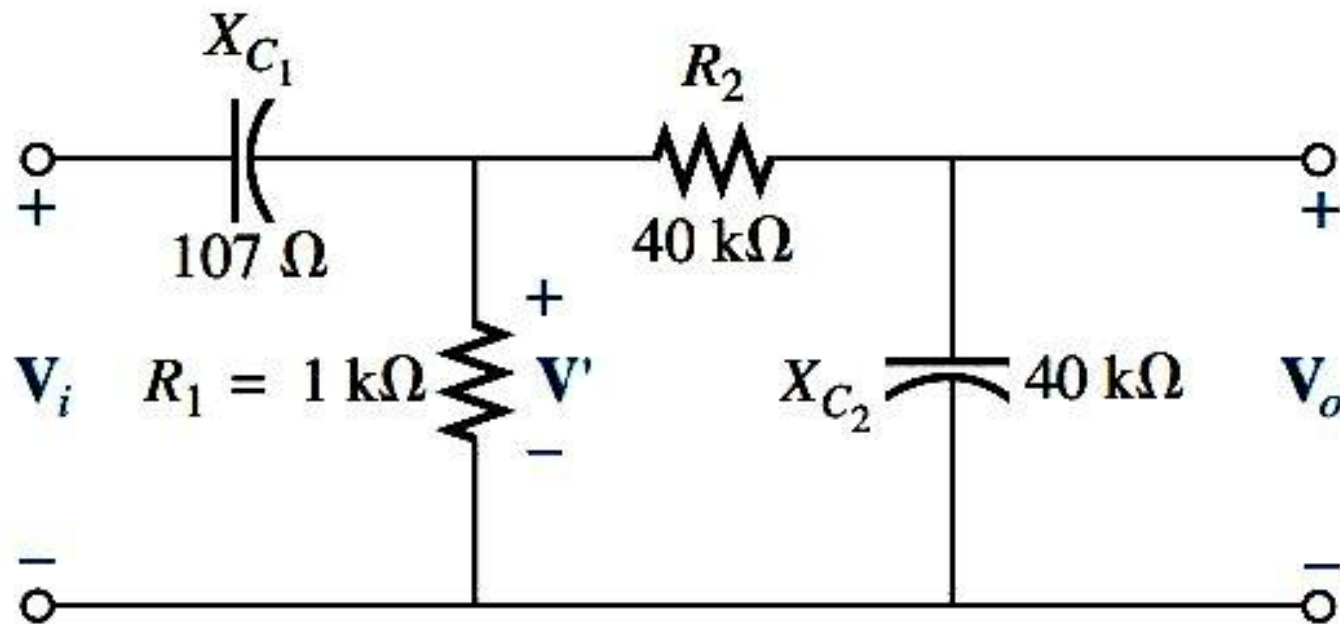

[sharafat.ali@ieee.org](mailto:sharafat.ali@ieee.org)

# Pass Band Filter

$$\mathbf{V}' = \frac{0.976 \text{ k}\Omega \angle 0^\circ (\mathbf{V}_i)}{0.976 \text{ k}\Omega - j0.107 \text{ k}\Omega} \cong 0.994 \mathbf{V}_i \angle 6.26^\circ$$

with

$$\mathbf{V}_o = \frac{(40 \text{ k}\Omega \angle -90^\circ)(0.994 \mathbf{V}_i \angle 6.26^\circ)}{40 \text{ k}\Omega - j40 \text{ k}\Omega}$$

$$\mathbf{V}_o \cong 0.703 \mathbf{V}_i \angle -39^\circ$$

so that




$$V_o \cong \mathbf{0.703V}_i \quad \text{at } f = 994.72 \text{ kHz}$$

Since the bandwidth is defined at  $0.636V_i$  the upper cutoff frequency will be higher than 994.72 kHz as shown in Fig.



# Pass Band Filter

Series Resonant Circuit,  $X_L = X_C$

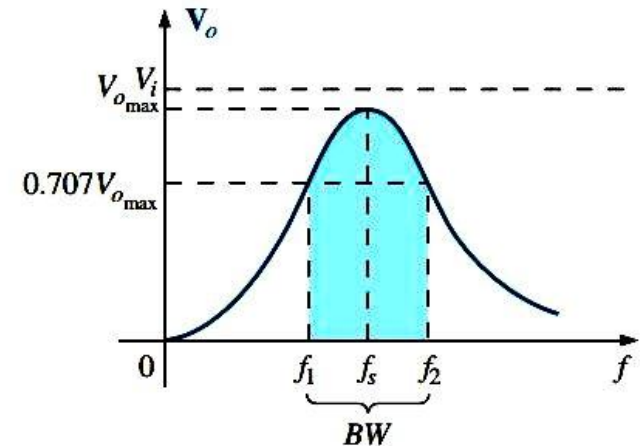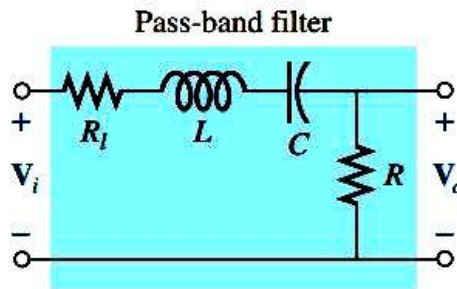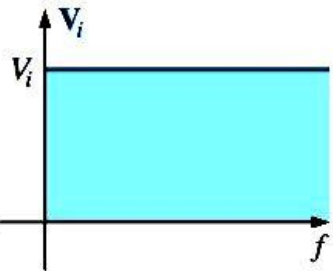

sharafat.ali@ieee.org

# Pass Band Filter

Series Resonant Circuit,

$$X_L = X_C$$

$$V_{o_{\max}} = \frac{R}{R + R_l} V_i \quad f = f_s$$

$$f_s = \frac{1}{2\pi\sqrt{LC}}$$




$$Q_s = \frac{X_L}{R + R_l}$$

$$BW = \frac{f_s}{Q_s}$$

sharafat.ali@

# Pass Band Filter

Parallel Resonant Circuit,  $X_L = X_C$

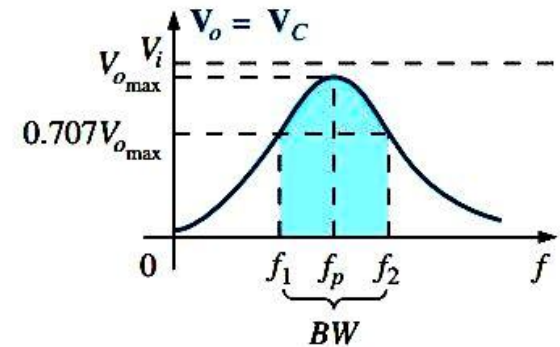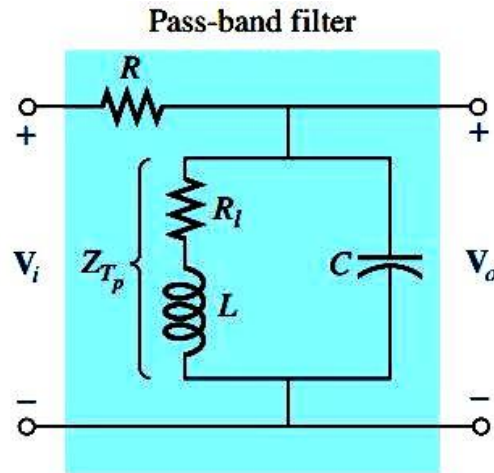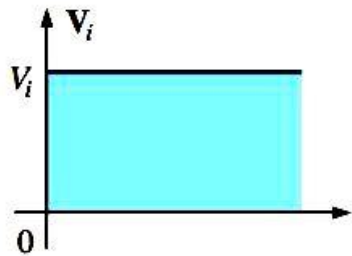

sharafat.ali@ieee.org

# Pass Band Filter

Parallel Resonant Circuit,  $X_L = X_C$

$$V_{o_{\max}} = \frac{Z_{T_p} V_i}{Z_{T_p} + R} \quad f = f_p$$

$$Q_p = \frac{X_L}{R_l}$$


$$Z_{T_p} = Q_l^2 R_l \quad Q_l \geq 10$$

$$BW = \frac{f_p}{Q_p}$$

$$f_p = \frac{1}{2\pi\sqrt{LC}} \quad Q_l \geq 10$$


[sharafat.ali@ieee.org](mailto:sharafat.ali@ieee.org)

# Stop Band Filter

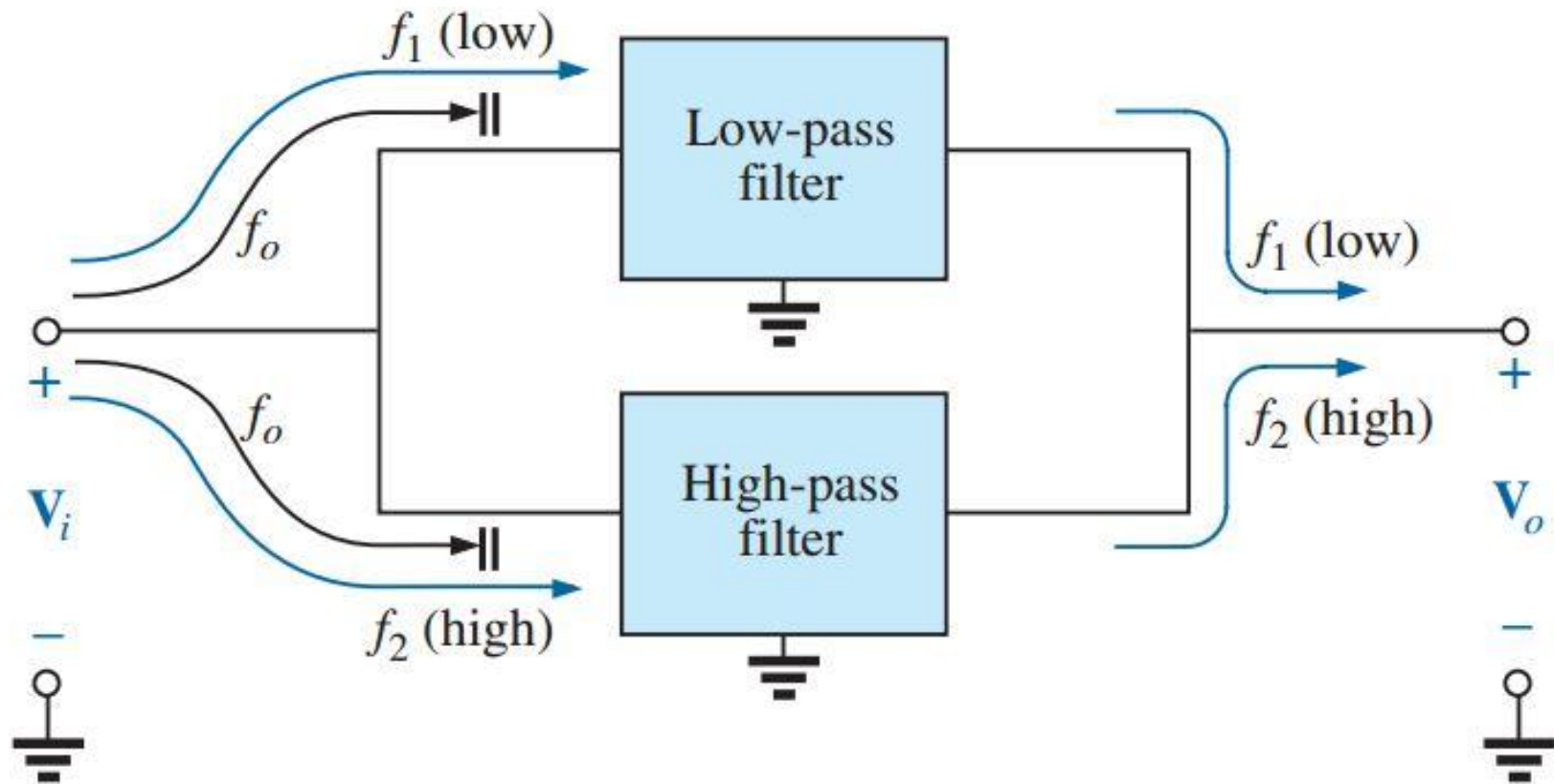


[snaratat.all@ieee.org](mailto:snaratat.all@ieee.org)

# Stop Band Filter

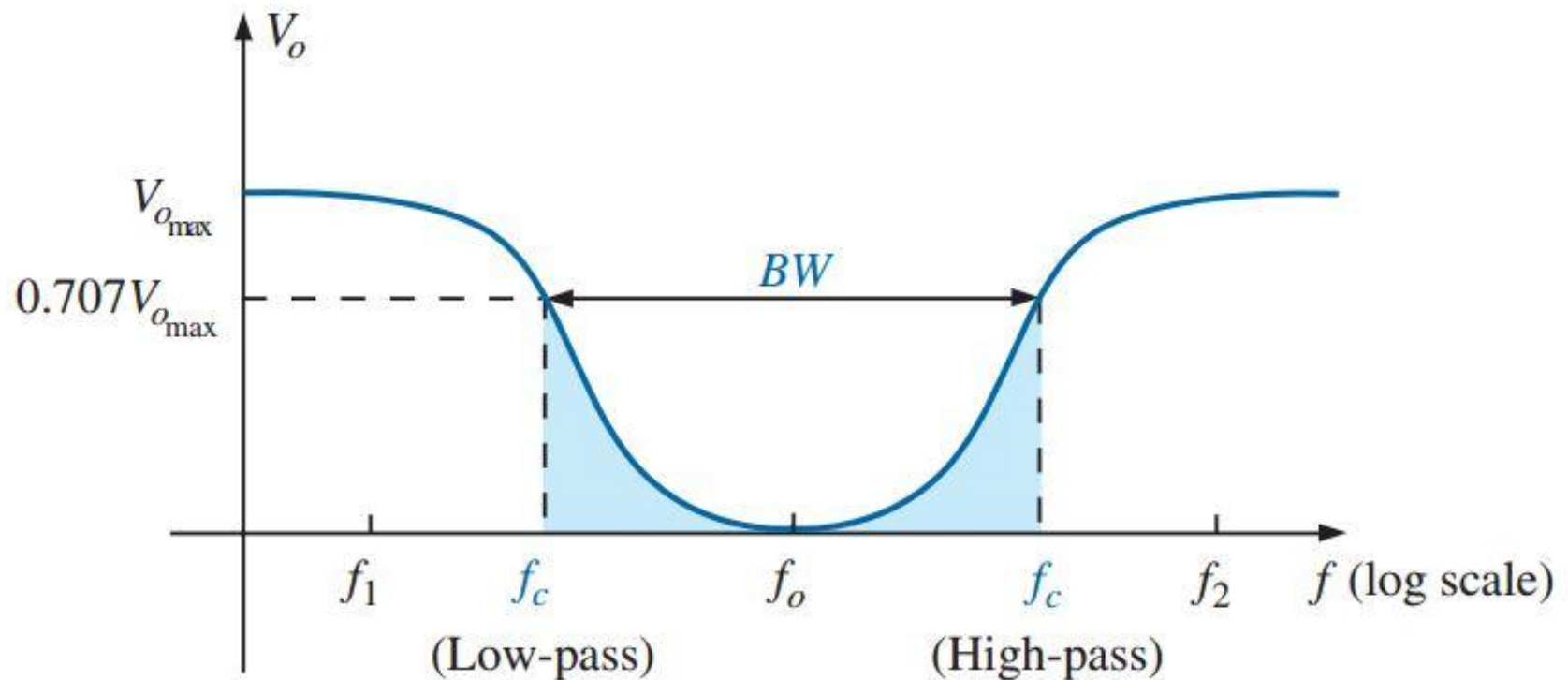

[sharafat.ali@ieee.org](mailto:sharafat.ali@ieee.org)


# Stop Band Filter

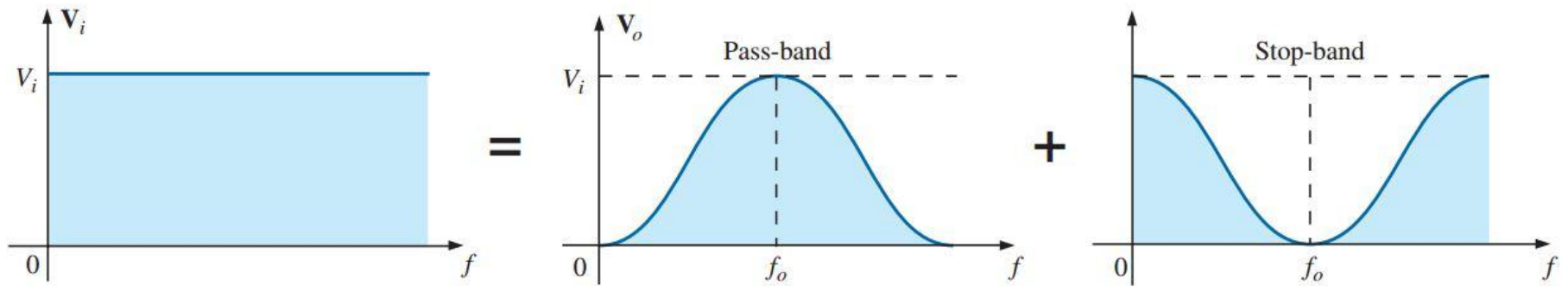

sharafat.ali@ieee.org



# Stop Band Filter

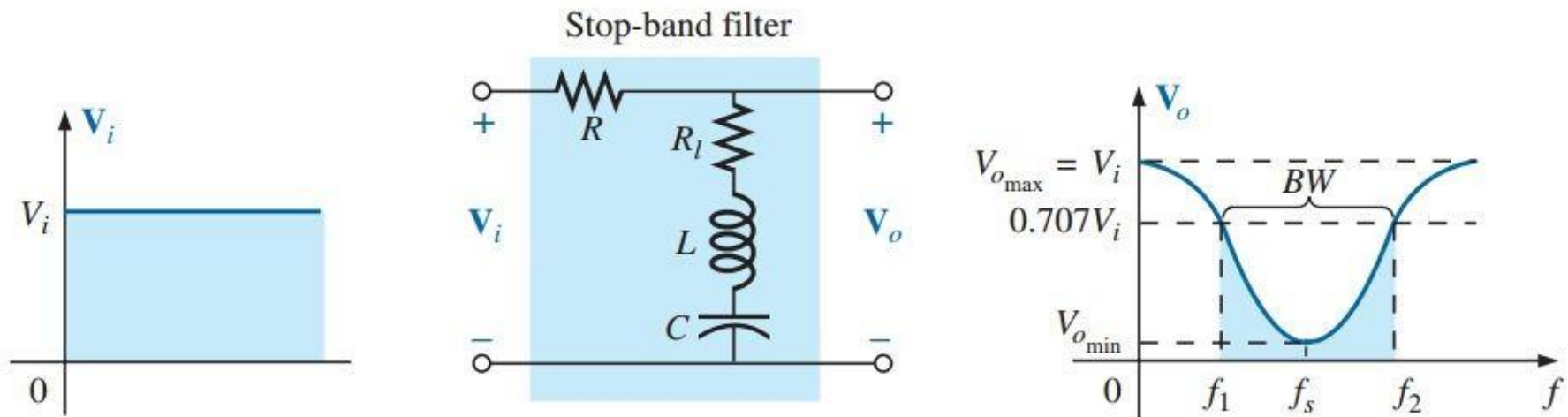


*Stop-band filter using a series resonant circuit.*

$$V_{o\min} = \frac{R_l V_i}{R_l + R}$$

sharaf

.org

# Stop Band Filter

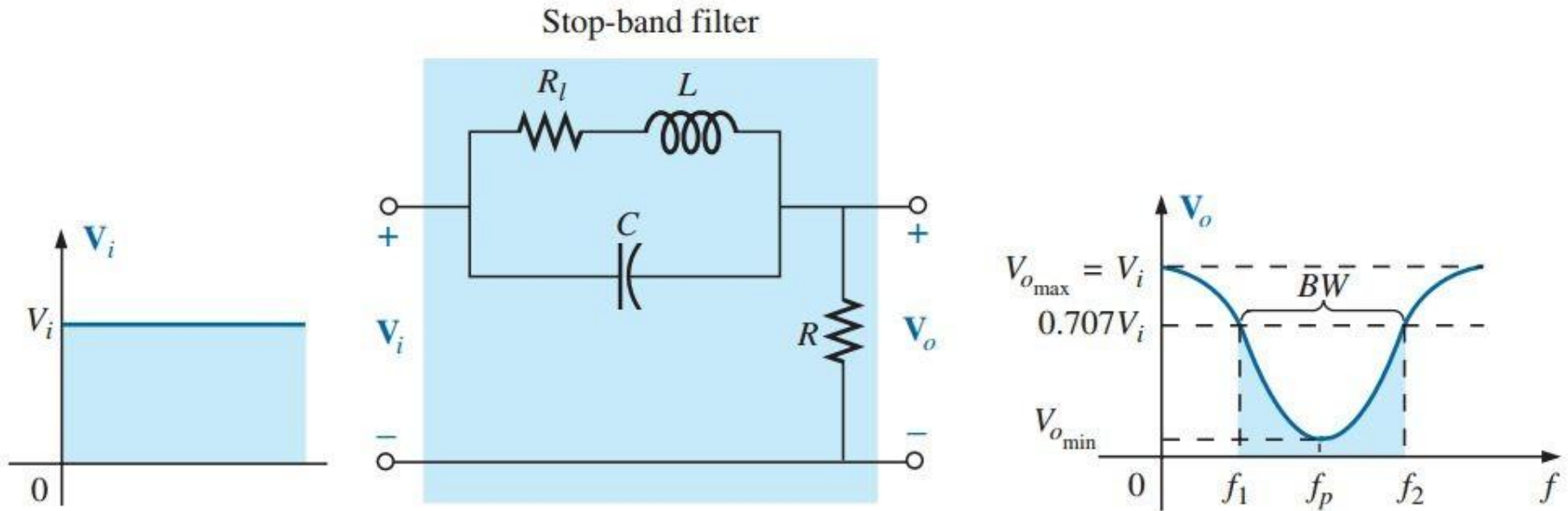

*Stop-band filter using a parallel resonant network.*

$$V_{o\min} = \frac{RV_i}{R + Z_{T_p}}$$

sharafa

.org

# ASSIGNMENT – 2

## EXAMPLE 21.8

- Determine the frequency response for the voltage  $V_o$  for the series circuit in Fig. 21.35.
- Plot the normalized response  $A_v = V_o/V_i$ .
- Plot a normalized response defined by  $A'_v = A_v/A_{v_{\max}}$ .

