

Experiment Name: Implementation of Carry
Look Ahead Adder.

Roll: 1710776121

Session: 2016-17

Course: CSE-2112


Date: 23-04-2018

Experiment: Implementation of Carry Look Ahead Adder.

Theory: Carry Look Ahead Adder is another type of adder. In normal adder when we want to add two numbers of many digits we face there a problem that the carry is not proper. Because there is a large gate delay in the carry. To reduce this problem we use carry look ahead adder. In this adder all carry from individual full adder is counted at a time. So it reduce the gate delay.

Instruments: wire, breadboard, power source and adder IC.

Circuit:

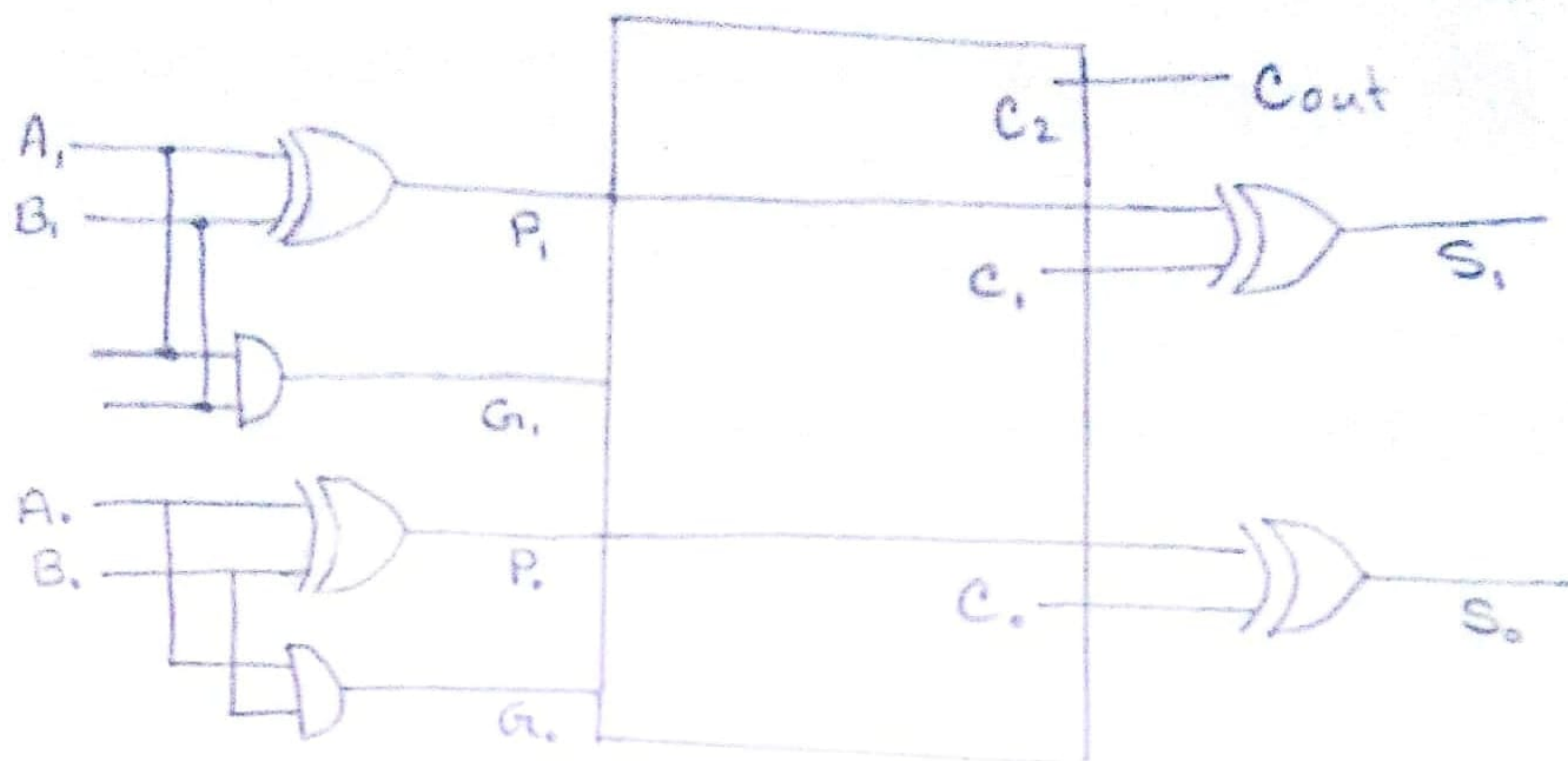

$$\left. \begin{aligned} P_i &= A_i \oplus B_i \\ G_i &= A_i \cdot B_i \end{aligned} \right\} \text{where } i = 0, 1 \text{ etc.}$$

$$S_0 = P_0 \oplus C_0$$

$$S_1 = P_1 \oplus C_1$$

Truth Table:

A_1	B_1	A_0	B_0	C_{out}	S_1	S_0
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	1	0
0	1	0	0	0	1	0
0	1	0	1	0	1	1
0	1	1	0	1	0	0
0	1	1	1	1	0	1
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	1	0	1
1	1	0	1	1	0	0
1	1	1	0	1	1	0
1	1	1	1	1	1	1

Result and Discussion: From circuit drawn we have designed the circuit. The result we get is similar to equivalent addition result for each value of A and B. So the circuit and equations are right.

Pre-caution:

1. Connect the circuit when design is complete.
2. Please check the circuit before connecting.
3. Wear shoes in the lab.
4. After finishing experiment switch off the power source.