


Computer Organization

- Computer design as an application of digital logic design procedures
- Computer = processing unit + memory system
- Processing unit = control + datapath
- Control = finite state machine
 - Inputs = machine instruction, datapath conditions
 - Outputs = register transfer control signals, ALU operation codes
 - Instruction interpretation = instruction fetch, decode, execute
- Datapath = functional units + registers
 - Functional units = ALU, multipliers, dividers, etc.
 - Registers = program counter, shifters, storage registers



CS 150 – Fall 2005 – Lec 13: Computer Org I - 1

Tri-State Buffers

- 0, 1, Z (high impedance state)

 


if OE then Out = In
else "disconnected"

  


Inverting Buffer

CS 150 – Fall 2005 – Lec 13: Computer Org I - 2

Tri-States vs. Mux

 


 Buffer circuits simple!
Scales nicely for high fan-in
and wide bit widths!



Scales poorly for high fan-in
or wide bit widths

Register Transfer

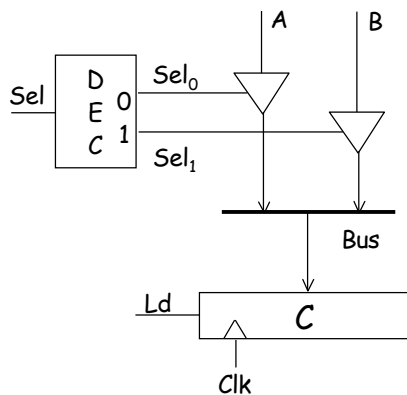


$C \leftarrow A$


$Sel \leftarrow 0; Ld \leftarrow 1$

$C \leftarrow B$

$Sel \leftarrow 1; Ld \leftarrow 1$

 


Open Collector Concept

 

Bad! Short circuit!

Low resistance path from
Vdd to Gnd

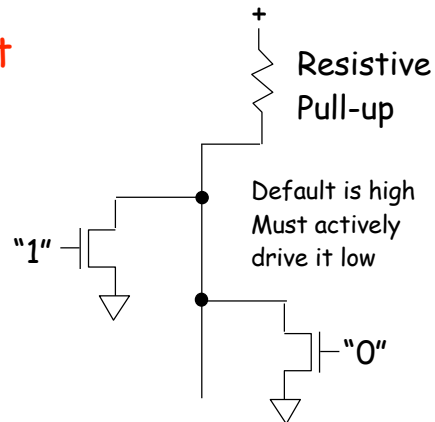


Wired AND Configuration:

If *any* attached device wants
wire to be "0", it wins

If *all* attached devices want
wire to be "1", it is


Structure of a Computer

■ Block diagram view

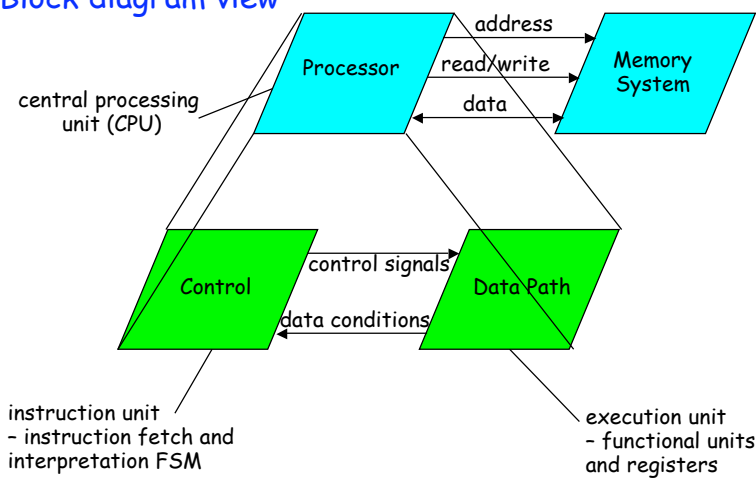

Registers

 - Selectively loaded - EN or LD input
- Output enable - OE input
- Multiple registers - group 4 or 8 in parallel




OE asserted causes FF state to be connected to output pins; otherwise they are left unconnected (high impedance)

LD asserted during a lo-to-hi clock transition loads new data into FFs


Register Transfer

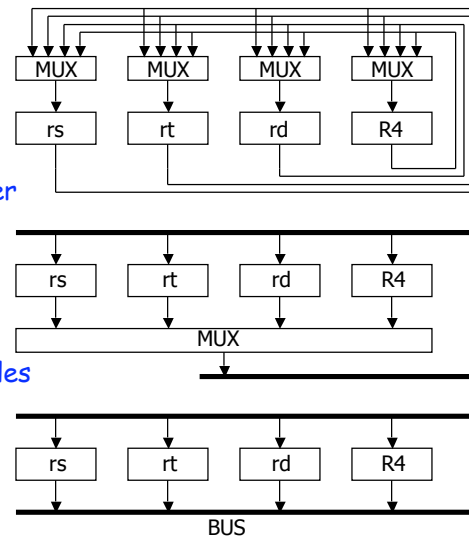- Point-to-point connection
 - Dedicated wires
 - Muxes on inputs of each register
- Common input from multiplexer
 - Load enables for each register
 - Control signals for multiplexer
- Common bus with output enables
 - Output enables and load enables for each register



Register Files


- Collections of registers in one package
 - Two-dimensional array of FFs
 - Address used as index to a particular word
 - Separate read and write addresses so can do both at same time
- 4 by 4 register file
 - 16 D-FFs
 - Organized as four words of four bits each
 - Write-enable (load)
 - Read-enable (output enable)

 

CS 150 – Fall 2005 – Lec 13: Computer Org I - 9

Memories

- Larger Collections of Storage Elements
 - Implemented not as FFs but as much more efficient latches
 - High-density memories use 1-5 switches (transistors) per bit
- Static RAM - 1024 words each 4 bits wide
 - Once written, memory holds forever (not true for denser dynamic RAM)
 - Address lines to select word (10 lines for 1024 words)
 - Read enable
 - Same as output enable
 - Often called chip select
 - Permits connection of many chips into larger array
 - Write enable (same as load enable)
 - Bi-directional data lines
 - output when reading, input when writing

 

CS 150 – Fall 2005 – Lec 13: Computer Org I - 10

Instruction Sequencing

- Example - an instruction to add the contents of two registers (Rx and Ry) and place result in a third register (Rz)
- Step 1: Get the ADD instruction from memory into an instruction register
- Step 2: Decode instruction
 - Instruction in IR has the code of an ADD instruction
 - Register indices used to generate output enables for registers Rx and Ry
 - Register index used to generate load signal for register Rz
- Step 3: Execute instruction
 - Enable Rx and Ry output and direct to ALU
 - Setup ALU to perform ADD operation
 - Direct result to Rz so that it can be loaded into register

CS 150 – Fall 2005 – Lec 13: Computer Org I - 11

Instruction Types

- Data Manipulation
 - Add, subtract
 - Increment, decrement
 - Multiply
 - Shift, rotate
 - Immediate operands
- Data Staging
 - Load/store data to/from memory
 - Register-to-register move
- Control
 - Conditional/unconditional branches in program flow
 - Subroutine call and return

CS 150 – Fall 2005 – Lec 13: Computer Org I - 12

Elements of the Control Unit (aka Instruction Unit)

■ Standard FSM Elements

- State register
- Next-state logic
- Output logic (datapath/control signaling)
- Moore or synchronous Mealy machine to avoid loops unbroken by FF

■ Plus Additional "Control" Registers

- Instruction register (IR)
- Program counter (PC)

■ Inputs/Outputs

- Outputs control elements of data path
- Inputs from data path used to alter flow of program (test if zero)

CS 150 – Fall 2005 – Lec 13: Computer Org I - 13

Instruction Execution


■ Control State Diagram (for each diagram)

- Reset
- Fetch instruction
- Decode
- Execute

■ Instructions partitioned into three classes

- Branch
- Load/store
- Register-to-register

■ Different sequence through diagram for each instruction type

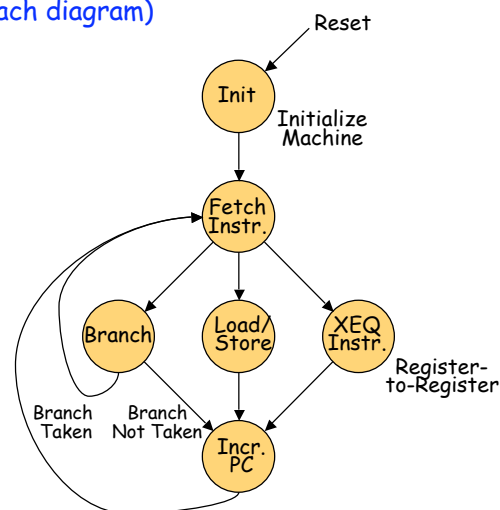


CS 150 – Fall 2005 – Lec 13: Computer Org I - 14

Data Path (Hierarchy)

■ Arithmetic circuits constructed in hierarchical and iterative fashion

- Each bit in datapath is functionally identical
- 4-bit, 8-bit, 16-bit, 32-bit datapaths

 


CS 150 – Fall 2005 – Lec 13: Computer Org I - 15

Data Path (ALU)

■ ALU Block Diagram


- Input: data and operation to perform
- Output: result of operation and status information

 

CS 150 – Fall 2005 – Lec 13: Computer Org I - 16

Data Path (ALU + Registers)


- Accumulator
 - Special register
 - One of the inputs to ALU
 - Output of ALU stored back in accumulator
- One-address instructions
 - Operation and address of one operand
 - Other operand and destination is accumulator register
 - $AC \leftarrow AC \text{ op Mem}[\text{addr}]$
 - "Single address instructions" (AC implicit operand)
- Multiple registers
 - Part of instruction used to choose register operands

 

CS 150 – Fall 2005 – Lec 13: Computer Org I - 17

Data Path (Bit-slice)

- Bit-slice concept: iterate to build n-bit wide datapaths

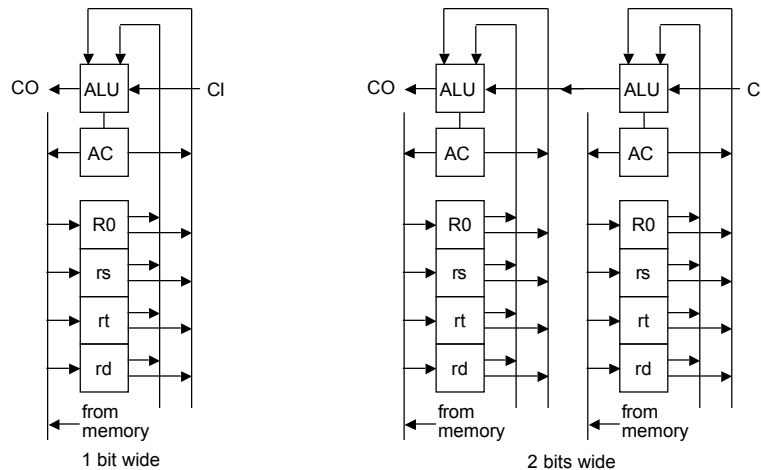

CS 150 – Fall 2005 – Lec 13: Computer Org I - 18

Announcements

- Quizzes: Good news and bad news!
- Additional readings on-line: CLD 1ed Chapters 11, 12
- Lab Checkpoints and Project
 - Project is a marathon, not a sprint
 - Not as completely specified or as straightforward as the labs: creativity, team work as well as technical skill required
 - Do NOT fall behind ... schedule may appear to look slack, but it probably won't be possible to catch up if you fall behind
 - Partner problems: Keep us informed! Don't let it fester!
 - Keep up with your TA design reviews. This is really important! Take them seriously!

CS 150 – Fall 2005 – Lec 13: Computer Org I - 19

Announcements

- After HW #6, length of hws will decrease ...
- HW #5, Q2 Re-revised specification (reposted to web):
 - N-S: Green Arrow 16, Yellow Arrow 8, Red 88, Green 24, Yellow 8 (NOTE: Red overlaps Green and Yellow Arrows for 24 seconds, leaving 64 seconds with the arrows off but the Red light on)
 - E-W: Red 56, Green 56, Yellow 8
 - Suppose each column represents an 8 second interval:

N-S

GA GA YA RA RA RA RA RA RA RA RA RA RA RA RA
R R R G G G Y R R R R R R R R R

E-W

R R R R R R R G G G G G G G Y

CS 150 – Fall 2005 – Lec 13: Computer Org I - 20

Instruction Path

- Program Counter
 - | Keeps track of program execution
 - | Address of next instruction to read from memory
 - | May have auto-increment feature or use ALU
- Instruction Register
 - | Current instruction
 - | Includes ALU operation and address of operand
 - | Also holds target of jump instruction
 - | Immediate operands
- Relationship to Data Path
 - | PC may be incremented through ALU
 - | Contents of IR may also be required as input to ALU

CS 150 – Fall 2005 – Lec 13: Computer Org I - 21

Data Path (Memory Interface)


- Memory
 - | Separate data and instruction memory (Harvard architecture)
 - | Two address busses, two data busses
 - | Single combined memory (Princeton architecture)
 - | Single address bus, single data bus
- Separate memory
 - | ALU output goes to data memory input
 - | Register input from data memory output
 - | Data memory address from instruction register
 - | Instruction register from instruction memory output
 - | Instruction memory address from program counter
- Single memory
 - | Address from PC or IR
 - | Memory output to instruction and data registers
 - | Memory input from ALU output

CS 150 – Fall 2005 – Lec 13: Computer Org I - 22

Block Diagram of Processor

■ Register Transfer View of Princeton Architecture

- Which register outputs are connected to which register inputs
- Arrows represent data-flow, other are control signals from control FSM
- MAR may be a simple multiplexer rather than separate register
- MBR is split in two (REG and IR)
- Load control for each register

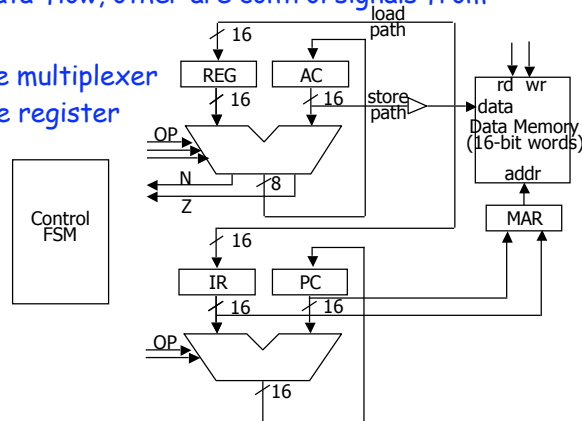


CS 150 – Fall 2005 – Lec 13: Computer Org I - 23

Block Diagram of Processor

■ Register transfer view of Harvard architecture

- Which register outputs are connected to which register inputs
- Arrows represent data-flow, other are control signals from control FSM
- Two MARs (PC and IR)
- Two MBRs (REG and IR)
- Load control for each register

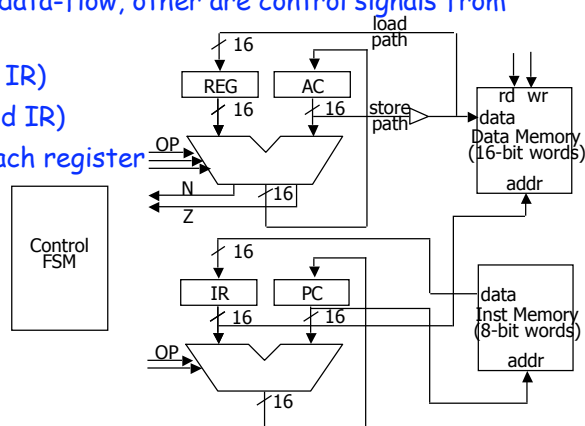


CS 150 – Fall 2005 – Lec 13: Computer Org I - 24

A Simplified Processor Data-path and Memory

- Princeton architecture
- Register file
- Instruction register
- PC incremented through ALU
- Modeled after MIPS rt000 (used in 61C textbook by Patterson & Hennessy)
 - Really a 32 bit machine
 - We'll do a 16 bit version


memory has only 255 words with a display on the last one

 

CS 150 – Fall 2005 – Lec 13: Computer Org I - 25

Processor Control

- Synchronous Mealy machine
- Multiple cycles per instruction

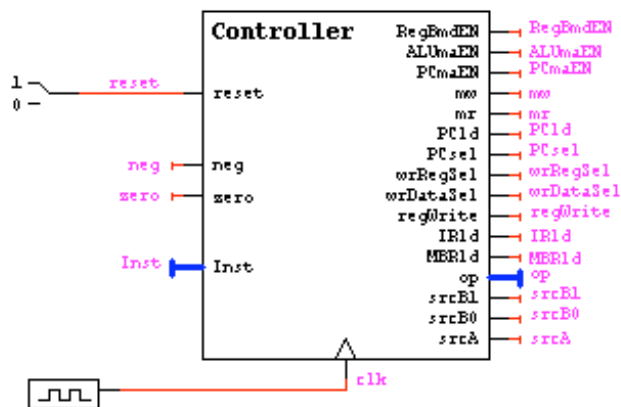

CS 150 – Fall 2005 – Lec 13: Computer Org I - 26

Processor Instructions

- Three principal types (16 bits in each instruction)

type	op	rs	rt	rd	funct
R(egister)	3	3	3	3	4
I(mmediate)	3	3	3	7	
J(ump)	3	13			

- Some of the instructions

R	add	0	rs	rt	rd	0	rd = rs + rt
	sub	0	rs	rt	rd	1	rd = rs - rt
	and	0	rs	rt	rd	2	rd = rs & rt
	or	0	rs	rt	rd	3	rd = rs rt
	slt	0	rs	rt	rd	4	rd = (rs < rt)
I	lw	1	rs	rt	offset		rt = mem[rs + offset]
	sw	2	rs	rt	offset		mem[rs + offset] = rt
	beq	3	rs	rt	offset		pc = pc + offset, if (rs == rt)
	addi	4	rs	rt	offset		rt = rs + offset
J	j	5	target address				pc = target address
	halt	7	-				stop execution until reset

CS 150 – Fall 2005 – Lec 13: Computer Org I - 27

Tracing an Instruction's Execution

- Instruction: $r3 = r1 + r2$


R	0	rs=r1	rt=r2	rd=r3	funct=0
---	---	-------	-------	-------	---------

- 1. Instruction fetch
 - Move instruction address from PC to memory address bus
 - Assert memory read
 - Move data from memory data bus into IR
 - Configure ALU to add 1 to PC
 - Configure PC to store new value from ALUout
- 2. Instruction decode
 - Op-code bits of IR are input to control FSM
 - Rest of IR bits encode the operand addresses (rs and rt)
 - These go to register file

CS 150 – Fall 2005 – Lec 13: Computer Org I - 28

Tracing an Instruction's Execution (cont'd)


Step 2

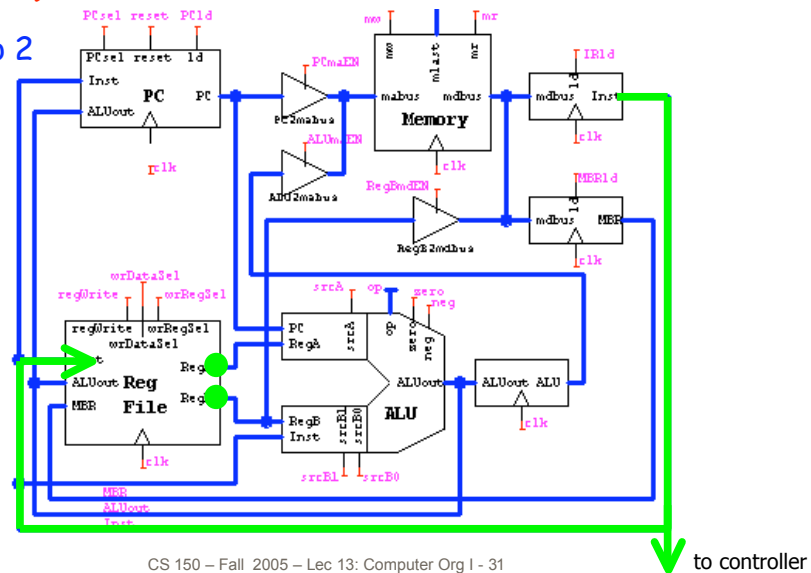

CS 150 – Fall 2005 – Lec 13: Computer Org I - 31

Tracing an Instruction's Execution (cont'd)

Step 3

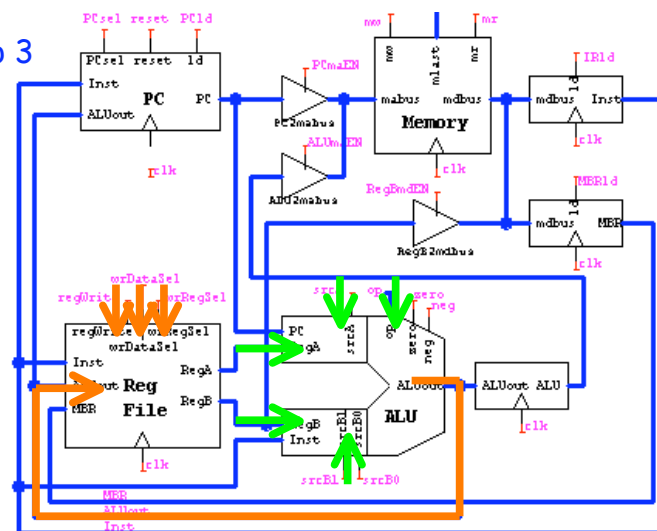

CS 150 – Fall 2005 – Lec 13: Computer Org I - 32

Register-Transfer-Level Description

■ Control

- Transfer data btwn registers by asserting appropriate control signals

- Register transfer notation: work from register to register

- Instruction fetch:
 - mbus \leftarrow PC; - move PC to memory address bus (PCmaEN, ALUmaEN)
 - memory read; - assert memory read signal (mr, RegBmdEN)
 - IR \leftarrow memory; - load IR from memory data bus (IRld)
 - op \leftarrow add - send PC into A input, 1 into B input, add
(srcA, srcB0, srcB1, op)
 - PC \leftarrow ALUout - load result of incrementing in ALU into PC (PCld, PCsel)
- Instruction decode:
 - IR to controller
 - values of A and B read from register file (rs, rt)
- Instruction execution:
 - op \leftarrow add - send regA into A input, regB into B input, add
(srcA, srcB0, srcB1, op)
 - rd \leftarrow ALUout - store result of add into destination register
(regWrite, wrDataSel, wrRegSel)

Register-Transfer-Level Description (cont'd)

- How many states are needed to accomplish these transfers?

- Data dependencies (where do values that are needed come from?)
- Resource conflicts (ALU, busses, etc.)


- In our case, it takes three cycles

- One for each step
- All operation within a cycle occur between rising edges of the clock

- How do we set all of the control signals to be output by the state machine?

- Depends on the type of machine (Mealy, Moore, synchronous Mealy)

Review of FSM Timing

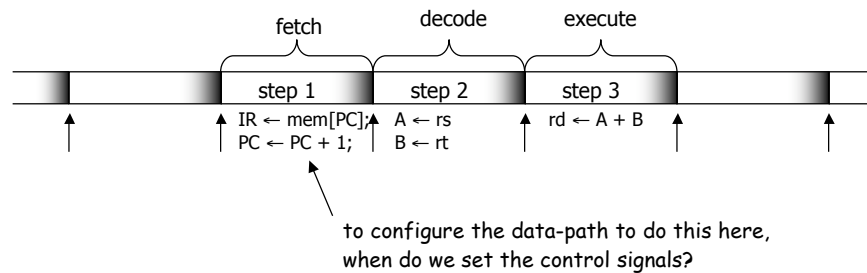


CS 150 – Fall 2005 – Lec 13: Computer Org I - 35

FSM Controller for CPU (skeletal Moore FSM)

- First pass at deriving the state diagram (Moore Machine)

- These will be further refined into sub-states

 

CS 150 – Fall 2005 – Lec 13: Computer Org I - 36

FSM Controller for CPU (reset and instruction fetch)

■ Assume Moore Machine


- Outputs associated with states rather than arcs

■ Reset state and instruction fetch sequence

■ On reset (go to Fetch state)

- Start fetching instructions
- PC will set itself to zero

```
mabus ← PC;  
memory read;  
IR ← memory data bus;  
PC ← PC + 1;
```

 


CS 150 – Fall 2005 – Lec 13: Computer Org I - 37

FSM Controller for CPU (decode)

■ Operation Decode State

- Next state branch based on operation code in instruction
- Read two operands out of register file
 - What if the instruction doesn't have two operands?

 

CS 150 – Fall 2005 – Lec 13: Computer Org I - 38


FSM Controller for CPU (Instruction Execution)

■ For add instruction

- Configure ALU and store result in register

$$rd \leftarrow A + B$$

 
- Other instructions may require multiple cycles



FSM Controller for CPU (Add Instruction)

■ Putting it all together and closing the loop

 - the famous instruction fetch decode execute cycle



FSM Controller for CPU

- Now we need to repeat this for all the instructions of our processor
 - Fetch and decode states stay the same
 - Different execution states for each instruction
 - Some may require multiple states if available register transfer paths require sequencing of steps