

Experiment Name: Gray to Binary and
Binary to Gray conversion.

Roll: 1710776121

Session: 2016-17

Course: CSE-2112


Date: 26-02-2018

Experiment: Gray to Binary conversion.

Theory: Gray to Binary conversion is a number conversion system by which we can convert a gray code to equivalent binary. In 4-bit gray to binary conversion we have to take four separate inputs as MSB to LSB corresponding. Then we have to draw a circuit to get 4 outputs as 4 binary digit. Inputs and outputs will be verified while the binary will be same to equivalent gray code.

Instruments: wire, bread-board, power source and IC-7486.

circuit:

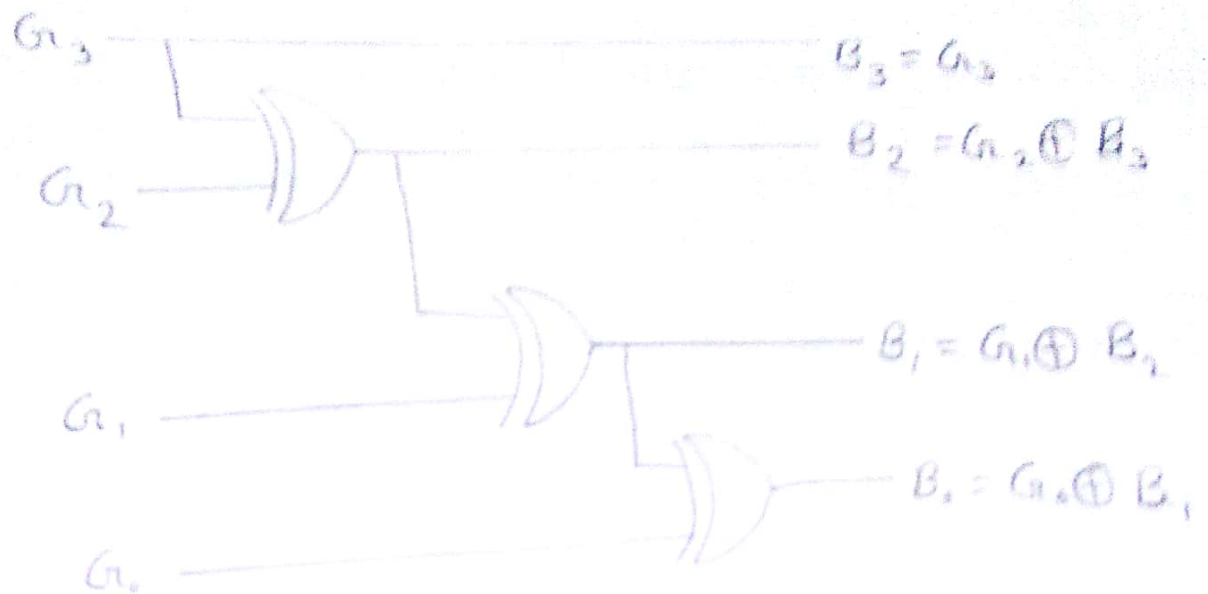

Truth Table:

G_3	G_2	G_1	G_0	Verification	B_3	B_2	B_1	B_0
0	0	0	0	✓	0	0	0	0
0	0	0	1	✓	0	0	0	1
0	0	1	1	✓	0	0	1	0
0	0	1	0	✓	0	0	1	1
0	1	1	0	✓	0	1	0	0
0	1	1	1	✓	0	1	0	1
0	1	0	1	✓	0	1	1	0
0	1	0	0	✓	0	1	1	1
1	1	0	0	✓	1	0	0	0
1	1	0	1	✓	1	0	0	1
1	1	1	1	✓	1	0	1	0
1	1	1	0	✓	1	0	1	1
1	0	1	0	✓	1	1	0	0
1	0	1	1	✓	1	1	0	1
1	0	0	1	✓	1	1	1	0
1	0	0	0	✓	1	1	1	1

Result and discussion: From the circuit we have designed the results we got is similar to equivalent binary of the given gray code. So the circuit and equations are ~~wright~~ right.

pre-caution:

1. connect the circuit when design is complete.
2. Please check the circuit before connecting.
3. Wear shoes in the lab.
4. After finishing experiment switch off the power source.


Experiment: Binary to Gray conversion.

Theory: Binary to Gray conversion oppose to gray to binary conversion. By binary to gray conversion we can get equivalent equivalent gray code of given binary.

In 4-bit of binary to gray conversion we have to take 4 separate inputs as MSB to LSB corresponding. Then we have to see if the results are equivalent.

Instruments: wire, bread-board, power source and IC-7486.

Circuit:

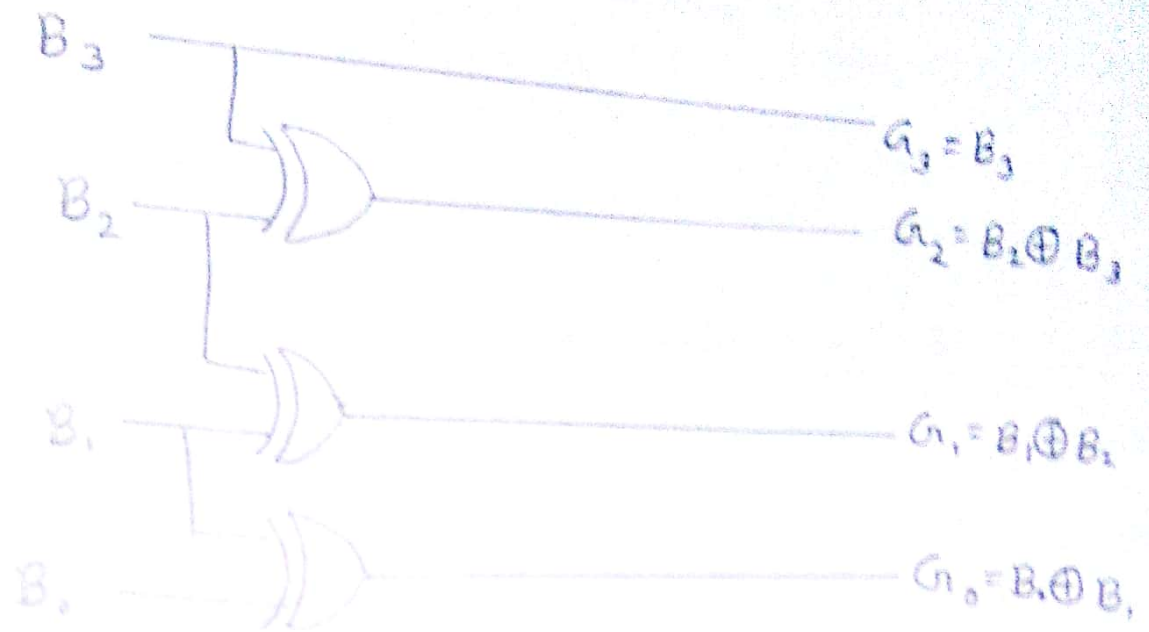

Truth Table:

B_3	B_2	B_1	B_0	Verification	G_3	G_2	G_1	G_0
0	0	0	0	✓	0	0	0	0
0	0	0	1	✓	0	0	0	0
0	0	1	0	✓	0	0	1	1
0	0	1	1	✓	0	0	1	1
0	1	0	0	✓	0	1	1	0
0	1	0	1	✓	0	1	1	0
0	1	1	0	✓	0	1	0	1
0	1	1	1	✓	0	1	0	1
1	0	0	0	✓	1	1	0	0
1	0	0	1	✓	1	1	0	0
1	0	1	0	✓	1	1	1	1
1	0	1	1	✓	1	1	1	1
1	1	0	0	✓	1	0	1	0
1	1	0	1	✓	1	0	1	0
1	1	1	0	✓	1	0	0	1
1	1	1	1	✓	1	0	0	1

Result and discussion: From the circuit we have designed the results we got is similar to equivalent gray code of given binary. So the circuit and equations are all right.

Pre-caution:

1. Connect the circuit when design is complete.
2. Please check the circuit before connecting.
3. Wear shoes in the lab.
4. After finishing experiment switch off the power source.